

## CH. 2 – PROBLEM SOLUTIONS (UPDATED DECEMBER 16, 2013)

© 2015 McGraw-Hill Education. All rights reserved.

2.1 Two conditions are necessary for successful BJT operation: (a) the emitter must be doped much more heavily than the base; (b) the emitter and collector must be separated by a thin contiguous base.

In the case of two discrete diodes, it is not known a priori whether (a) is met; (b) is certainly not met, as the two anodes are not contiguous; the holes injected from the emitter-acting anode would rather recombine with the electrons supplied by the "base" wire, than progress towards the collector-acting anode.

In the case of two half-BJTs, condition (a) is met, but condition (b) still isn't, as the two base regions, though thin, are not contiguous, but separated by interconnecting wires. The electrons supplied by those wires will recombine with the holes injected by the emitter, resulting in virtually zero collector current. Thus,  $\beta_F \cong 0/I_B = 0$ .

2.2

$$(a) I_s = 10 \times 20 \times 10^{-8} \frac{1}{10^{-4}} 2 \times 10^{20} \frac{1.6 \times 10^{-19} \times 18}{10^{17}} = 0.115 \text{ fA.}$$

$$\beta_F = \frac{1}{\frac{1.8}{18} \frac{10^{17}}{10^{19}} \frac{1}{1} + \frac{(10^{-4})^2}{2 \times 150 \times 10^{-9} \times 18}} = \frac{1}{\frac{1}{1000} + \frac{1}{540}} = 351$$

$$(b) I_C = 0.115 \times 10^{-15} \times \exp(700/26) = 56.8 \text{ } \mu\text{A}$$

$$I_B = I_C / \beta_F = 56.8 / 351 = 162 \text{ nA.}$$

$$(c) I_{BE} = 56.8 / 1000 = 57 \text{ nA; } I_{BB} = 56.8 / 540 = 105 \text{ nA.}$$


2.3

$$(a) \beta_F = 250 \Rightarrow 1/(1/x + 1/y) = 250; i_{BE} = i_{BB} \Rightarrow$$

$$x = y; 1/(1/x + 1/x) = 250 \Rightarrow x = 500$$

$$\frac{1}{500} = \frac{W_B^2}{2\tau_m D_m} = \frac{W_B^2}{2 \times 150 \times 10^{-9} \times 18} \Rightarrow W_B = 1.039 \mu\text{m}$$
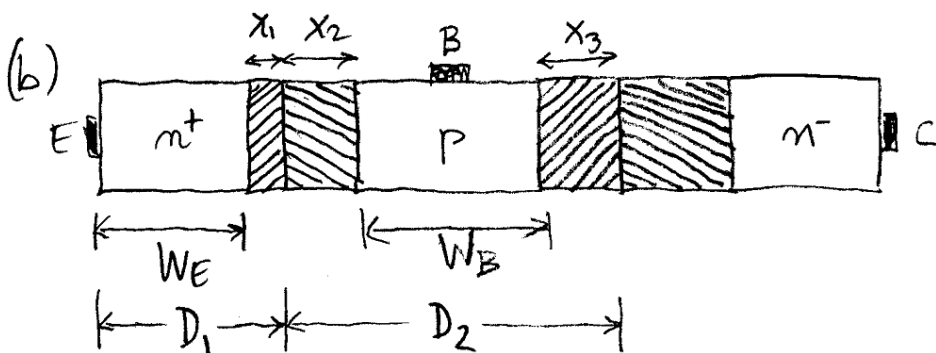
$$\frac{1}{500} = \frac{D_P N_{AB} W_B}{D_m N_{DE} W_E} = \frac{1.8 \times 10^{17} \times 1.039 \times 10^{-4}}{1.8 \times 10^{19} \times W_E} \Rightarrow W_E = 0.520 \mu\text{m}$$



$$\phi_e = 26 \ln \frac{10^{17} \times 10^{19}}{2 \times 10^{20}} = 940 \text{ mV}; \phi_c = 700 \text{ mV}$$

$$x_{20} = \sqrt{\frac{2\epsilon_{si}\phi_e}{qN_{AB}} \frac{N_{DE}}{N_{AB} + N_{DE}}} = \sqrt{\frac{2 \times 10^{-12} \times 0.94}{1.6 \times 10^{-19} \times 10^{17}} \frac{10^{19}}{10^{17} + 10^{19}}} = 108 \text{ mm}$$

$$x_{10} = \frac{N_{AB}}{N_{DE}} x_{20} = \frac{108}{100} \approx 1.1 \text{ mm}$$

$$x_{30} = \sqrt{\frac{2 \times 10^{-12} \times 0.7}{1.6 \times 10^{-19} \times 10^{17}} \frac{10^{15}}{10^{17} + 10^{15}}} = 9.4 \text{ mm}$$

$$D_1 = W_E + x_1 = 520 \text{ mm} + (1.1 \text{ mm}) \sqrt{1 - \frac{0.7}{0.94}} \approx 520 \text{ mm}$$

$$D_2 = W_B + x_2 + x_3 = 1,039 \text{ mm} + (108 \text{ mm}) \sqrt{1 - \frac{0.7}{0.94}} + (9.4 \text{ mm}) \sqrt{1 - \frac{0.7}{0.94}} \approx 1,039 + 55 + 18 = 1,112 \text{ mm}$$

2.4

$$(a) I_s = (25 \times 10^{-4})(50 \times 10^{-4}) \frac{1}{10^{-4}} \times 2 \times 10^{20} \frac{1.6 \times 10^{-19}}{10^{17}} 8 = 0.32 \text{ fA.}$$

$$\beta_F = \frac{1}{\frac{3}{8} \frac{10^{17}}{10^{19}} \frac{1}{1} + \frac{(10^{-4})^2}{2 \times 100 \times 10^{-9} \times 8}} = \frac{1}{\frac{1}{267} + \frac{1}{160}} = 100$$

$$(b) I_s = \frac{K_1}{W_B} \Rightarrow I_s \text{ doubles to } 0.64 \text{ fA.}$$

$$\beta_F = \frac{1}{K_2 W_B + K_3 W_B^2} \Rightarrow \beta_F = \frac{1}{\frac{0.5}{267} + \frac{0.5^2}{160}} = \frac{1}{\frac{1}{533} + \frac{1}{640}} = 291.$$

$$(c) I_s = 0.32 \text{ fA (unchanged).}$$

$$\beta_F = \frac{1}{K_3/W_E + 1/160} = \frac{1}{\frac{1}{267 \times 2} + \frac{1}{160}} = 123.$$

$W_B$  affects both  $I_s$  and  $\beta_F$ , and halving it will double  $I_s$  and increase  $\beta_F$  by more than a factor of 2.

$W_E$  affects only  $\beta_F$ , and doubling it will halve the B-E diffusion component of  $I_B$ , thus increasing  $\beta_F$ .

2.5

$$(a) I_E \cong \frac{4 - 0.7}{3.3} = 1 \text{ mA}; V_{EB} = 0.026 \ln \frac{10^{-3}}{4 \times 10^{-15}} = 0.682 \text{ V};$$

$$I_E = \frac{4 - 0.682}{3.3} = 1.005 \text{ mA}$$


$$\beta_F = \frac{1}{0.002 + 0.004} = 167 \Rightarrow I_B = \frac{1.005}{167 + 1} \cong 6 \mu\text{A}$$

$$I_C = I_E - I_B = 1.005 - 0.006 = 0.999 \text{ mA.}$$

$$(b) I_{EB} = 0.002 \times 0.999 \cong 2 \mu\text{A}; I_{BB} \cong 4 \mu\text{A.}$$


$$(c) I_C = 0; I_B = I_E \cong 1 \text{ mA.}$$

2.6

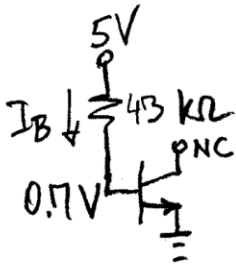

$$I_B = \frac{5 - 0.7}{43} = 100 \mu\text{A} = I_E. \quad I_C = 0$$

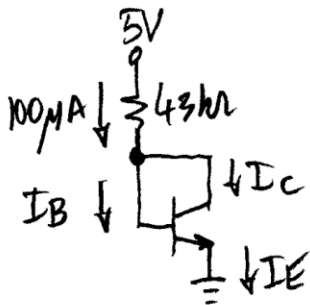About  $1 \mu\text{A}$  of holes diffusing from B to E, and  $99 \mu\text{A}$  of electrons diffusing from E to B.




$I_E = 100 \mu\text{A}$  ( $\approx 1 \mu\text{A}$  holes from B to E, and  $\approx 99 \mu\text{A}$  electrons from E to C).

$$I_C + I_B = 100 I_B + I_B = 100 \mu\text{A}$$

$\Rightarrow I_B \approx 1 \mu\text{A}$  (holes from B to E plus holes recombining with electrons within B).

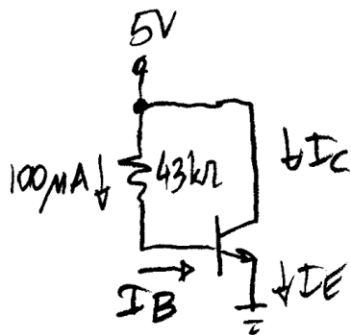$I_C \approx 99 \mu\text{A}$  (electrons from E to B to C).



$I_B = 100 \mu\text{A}$  (holes from B to E plus holes recombining with electrons within B).

$I_C = \beta_F I_B = 100 \times 0.1 = 10 \text{ mA}$  (electrons from E to B).

$I_E = I_B + I_C = 10.1 \text{ mA}$

(mostly) electrons from E to C).

2.7

$$V_B = -5 - 0.8 = -5.8 \text{ V}; \quad I_E = I_L = 500 \mu\text{A};$$

$$I_B = I_E / (\beta_F + 1) = 500 / 81 = 6.17 \mu\text{A}; \quad I_C = I_E - I_B \approx 494 \mu\text{A}.$$

2.8

$$(a) i_{o1} = \frac{1}{100} = 10 \text{ mA}; i_{o2} = 0; V_I = V_o + V_{BE1} = 1 + 0.026 \ln[(10 \times 10^{-3}) / (10 \times 10^{-15})] = 1.72 \text{ V}; i_{I1} = 10 / 151 = 66.2 \mu\text{A}.$$

$$(b) i_{o1} = 0; i_{o2} = 10 \text{ mA}; V_I = V_o - V_{EB2} = -1 - 0.026 \times \ln[(10 \times 10^{-3}) / (20 \times 10^{-15})] = -1.70 \text{ V}; i_{I2} = 10 / 101 \approx 9.9 \mu\text{A}.$$

$$(c) i_{o1} = 50 \text{ mA}; i_{I1} = 0.33 \text{ mA}; V_I = 5 + 0.76 = 5.76 \text{ V}$$

$$(d) i_{o2} = 80 \text{ mA}; i_{I2} = 0.792 \text{ mA}; V_I = -8 - 0.75 = -8.75 \text{ V}$$

2.9

$$(a) i_{c2} \approx i_{E2} = V_o / R_L = 1/8 = 125 \text{ mA}; i_{I1} = \frac{125}{101 \times 51}$$

$$\approx 24 \mu\text{A}; i_{c1} = 100 \times 24 = 2.43 \text{ mA}.$$

$$V_I = 1 + 0.026 \left[ \ln \frac{2.43 \times 10^{-3}}{10 \times 10^{-15}} + \ln \frac{125 \times 10^{-3}}{10^{-12}} \right] = 1 + 1.346 = 2.346 \text{ V}.$$

$$(b) i_{c2} \approx \frac{4}{8} = 500 \text{ mA} (= 2 \times 2 \times 125 \text{ mA}); i_{I1} \approx 97 \mu\text{A};$$

$$V_I = 4 + 1.346 + 2(18 + 18) \times 10^{-3} = 5.418 \text{ V}$$

$$(c) i_{c2} = 2 \text{ A} (= 16 \times 125 \text{ mA}); i_{I1} \approx 0.388 \text{ mA}.$$

$$V_I = 16 + 1.346 + 2(18 + 18 + 18 + 18) \times 10^{-3} = 17.490 \text{ V}.$$

2.10 (a)  $i_{C2} \approx i_{E2} = 1/4 = 250 \mu\text{A}$ ;  $i_{E1} = \frac{250}{101 \times 41} \approx 60.4 \mu\text{A}$ ;  
 $i_{C1} = 100 \times 60.4 = 6.04 \text{ mA}$ .  
 $V_{E1} = -1 - 0.026 \left[ \ln \frac{6.04 \times 10^{-3}}{5 \times 10^{-15}} + 1.5 \ln \frac{250 \times 10^{-3}}{100 \times 10^{-12}} \right] =$   
 $= -1 - (0.723 + 0.844) = -2.567 \text{ V}.$

(b)  $i_{C2} \approx i_{E2} = 5/4 = 1.25 \text{ A} (= 250 \times 10/2 \mu\text{A})$ ;  
 $i_{E1} = 60.4 \times 10/2 = 302 \mu\text{A}$ ;  
 $V_{E1} = -1 \text{ V} - [(723 + 60 - 18) \text{ mV} + (844 + 1.5 \times 60 - 1.5 \times 18) \text{ mV}]$   
 $= -1 - (0.765 + 0.907) = -2.672 \text{ V}.$

2.11 (a)  $1 \times 10^{-3} = 10^{-5} e^{V_{BE}/26 \text{ mV}} \left(1 + \frac{5}{75}\right) \Rightarrow V_{BE} \approx 717 \text{ mV}.$   
 (b)  $I_C = (1.0 \text{ mA}) \times \left[ \frac{(1 + 12/75)}{(1 + 5/75)} \right] = 1.0875 \text{ mA}$   
 $I_C = (1.0 \text{ mA}) \times \left[ \frac{(1 + 1/75)}{(1 + 5/75)} \right] = 0.95 \text{ mA}.$   
 (c)  $\Delta T = -25^\circ\text{C} \Rightarrow \Delta V_{BE} = -2(-25) = +50 \text{ mV} \Rightarrow$   
 $V_{BE} = 717 + 50 = 767 \text{ mV}.$   
 $I_C = 0.7 \text{ mA} = (1 \text{ mA}) \times (2/10) \Rightarrow \Delta V_{BE} = +18 - 60 = -42 \text{ mV};$   
 $\Delta T = 50 - 25 = +25 \text{ mV} \Rightarrow \Delta V_{BE} = -2(25) = -50 \text{ mV};$   
 $\Delta V_{(\text{net})} = -42 - 50 = -92 \text{ mV}; V_{BE} = 717 - 92 = 625 \text{ mV}.$   
 $\Delta V_{(\text{net})} = 18 + 18 - 2(40 - 25) = 6 \text{ mV}; V_{BE} = 723 \text{ mV}.$

2.12

$$(a) 500 \times 10^{-6} = 2 \times 10^{-15} e^{V_{EB}/26} \left(1 + \frac{4}{50}\right) \Rightarrow V_{EB} \approx 680 \text{ mV.}$$

$$(b) I_C = (500 \mu\text{A}) \times \left[ \frac{(1 + 1/50)}{(1 + 4/50)} \right] \approx 472 \mu\text{A.}$$

$$I_C = (500 \mu\text{A}) \left[ \frac{(1 + 8/50)}{(1 + 4/50)} \right] = 537 \mu\text{A.}$$

$$(c) 200 \mu\text{A} = 500 \mu\text{A} \times 2/10 \Rightarrow \Delta V_{EB} = +18 - 60 = -42 \text{ mV};$$

$$\Delta T = 75 - 25 = 50^\circ\text{C}; \Delta V_{EB} = (-2 \text{ mV}) 50 = -100 \text{ mV}; \Delta V_{EB} (\text{tot})$$

$$= -42 - 100 = -142 \text{ mV}; V_{EB} = 680 - 142 = 538 \text{ mV.}$$

(d)  $\Delta T = 55 - 25 = 30^\circ\text{C}$ . If we were to keep  $I_C$  constant at  $500 \mu\text{A}$ , we'd have to decrease  $V_{EB}$  by  $30 \times 2 = 60$  mV, or lower it to  $680 - 60 = 620$  mV. We are instead keeping it constant at a value  $60$  mV higher, indicating a  $10$ -fold increase in  $I_C$ , so  $I_C = 10 \times 500 = 5 \text{ mA}$ .



2.13

$$(a) I_B = \frac{5-0.7}{300} = 14.3 \mu\text{A}; I_C = \beta_F I_B = 120 \times 14.3 = 1.720 \text{ mA}; V_C = V_S - R_C I_C = 5 - 2 \times 1.720 = 1.56 \text{ V}.$$

(b) Shorting out  $R_C$  changes  $V_{CE}$  from 1.56 V to 5 V.

Since  $I_C = k(1 + V_{CE}/V_A)$ , we have

$$1.720 = k(1 + 1.56/100), I_C = k(1 + 5/100)$$

$$I_C/1.720 = (1 + 5/100)/(1 + 1.56/100) \Rightarrow I_C = 1.778 \text{ mA}.$$

$$(c) I_B = \frac{5-0.7}{30} = 0.143 \text{ mA}; I'_C = \beta_R I_B = 2 \times 0.143 = 0.286 \text{ V}; V_E = 5 - 10 \times 0.286 = 2.13 \text{ V}.$$

2.14

$$(a) I_C = \frac{5-1}{2} = 2 \text{ mA}; I_B = \frac{5-0.71}{300} = 14.3 \mu\text{A}$$

$$\Rightarrow \beta_F = 2/0.0143 \approx 140.$$

$$I_S = I_C / e^{V_{BE}/V_T} = 2 \times 10^{-3} / \exp(700/26) = 2.76 \text{ fA}.$$

$$(b) V_{CE1} = 1 \text{ V}, I_{C1} = 2 \text{ mA}; V_{CE2} = 2.950 \text{ V}, I_{C2} = (5 - 2.950)/1 = 2.05 \text{ mA}$$

$$2.05/2 = (1 + 2.950/V_A)/(1 + 1.0/V_A) \Rightarrow V_A = 77 \text{ V}.$$

$$(c) I'_C = (5 - 2)/10 = 0.3 \text{ mA}; I_B \approx (5 - 0.7)/30 = 0.143 \text{ mA};$$

$$\beta_R = 0.3/0.143 \approx 2.$$

2.15

$$(a) I_B = \frac{6 - 0.69}{470} = 11.3 \mu\text{A}; I_C = \frac{6 - 1}{3} = \frac{5}{3} \text{ mA};$$

$$\beta_F = (5/3) / 0.0113 = 147.5. (5/3) \times 10^{-3} = I_S e^{690/26} \Rightarrow$$

$$I_S \approx 5 \text{ fA. (b) } V_A / I_C = \Delta V_C / \Delta I_C \Rightarrow V_A = \frac{5 - 0}{0.1 \times 5/3} \frac{5}{3} = 50 \text{ V.}$$

$$(c) I'_C = 3.5 / 10 = 0.35 \text{ mA}; I_B \approx \frac{6 - 0.7}{20} = 0.265; \beta_R =$$

$$0.35 / 0.265 = 1.3.$$

2.16

$$(a) V_{BC} = 0 \Rightarrow I_C = (10.7 - 0.7) / 10 = 1.000 \text{ mA};$$


$$\beta_F = 1000 / 8 = 125.$$

$$(b) V_{BC} = -10 \text{ V} \Rightarrow x_p = 20 \text{ mm} \sqrt{1 - \frac{-10}{0.8}} = 73.5 \mu\text{m}.$$

$$W_B = 500 - 73.5 = 426.5 \text{ mm. } I_C = 1 \text{ mA} \frac{500}{426.5} = 1.172 \text{ mA}$$

$$(c) r_o = \frac{\Delta V_C}{\Delta I_C} = \frac{10}{0.172} = 58 \text{ k}\Omega = \frac{V_A}{I_C} \Rightarrow V_A \approx 60 \text{ V.}$$

2.17

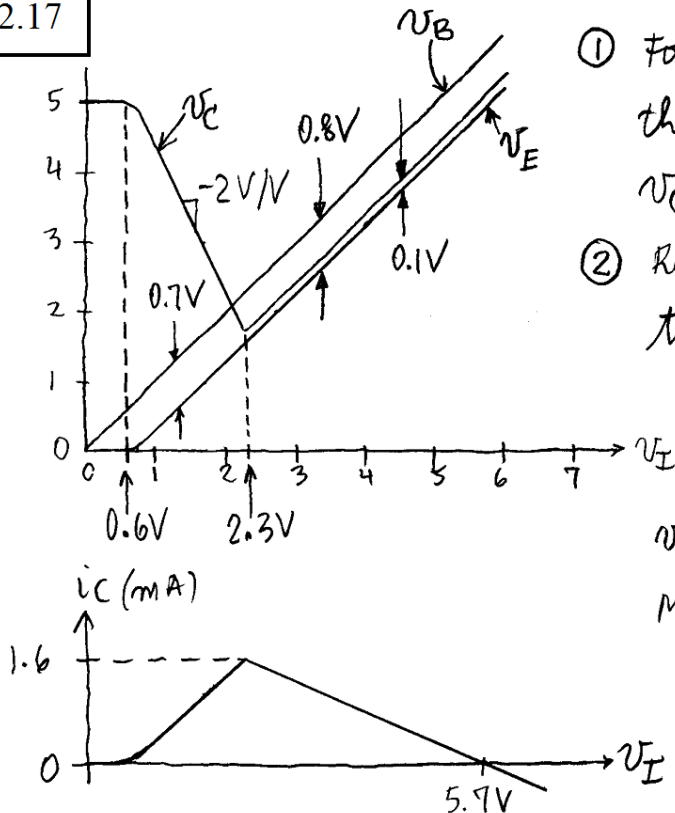

① For  $v_I < V_{BE(EO)} = 0.6V$ , the BJT is in cutoff;  $v_C = V_S = 5V$ ,  $i_C = 0$ .

② Raising  $v_I$  above  $0.6V$  turns the BJT on.

Initially, it is in FA, where

$$v_E = v_B - V_{BE(on)} = v_I - 0.7V.$$

$$\text{Moreover, } v_C = V_S - R_C i_C$$

$$\cong V_S - R_C i_E = V_S - R_C \times$$

$$\frac{v_I - V_{BE(on)}}{R_E}, \text{ or}$$


$v_C = V_S + \frac{R_C}{R_E} V_{BE(on)} - \frac{R_C}{R_E} v_I$ . Clearly, the plot of  $v_C$  v.s.  $v_I$  has a slope of  $-R_C/R_E = -2V/V$ .

③ The BJT reaches the EOS when  $\frac{v_E}{1} \cong \frac{5 - (v_E + 0.2)}{2}$ , or  $v_E = 1.6V$ . At this point,  $v_C = v_E + 0.2 = 1.8V$ , and  $v_B = 1.6 + 0.7 = 2.3V = v_I$ . Also,  $i_C = (5 - 1.8)/2 = 1.6mA$

④ As we keep increasing  $v_I$ , the BJ saturates, and  $v_E = v_I - 0.8V$ ,  $v_C = v_E + 0.1 = v_I - 0.7V$ , and  $i_C = (5 - v_C)/2 = [5 - (v_I - 0.7)]/2 = (5.7 - v_I)/2$ . Clearly,  $i_C$  now decreases with  $v_I$ .

⑤ As  $v_I$  reaches  $5.7V$ ,  $i_C$  drops to zero. For  $v_I > 5.7V$ ,  $i_C$  becomes negative. The B-C junction is forward biased, and  $i_C$  flows out of the collector!

2.18

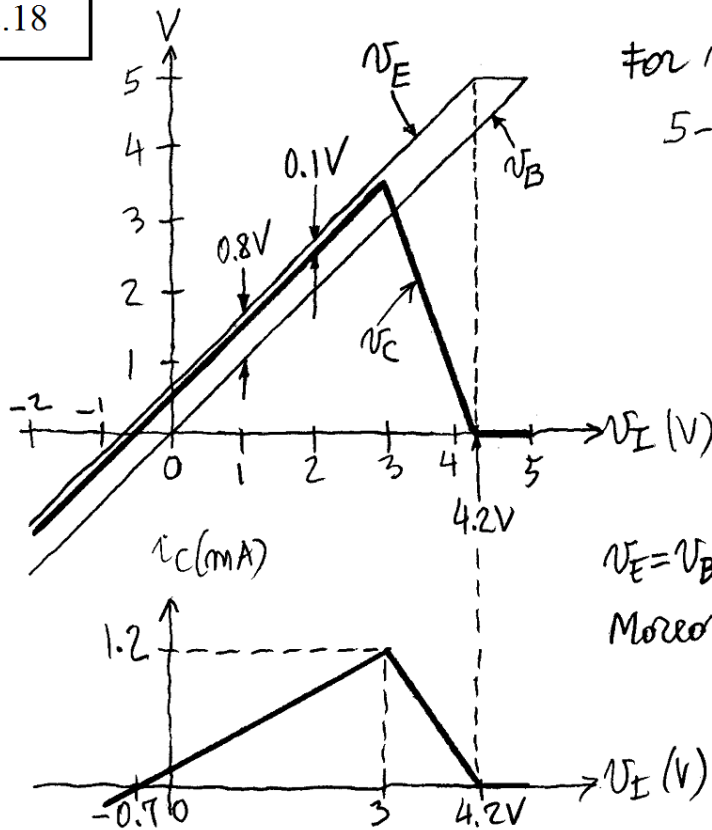

For  $V_E > V_S - V_{EB(EOC)} =$   
 $5 - 0.8 = 4.2V$ , BJT = CO

$\Rightarrow V_C = 0, i_C = 0.$

Lowering  $V_E$  below  
 $4.2V$  turns BJT  
 on, initially FA,  
 where we have

$$V_E = V_B + V_{EB(on)} = V_E + 0.8V.$$

Moreover,  $V_C = R_C i_C \approx R_C i_E$

$$= R_C \frac{V_S - V_E}{R_E}$$

$$= \frac{3}{1} (5 - V_E - 0.8)$$

or  $V_C = 3(4.2 - V_E)$ . Clearly, as  $V_E$  is lowered below  $4.2V$ ,  $V_C$  increases at the rate of  $+3V/V$ , and  $i_C$  increases at the rate of  $(3V)/(3k\Omega) = 1mA/V$ . Once  $V_C$  comes within  $0.1V$  of  $V_E$ , the BJT reaches the EOS. Imposing  $V_C = V_E - 0.1$ , or  $3(4.2 - V_E) = (V_E + 0.8) - 0.1$ , we find that the BJT reaches the EOS for  $V_E = 2.975 \approx 3V$ . At this point,  $i_C = \frac{V_C}{R_C} \approx \frac{3}{3} (4.2 - 3) = 1.2mA$ . Lowering  $V_E$  below  $3V$  drives the BJT more and more into saturation, and  $V_C = V_E - 0.1 = V_E + 0.8 - 0.1 = V_E + 0.7V$ ,  $i_C = V_C/R_C = (V_E + 0.7V)/(3k\Omega)$ . Once  $V_E$  is lowered to  $-0.7V$ ,  $i_C$  becomes 0, and turns negative (i.e. flowing into the FB B-C junction) for  $V_E < -0.7V$ .

2.19

[V, mA, kΩ].

1.  $V_S < 0.7\text{V} \Rightarrow \text{BJT} = \text{CO} \Rightarrow i_C = i_B = 0, V_C = -5\text{V}$ .2.  $V_S > 0.7\text{V} \Rightarrow \text{BJT} = \text{ON}$ , initially FA:

$$i_E = \frac{V_S - 0.7}{1}; i_B = \frac{i_E}{\beta_F + 1} = \frac{V_S - 0.7}{101}; i_C = \alpha_F i_E = \frac{100}{101} \frac{V_S - 0.7}{1} \cong$$

$$i_E = \frac{V_S - 0.7}{1}; V_C = -5 + 2 \left( \frac{V_S - 0.7}{1} \right).$$

(3) When  $V_C$  reaches  $V_{EB} - V_{EC}(\text{EOS}) = 0.7 - 0.1 = 0.6\text{V}$ , BJT reaches EOS. At this point,





$$I_C(\text{EOS}) = \frac{0.6 - (-5)}{2} = 2.8\text{mA}, V_S(\text{EOS}) = 0.7 + 1 \times I_E(\text{EOS}) \cong$$

$$0.7 + 1 \times I_C(\text{EOS}) = 0.7 + 2.8 = 3.5\text{V}; I_B(\text{EOS}) = \frac{2.8}{100} = 28\mu\text{A}.$$

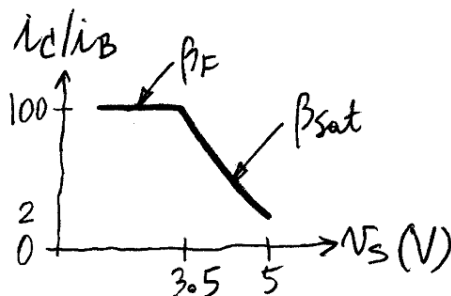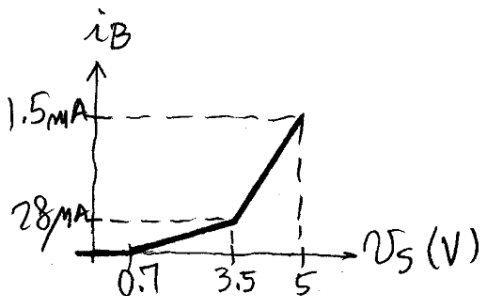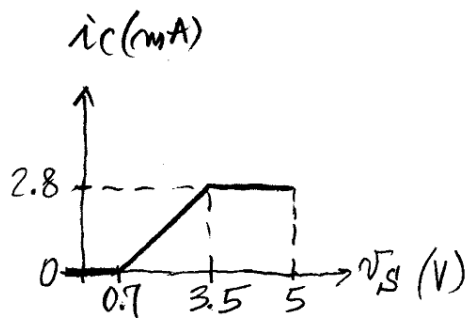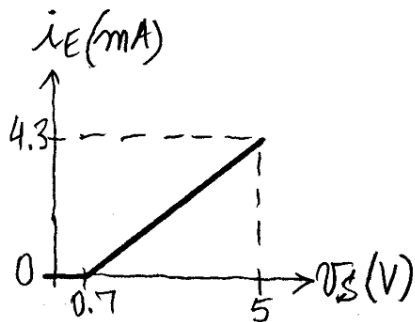(4) For  $V_S > 3.5\text{V}$ , BJT = sat:  $i_C = I_C(\text{EOS}) = 2.8\text{mA}$ ,

$$V_E = \frac{V_S - 0.7}{1}, i_B = i_E - i_C = \frac{V_S - 0.7}{1} - 2.8 = (V_S - 3.5)\text{mA}.$$

$$\frac{i_C}{i_B} = \frac{2.8}{V_S - 3.5}. \text{ For } V_S = 5\text{V}, \frac{i_C}{i_B} = \frac{2.8}{1.5} = 1.8\bar{6}.$$



2.20

(a)

$$\text{KVL: } V_{CC} = R_C I_C + V_{CE} + R_E I_E \Rightarrow 5 = 1\beta_F I_B + 2 + 2(\beta_F + 1)I_B;$$

$$\text{KVL: } V_{CC} = R_B I_B + V_{BE(m)} + R_E I_E \Rightarrow 5 = 300 I_B + 0.7 + 2(\beta_F + 1)I_B;$$

$$\Rightarrow 3 = (3\beta_F + 2) I_B, \quad 4.3 = (302 + 2\beta_F) I_B \Rightarrow$$


$$\frac{3}{4.3} = \frac{3\beta_F + 2}{302 + 2\beta_F} \Rightarrow \beta_F = 130.$$

$$(b) \text{ KVL: } 5 = 1 I_C + 0.2 + 2 I_E \cong \alpha_F I_E + 0.2 + 2 I_E \cong 0.2 + 3 I_E$$

$$\Rightarrow I_E \cong (5 - 0.2)/3 = 1.6 \text{ mA}; \quad V_E = 2 \times 1.6 = 3.2 \text{ V}; \quad V_B = 3.2 + 0.7 =$$

$$3.9 \text{ V}; \quad I_B = 1.6/131 = 12.2 \mu\text{A}; \quad R_B = (5 - 3.9)/0.0122 = 90 \text{ k}\Omega.$$
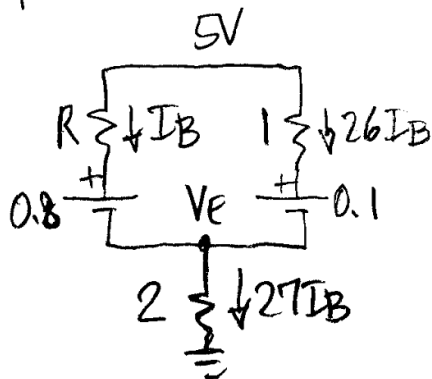
$$(c) \beta_{\text{sat}} = 130/5 = 26 \Rightarrow I_C = 26 I_B; \quad I_E = 27 I_B.$$




$$V_E = 2 \times 27 I_B = 54 I_B.$$

$$5 = 1 \times 26 I_B + 0.1 + 54 I_B \Rightarrow I_B = 61.25 \mu\text{A}.$$

$$V_B = 54 \times 0.062125 + 0.8 = 3.4075 \text{ V}.$$

$$R = (5 - 3.4075)/0.06175 = 14.6 \text{ k}\Omega.$$

2.21

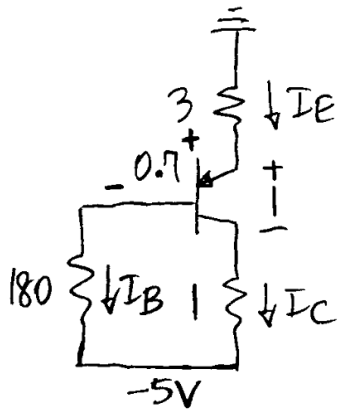(a) [V, k $\Omega$ , mA].

$$\text{KVL: } 5 = 3I_E + 1 + 1I_C, \text{ or}$$


$$4 = 3(\beta_F + 1)I_B + \beta_F I_B = (4\beta_F + 3)I_B$$

$$\text{KVL: } 5 = 3I_E + 0.7 + 180I_B, \text{ or}$$

$$4.3 = 3(\beta_F + 1)I_B + 180I_B = (3\beta_F + 183)I_B$$

Take the ratio of the two eqns:

$$\frac{4}{4.3} = \frac{4\beta_F + 3}{3\beta_F + 183} \Rightarrow \beta_F = 138$$

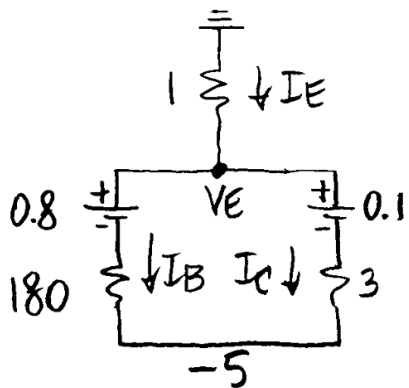(b) Swapping  $R_E$  and  $R_C$  causes the BJT to saturate.

$$\text{KCL: } \frac{0 - V_E}{1} = \frac{V_E - 0.8 - (-5)}{180} + \frac{V_E - 0.1 + 5}{3}$$

$$\Rightarrow V_E = -1.237 \text{ V. } I_E = 1.237 \text{ mA;}$$

$$I_C = 1.221 \text{ mA; } I_B = 16.5 \text{ } \mu\text{A.}$$

$$\beta_{\text{sat}} = \frac{1.221}{0.0165} = 74 < 138 (= \beta_F).$$

2.22

$$(a) \text{KVL: } V_S = V_{BE(on)} + R_1 I_B + R_2 (I_B + I_C).$$

$$I_{mFA}, 5 = 0.7 + 20 I_B + 3(1 + 150) I_B \Rightarrow I_B = 9.09 \mu A;$$


$$I_C = 150 \times 9.09 = 1.36 \text{ mA}; I_E = 1.372 \text{ mA}; \text{KVL:}$$

$$V_C = 0.7 + 20 \times 0.00909 - R_3 \times 1.36 = 0.881 - R_3 \times 1.36.$$

$$V_C(\min) = V_{CE(EOS)} = 0.2 \text{ V} \Rightarrow 0.2 = 0.881 - R_3(\max) \times 1.36 \Rightarrow$$

$$0 \leq R_3 \leq 0.5 \text{ k}\Omega.$$
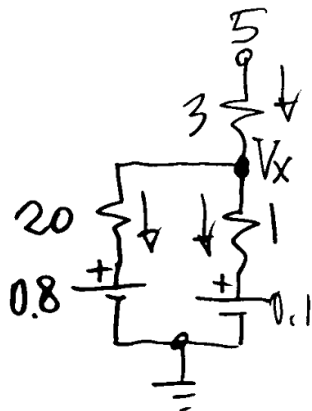
$$(b) R_3 = 2 \times 0.5 = 1 \text{ k}\Omega \Rightarrow \text{BJT} = \text{sat} \Rightarrow V_{CE} = 0.1 \text{ V}, V_{BE} = 0.8 \text{ V}.$$



$$\frac{5 - V_x}{3} = \frac{V_x - 0.8}{20} + \frac{V_x - 0.1}{1} \Rightarrow V_x = 1.306 \text{ V}.$$

$$\Rightarrow I_B = 25.3 \mu A, I_C = 1.206 \text{ mA},$$

$$\beta_{\text{sat}} = 1.206 / 0.0253 \approx 48.$$

$$(c) I_C = 0 \Rightarrow \beta_{\text{sat}} = 0 / I_B = 0.$$



2.23 (a) Assume FA, and check. By inspection,  $I_{R_2} = I_B + I_C = (\beta_F + 1)I_B = 151I_B$ . KVL:


$$9 = 20(151I_B) + 100I_B + 0.7 \Rightarrow I_B = 2.66 \mu A, I_C = 150I_B = 0.399 \text{ mA}$$

$$I_E = 151I_B = 0.402 \text{ mA. By KVL again,}$$

$$V_{CE} = V_C = V_S - R_2 I_E - R_3 I_C = 9 - 20 \times 0.402 - 1 \times 0.399 = 0.567 \text{ V}$$

$$> 0.2 \text{ V} \Rightarrow \text{FA!}$$

(b) Assume saturation, and check. KCL:

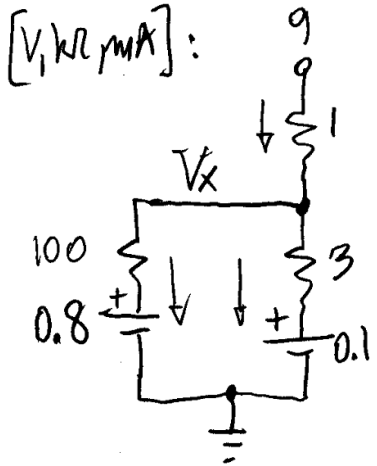

$$\frac{9 - V_x}{1} = \frac{V_x - 0.1}{3} + \frac{V_x - 0.8}{100} \Rightarrow V_x = 6.73 \text{ V}$$

$$I_B = \frac{6.73 - 0.8}{100} = 59.3 \mu A$$


$$I_C = \frac{6.73 - 0.1}{3} = 2.221 \text{ mA}$$

$$I_E = I_C + I_B = 2.28 \text{ mA}$$

$$\beta_{\text{sat}} = I_C / I_B = 2.221 / 0.0593 = 37 < 150 \Rightarrow \text{Sat!}$$

2.24

(a) [V, mA, kR]. Assume FA. KVL:

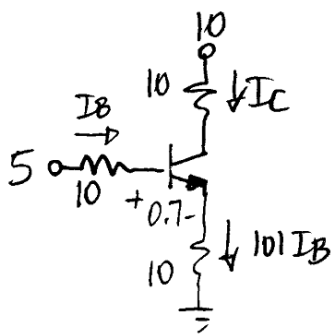

$$5 = 10I_B + 0.7 + 10(10I_B) \Rightarrow I_B = 4.2 \mu\text{A}$$



$$I_C = 0.422 \text{ mA}; I_E = 0.426 \text{ mA}$$

$$V_B = 5 - 10I_B = 4.958 \text{ V}; V_E = 4.26 \text{ V}$$

$$V_C = 10 - 10 \times 0.422 = 5.78 \text{ V}$$

$$V_{CE} = 5.78 - 4.26 = 1.52 \text{ V} > 0.2 \text{ V} \Rightarrow \text{FA!}$$

(b)

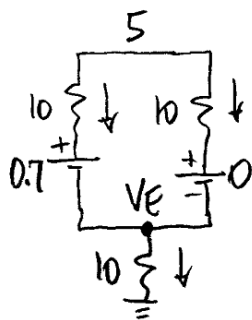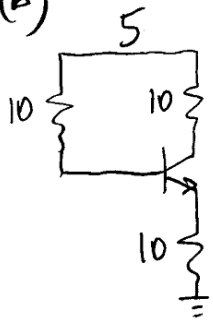

Now BJT is saturated.


KCL:

$$\frac{5 - (V_E + 0.7)}{10} + \frac{5 - V_E}{10} = \frac{V_E}{10}$$

$$\Rightarrow V_E = 3.1 \text{ V.}$$

$$I_E = 0.31 \text{ mA}; I_B = 0.12 \text{ mA}; I_C = 0.19 \text{ mA. } \beta_{\text{sat}} = \frac{0.19}{0.12} = 1.6.$$

(c)

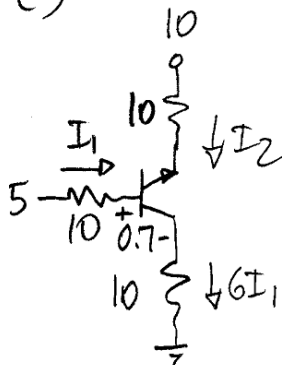

Reverse active mode. KVL:

$$5 = 10I_1 + 0.7 + 6I_1 \Rightarrow I_1 = 61.4 \mu\text{A}$$



$$I_2 = 5I_1 = 307 \mu\text{A}; 6I_1 = 369 \mu\text{A.}$$

$$V_B = 5 - 10I_1 = 4.39 \text{ V}; V_C = V_B - 0.7$$

$$= 3.69 \text{ V}; V_E = 10 - 10I_2 = 6.93 \text{ V}$$

$$V_{EC} = 6.93 - 3.69 > 0.2 \text{ V} \Rightarrow \text{RA!}$$

(d)

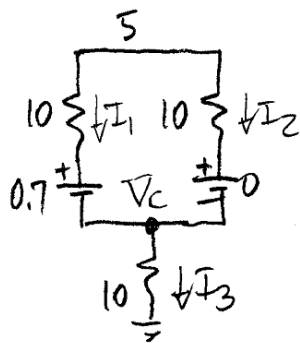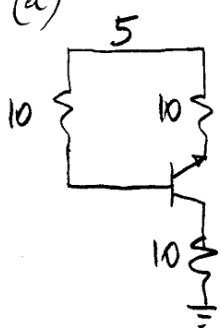

BJT is in reverse-mode

saturation. Equivalent circuit is similar to (b).


$$V_C = 3.1 \text{ V}, I_1 = 0.12 \text{ mA}$$

$$I_2 = 0.19 \text{ mA}, \beta_{\text{sat}} =$$

$$0.19/0.12 = 1.6.$$

2.25

[V, mA, kΩ].

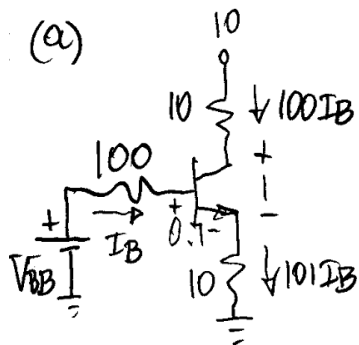


$$\text{KVL: } 10 = 10(100I_B) + 1 + 10(10I_B)$$

$$\Rightarrow I_B = 4.478 \mu\text{A};$$

$$V_E = 10 \times 10I_B = 4.522 \text{ V}; V_B = V_E + 0.7 \text{ V}$$
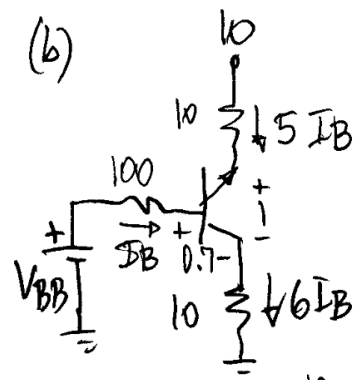
$$= 5.22 \text{ V}; V_{BB} = V_B + 100I_B = 5.67 \text{ V}.$$




$$\text{KVL: } 10 = 10(5I_B) + 1 + 10(6I_B)$$

$$\Rightarrow I_B = 81.81 \mu\text{A}$$

$$V_C = 10 \times 6I_B = 4.91 \text{ V}; V_B = 5.61 \text{ V}$$
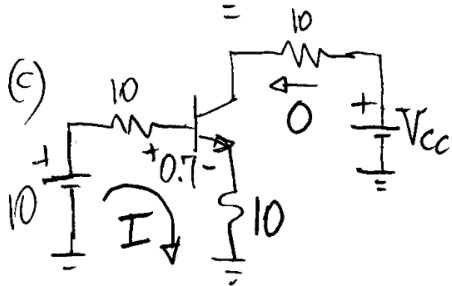
$$V_{BB} = 5.61 + 100 \times 0.081 = 13.8 \text{ V}.$$




$$I_C = 0 \Rightarrow I_B = I_E = I. \text{ KVL:}$$

$$10 = 10I + 0.7 + 10I \Rightarrow I = 0.465 \text{ mA}$$

$$\Rightarrow V_E = 4.65 \text{ V}, V_B = 5.35 \text{ V}.$$
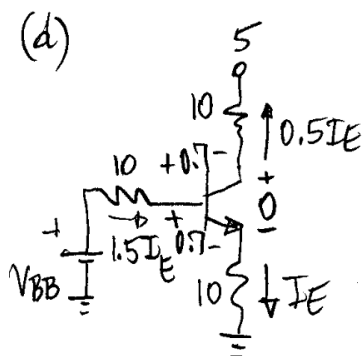
$$\text{For } I_C = 0, V_{CC} \approx V_B - 0.65 = 4.7 \text{ V}.$$



$$I_B = 1.5I_E \Rightarrow I_C = -0.5I_E \text{ (out of collector)}$$


$$\Rightarrow \beta_{\text{sat}} = (-0.5I_E) / (1.5I_B) = -\frac{1}{3} < \beta_F \Rightarrow \text{sat.}$$

$$\Rightarrow V_{BC} = V_{BE} = 0.7 \text{ V} \Rightarrow 10I_E = 5 + 10(0.5I_E)$$

$$\Rightarrow I_E = 1 \text{ mA} \Rightarrow V_{BB} = 10(1.5 \times 1) + 0.7 + 10(1) = 25.7 \text{ V}.$$

2.26

(a) [V, mA, kΩ].

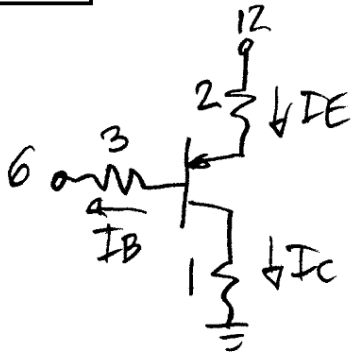

Assume FA: KVL:

$$12 = 2 \times 15 I_B + 0.7 + 3 I_B + 6$$


$$\Rightarrow I_B = 17.4 \mu\text{A}, I_C = 2.61 \text{ mA}$$

$$I_E = 2.62 \text{ mA}, V_B = 6.052 \text{ V},$$

$$V_E = 6.752 \text{ V}, V_C = 2.607 \text{ V}$$

$$V_{EC} = 4.14 \text{ V} > 0.1 \text{ V} \Rightarrow \text{FA!}$$

(b)

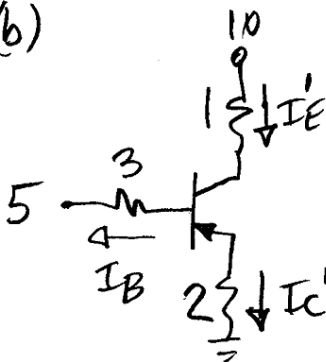

Assume RA: KVL

$$10 = 1 \times 5 I_B + 0.7 + 3 I_B + 5$$

$$\Rightarrow I_B = 0.5375 \text{ mA}$$

$$I_C' = 4 \times 0.5375 = 2.15 \text{ mA}$$

$$I_E' = 5 \times 0.5375 = 2.6875 \text{ mA}$$

$$V_B = 5 + 3 \times 0.5375 = 6.6125 \text{ V}; V_C = 6.6125 + 0.7 = 7.3125 \text{ V};$$

$$V_E = 2 \times 2.15 = 4.3 \text{ V}. 7.3125 - 4.3 > 0.1 \Rightarrow \text{RA!}$$

(c)



Assume sat: KCL:

$$\frac{6 - V_E}{2} = \frac{V_E - 0.7}{3} + \frac{V_E - 0}{1}$$

$$\Rightarrow V_E = 1.736 \text{ V}$$

$$V_C = 1.736 \text{ V}$$


$$I_C = 1.736 \text{ mA}$$

$$V_B = 1.036 \text{ V}$$


$$I_B = 1.036 / 3 = 0.345 \text{ mA}; \beta_{\text{sat}} = 1.736 / 0.345 \approx 5 < \beta_F$$

$$\Rightarrow \text{Sat!}$$


2.27 [V, mA, kΩ].

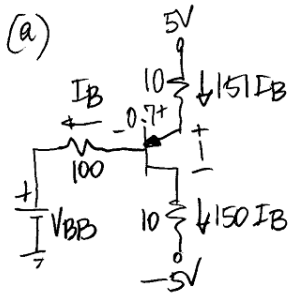

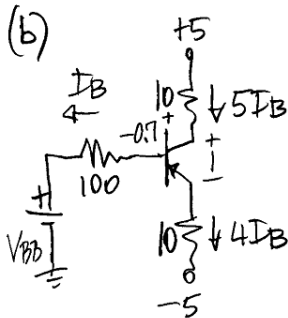
$$\begin{aligned} \text{kVL: } 5 - (-5) &= 10(151I_B) + 1 + 10(150I_B) \\ \Rightarrow I_B &= 2.99 \text{ mA} \\ V_{BB} &= 5 - 10(151I_B) - 0.7 - 100I_B \\ &= -0.514 \text{ V.} \end{aligned}$$



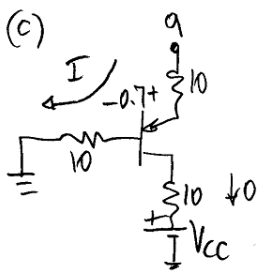
$$\begin{aligned} 10 &= 10(5I_B) + 1 + 10(4I_B) \\ \Rightarrow I_B &= 0.1 \text{ mA} \\ V_{BB} &= 5 - 10(5 \times 0.1) - 0.7 - 100 \times 0.1 \\ &= -10.7 \text{ V} \end{aligned}$$


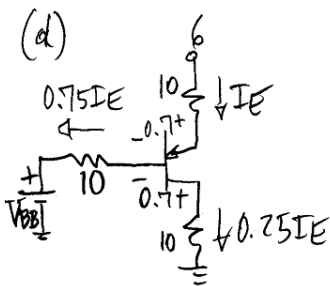
$$\begin{aligned} I_C = 0 \Rightarrow I_B = I_E = I. \text{ kVL:} \\ 9 &= 10I + 0.7 + 10I \Rightarrow I = 0.415 \text{ mA.} \\ V_B &= 10I = 4.15 \text{ V. For } I_C = 0, \text{ need} \\ V_{CC} &\cong V_B + 0.65 = 4.15 + 0.65 = 4.8 \text{ V.} \end{aligned}$$



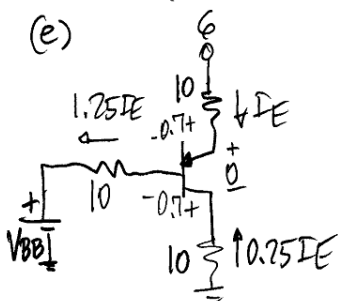
$$\begin{aligned} I_B = 0.75I_E \Rightarrow I_C = 0.25I_E, \text{ by kCL.} \\ \beta_{\text{sat}} = I_C / I_B = (0.25I_E) / (0.75I_E) = \frac{1}{3} \\ \frac{1}{3} < 150 \Rightarrow \text{saturation} \Rightarrow V_{EC} = 0 \\ \text{kVL: } 6 &= 10I_E + 10(0.25I_E) \Rightarrow \\ I_E &= 0.48 \text{ mA. kVL:} \\ V_{BB} &= 6 - 10(0.48) - 0.7 - 10(0.75 \times 0.48) = -3.1 \text{ V.} \end{aligned}$$



$$\begin{aligned} I_B = 1.25I_E \Rightarrow I_C = 0.25I_E \text{ (into the collector).} \\ \beta_{\text{sat}} = (-0.25I_E) / (1.25I_E) = -0.2 < 150 \Rightarrow \text{saturation} \Rightarrow \\ V_{EC} &= 0. \text{ kVL:} \\ 6 + 10(0.25I_E) &= 10I_E \Rightarrow I_E = 0.8 \text{ mA.} \\ V_{BB} &= 6 - 10(0.8) - 0.7 - 10(1.25 \times 0.8) = -12.7 \text{ V.} \end{aligned}$$

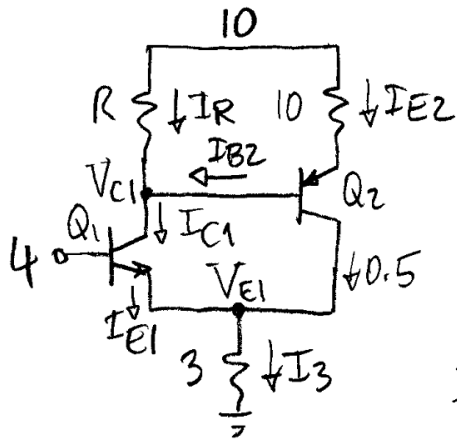2.28

$[V, mA, k\Omega]$ . Assume  $Q_1 = Q_2 = FA$ .  $I_{E2} = \frac{51}{50} 0.5 = 0.51 \text{ mA}$ .



$$\text{kVL: } V_{E2} = 10 - 10 \times 0.51 = 4.9 \text{ V. kVL:}$$

$$V_{B2} = 4.9 - 0.7 = 4.2 \text{ V} = V_{C1}. \text{ kCL:}$$

$$I_{E1} = I_3 - I_{C2} = \frac{4 - 0.7}{3} - 0.5 = 0.6 \text{ mA.}$$

$$I_{C1} = \frac{55}{56} 0.6 = \frac{33}{56} \text{ mA. kCL:}$$

$$I_R = I_{C1} - I_{B2} = \frac{33}{56} - \frac{0.5}{50} = \frac{811}{1400} \text{ mA.}$$


$$\text{Ohm: } R = \frac{10 - 4.2}{811/1400} = 10.0 \text{ k}\Omega. \text{ Check: } V_{CE1} = 4.2 - (4 - 0.7) > 0.2 \text{ V}$$

$$\Rightarrow Q_1 = FA. V_{EC2} = 4.9 - (4 - 0.7) > 0.2 \text{ V} \Rightarrow Q_2 = FA.$$

$$I_{4V} = I_{B1} = I_{C1} / \beta_{FE1} = (33/56) / 55 = 10.7 \text{ }\mu\text{A.}$$

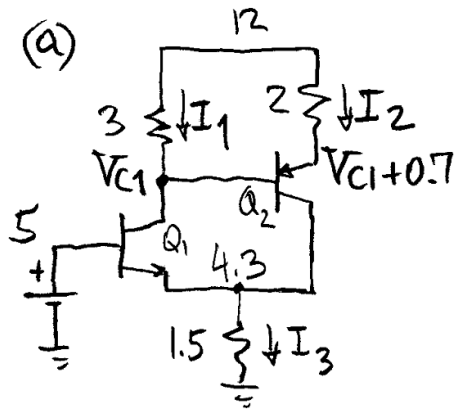2.29

$[V, mA, k\Omega]$ . Assume  $Q_1 = Q_2 = FA$ , and check.  $V_{E1} = V_{C2} =$



$5 - 0.7 = 4.3V$ . Ignoring base currents,

$$I_3 = I_{E1} + I_{C2} \approx I_1 + I_2, \text{ or}$$

$$\frac{4.3}{1.5} = \frac{12 - V_{C1}}{3} + \frac{12 - (V_{C1} + 0.7)}{2}$$


$$\Rightarrow V_{C1} = 8.14V \Rightarrow I_{C1} \approx I_1 = \frac{12 - 8.14}{3} \approx$$

$$1.29mA; I_{C2} \approx I_2 = \frac{12 - (8.14 + 0.7)}{2} \approx$$

$$1.58mA; V_{CE1} = 8.14 - 4.3 = 3.84V (\Rightarrow 0.1V \Rightarrow \text{Sat}); V_{CE2} =$$

$$(8.14 + 0.7) - 4.3 = 4.54V (\Rightarrow 0.1V \Rightarrow \text{Sat}). \text{ Consequently,}$$
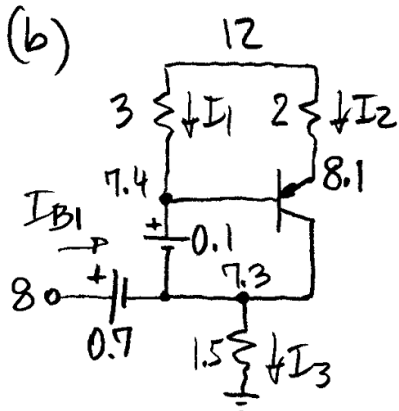
$$Q_1 = Q_1(1.29mA, 3.84V), Q_2 = Q_2(1.58mA, 4.54V).$$



Assume  $Q_1 = \text{Sat}$ ,  $Q_2 = FA$ , and check.

$$V_{E1} = V_{C2} = 8 - 0.7 = 7.3V; I_3 = 7.3/1.5 = 4.87mA; V_{C1} = V_{B2} = 7.3 + 0.1 = 7.4V;$$


$$V_{E2} = V_{B2} + 0.7 = 8.1V. I_1 = (12 - 7.4)/3 = 1.53mA; I_2 = (12 - 8.1)/2 = 1.95mA.$$

$$Q_2 = Q_2(1.95mA, 0.8V), FA. \text{ KCL:}$$

$$I_{B1} = I_3 - (I_1 + I_2) = 4.87 - (1.53 + 1.95) = 1.38mA. I_{C1}/I_{B1} \approx$$

$$I_1/I_{B1} = 1.53/1.38 = 1.1 \Rightarrow Q_1 = \text{Sat}, \text{ and } Q_1 = (1.53mA, 0.1V).$$

2.30

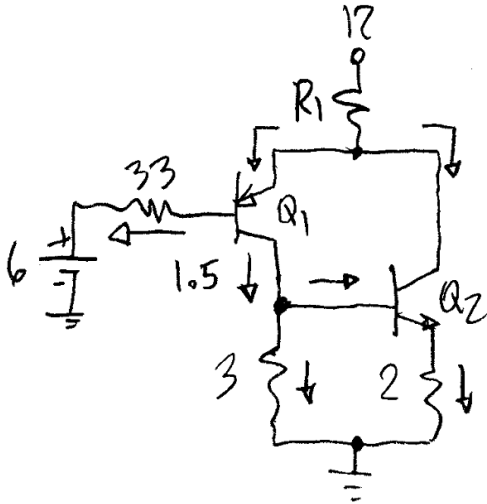(a)  $[V, mA, k\Omega]: KCL: 15 = I_{3k\Omega} + I_{B2} = I_{3k\Omega} + I_{E2}/(\beta_2 + 1)$ 

$$15 = \frac{V_{C1}}{3} + \frac{1}{50+1} \frac{V_{C1}-0.7}{2} \Rightarrow V_{C1} = 4.39V$$

$$I_{E2} = \frac{4.39 - 0.7}{2} = 1.85 mA$$

$$I_{C2} = \frac{50}{51} I_{E2} = 1.81 mA$$

$$I_{E1} = \frac{51}{50} I_{C1} = \frac{51}{50} 1.5 = 1.53 mA$$

$$I_{R1} = I_{E1} + I_{C2} = 3.34 mA$$

$$I_{B1} = I_{C1}/\beta_1 = 1.5/50 = 0.03 mA; V_{B1} = 6 + 33 \times 0.03 = 6.99 V;$$

$$V_{E1} = V_{B1} + 0.7 = 7.69 V. R_1 = (12 - 7.69)/3.34 \approx 1.3 k\Omega.$$

$$\text{Check: } V_{EC1} = (12 - 1.3 \times 3.34) - 4.39 \approx 3.3 V \gg 0.1 V \Rightarrow \text{FA.}$$

$$V_{CE2} = (12 - 1.3 \times 3.34) - (4.39 - 0.7) \approx 4 V \gg 0.1 V \Rightarrow \text{FA.}$$


(b) The base currents can be ignored, except when calculating the voltage drop across  $R_2$ . Thus,

$$V_{C1} \approx 3 \times 1.5 = 4.5 V; I_{E2} \approx (4.5 - 0.7)/2 = 1.9 mA; I_{R1} \approx$$

$$1.5 + 1.9 = 3.4 mA; R_1 = (12 - 7.69)/3.4 = 1.27 k\Omega \approx 1.3 k\Omega.$$



2.31

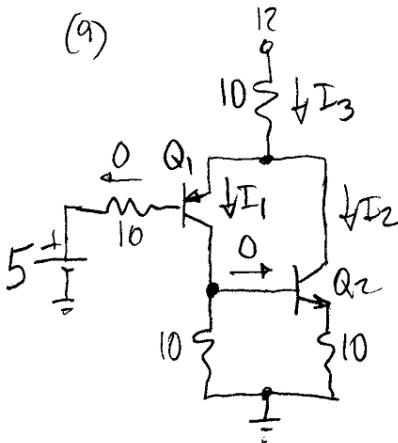[V, mA, kΩ]. Assume  $Q_1 = Q_2 = FA$ , and check.Ignoring  $I_{B1}$  and  $I_{B2}$ , we have, by KVL,

$$V_{C2} = V_{E1} = V_{B1} + 0.7 \approx 5 + 0.7 = 5.7 \text{ V}, \Omega:$$


$$I_3 = (12 - 5.7) / 10 = 0.63 \text{ mA}. \text{ KCL:}$$

$$I_3 = I_1 + I_2 \Rightarrow 0.63 \approx \frac{V_{C1}}{10} + \frac{V_{C1} - 0.7}{10}$$

$$\Rightarrow V_{B2} = V_{C1} = 3.5 \text{ V} \Rightarrow I_{C1} = \frac{3.5}{10} = 0.35 \text{ mA}.$$

$$I_{C2} = 0.63 - 0.35 = 0.28 \text{ mA}.$$

$V_{E1} = 5.7 - 3.5 = 2.2 \text{ V} \gg 0.1 \text{ V} \Rightarrow FA$ ;  $V_{CE2} = 5.7 - (3.5 - 0.7) = 2.9 \text{ V} \gg 0.1 \text{ V} \Rightarrow FA$ . Thus,  $Q_1 = Q_1(0.35 \text{ mA}, 2.2 \text{ V})$ ;  $Q_2 = Q_2(0.28 \text{ mA}, 2.9 \text{ V})$ .

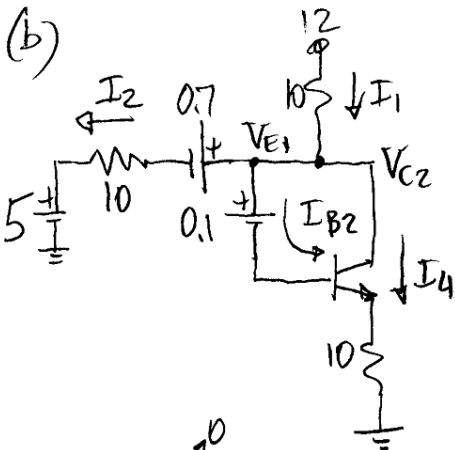With  $R_3$  out of the way,  $I_{C1}$  $= I_{B2} = \text{very small}$ , so weexpect  $I_{C1}/I_{B1} \ll \beta_{F1} \Rightarrow \text{sat.}$ Thus, assume  $Q_1 = \text{sat.}$  Byinspection,  $V_{CE2} = 0.7 + 0.1 =$  $0.8 \text{ V} > 0.1 \text{ V} \Rightarrow Q_2 = FA$ .Let  $V_x = V_{E1} = V_{C2}$ . KCL:

$$I_1 = I_2 + I_{B2} + I_4 \approx I_2 + I_4, \text{ or}$$

$$\frac{12 - V_x}{10} = \frac{(V_x - 0.7) - 5}{10} + \frac{(V_x - 0.1) - 0.7}{10} \Rightarrow V_x = 6.1\bar{6} \text{ V}.$$

$$I_{B1} = I_2 = \frac{(6.1\bar{6} - 0.7) - 5}{10} = 0.04\bar{6} \text{ mA}; I_{C2} \approx I_4 = \frac{(6.1\bar{6} - 0.1) - 0.7}{10}$$

$$= 0.53\bar{6} \text{ mA}. I_{C1} = I_{B2} = I_{C2} / \beta_{F2}. \text{ Assuming } \beta_{F2} > 100,$$

we have  $I_{C1} < 0.53\bar{6} / 100 = 5.3\bar{6} \mu\text{A} \Rightarrow \beta_{\text{sat}1} < 5.3\bar{6} / 46.6$  $\approx 0.1 \Rightarrow Q_1 = \text{sat.}$  Thus,  $Q_1 = Q_1(< 5.3\bar{6} \mu\text{A}, 0.1 \text{ V})$ , and $Q_2 = Q_2(0.53\bar{6} \text{ mA}, 0.8 \text{ V})$ .

2.32

[V, mA, k $\Omega$ ]. Use KVL, KCL, Ohm's law repeatedly.

$$V_{CC} = R_4 I_{C2} + V_{EC2}(E05) + R_5 I_2 \cong (R_4 + R_5) I_{C2} + V_{EC2}(E05) \Rightarrow$$

$$15 \cong 2.2 I_{C2} + 0.2 \Rightarrow I_{C2} = 6.72 \text{ mA.}$$

$$V_{E2} = 1 \times 6.72 = 6.72 \text{ V}; V_{B2} = 6.72 - 0.7 = 6.027 \text{ V} = V_{C1}.$$

$$I_{B2} = 6.72 / 100 = 67.27 \mu\text{A}$$

$$I_{C1} = (15 - 6.027) / 30 + 67.27 \times 10^{-3} = 0.3663 \text{ mA. Assume } Q_1 = FA.$$

$$I_{B1} = 0.3663 / 100 = 3.66 \mu\text{A}$$

$$V_{B1} = V_1 - R_1 I_{B1} = 5 - 110 \times 3.66 \times 10^{-3} \cong 4.6 \text{ V}$$

$$V_{E1} = 4.6 - 0.7 = 3.9 \text{ V}$$

$$I_{E1} \cong I_{C1} = 0.37 \text{ mA}$$

$$R_3 = 3.9 / 0.37 = 10.5 \text{ k}\Omega$$

$$V_{CE1} = 6.027 - 3.9 \gg 0.2 \Rightarrow Q_1 = FA.$$

2.33

Consider  $Q_1$  first, and assume FA. KVL, KCL,  $\beta$ :

$$I_{B1} = \frac{5 - 0.7}{110 + 101 \times 18} = 2.23 \text{ mA}$$


$$V_{B1} = 5 - 110 \times 2.23 \times 10^{-3} = 4.75 \text{ V}; V_{E1} = 4.05 \text{ V}$$

$$I_{C1} = 100 \times 2.23 = 0.223 \text{ mA}$$

$$V_{C1} = 15 - 30 \times 0.223 = 8.31 \text{ V}$$

$V_{CE1} = 8.31 - 4.05 >> 0.2 \Rightarrow Q_1 = \text{FA}$ . Equivalent ckt:

Assume  $Q_2 = \text{FA}$ .

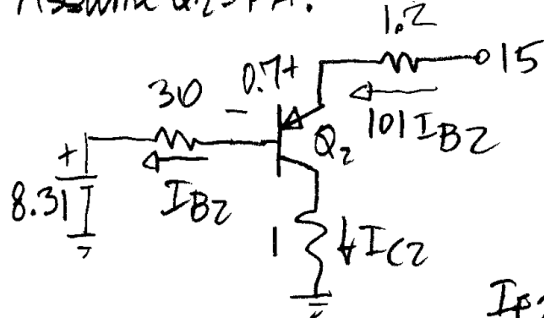

$$I_{B2} = \frac{15 - 8.31 - 0.7}{30 + 101 \times 1.2} \approx 39.6 \mu\text{A}$$



$$V_{B2} = 8.31 + 30 \times 39.6 \times 10^{-3} = 9.5 \text{ V}$$

$$V_{E2} = 9.5 + 0.7 = 10.2 \text{ V}$$

$$I_{E2} \approx I_{C2} = 100 I_{B2} = 3.96 \text{ mA}$$

$V_{C2} = 1 \times 3.96 \approx 4 \text{ V}$ .  $V_{EC2} = 10.2 - 4 >> 0.2 \Rightarrow Q_2 = \text{FA}$ .

2.34

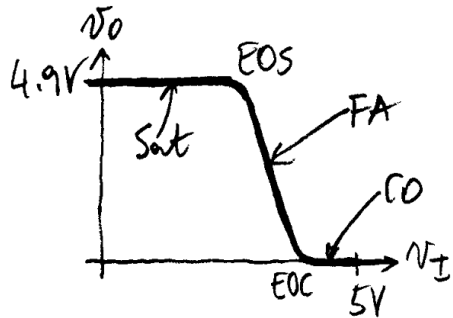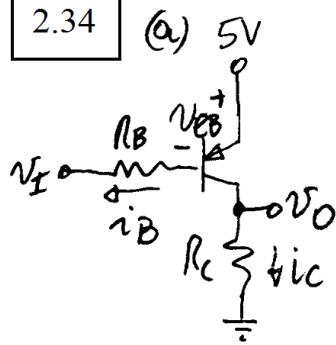

For  $v_I > V_{CC} - V_{EB}(EOC) \approx 5 - 0.6 = 4.4V$ , the BJT is in cutoff. Lowering  $v_I$  below 4.4V drives the BJT in FA:

$$\begin{aligned} v_I &= V_{CC} - V_{EB} - R_B i_B \\ &= V_{CC} - V_T \ln \frac{v_O/R_C}{I_S} - R_B \frac{v_O/R_C}{\beta F} \\ &= 5 - 0.026 \ln \frac{v_O}{10^3 \times 10^{-15}} - \frac{10}{1} \frac{v_O}{80}, \text{ or} \end{aligned}$$

$$v_I = 5 - \frac{v_O}{8} - 0.026 \ln(10^{12} v_O).$$

The EOS is reached when  $v_O = V_{CC} - V_{EC}(\text{sat}) = 5 - 0.1 = 4.9V$ .

This occurs for  $v_I = 5 - \frac{4.9}{8} - 0.026 \ln(10^{12} \times 4.9) = 3.628V$ .

$$(b) v_I = 5 - \frac{4}{8} - 0.026 \ln(10^{12} \times 4) = 3.746V$$

$$(c) \frac{dv_I}{dv_I} = -\frac{1}{8} \frac{dv_O}{dv_I} - 0.026 \frac{1}{10^{12} v_O} 10^{12} \frac{dv_O}{dv_I}, \text{ or}$$

$$1 = -\frac{a}{8} - 0.026 \frac{a}{v_O} \Rightarrow a = \frac{-8v_O}{v_O - 0.208}; a|_{v_O=4V} = -8.44 V/V.$$

2.35

$$(a) \text{ KVL: } v_I = R_B i_{RB} + v_{BE} = R_B (i_B + \frac{v_{BE}}{R_{BE}}) + v_{BE} = R_B i_B + (1 + R_B/R_{BE}) v_{BE}.$$

$$(b) v_I = 10^4 \left( \frac{5 - v_0}{10^3} \right) / 100 + \left( 1 + \frac{10}{5} \right) 0.026 \ln \frac{5 - v_0}{10^3 \times 2 \times 10^{-15}}$$

$$v_I = \frac{5 - v_0}{10} + 0.078 \ln \frac{5 - v_0}{2 \times 10^{-12}}.$$

$$(c) v_I = \frac{5 - 2.5}{10} + 0.078 \ln \frac{5 - 2.5}{2 \times 10^{-12}} = 0.25 + 2.173 = 2.423 \text{ V}$$

(shifted to the right by about  $2V_{BE}$ 's).


$$(d) \frac{dv_I}{dv_I} = \frac{1}{10} \frac{dv_0}{dv_I} + 0.078 \frac{2 \times 10^{-12}}{5 - v_0} \left( -\frac{1}{2 \times 10^{-12}} \frac{dv_0}{dv_I} \right) \Rightarrow$$

$$1 = -\frac{a}{10} - 0.078 \frac{a}{5 - v_0} \Rightarrow a = -10 \frac{5 - v_0}{5.78 - v_0}.$$

@  $v_0 = 2.5 \text{ V}$ ,  $a = -7.62 \text{ V/V}$ . In the example,  $a = -9.06 \text{ V/V}$ .

Reduced gain stems from the presence of  $R_{BE}$ , which forms an input voltage divider with  $R_B$ .

2.36

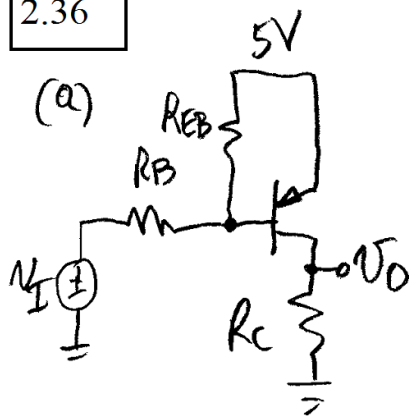

$$V_I = 5 - V_{EB} - R_B \left( i_B + \frac{V_{EB}}{R_{EB}} \right)$$

$$= 5 - R_B i_B - \left( 1 + \frac{R_B}{R_{EB}} \right) V_{EB}, \quad i_B = \frac{I_C}{\beta} = \frac{V_O}{80 \times 10^3}$$

$$\text{Impose } 2.5 = 5 - 10^4 \frac{2.5}{80 \times 10^3} - \left( 1 + \frac{10^4}{R_{EB}} \right) \times$$

$$\times 0.026 \ln \frac{2.5/10^3}{10^{-15}} \Rightarrow R_{EB} \cong 5 \text{ k}\Omega$$

(b)  $V_I = 5 - 10 \frac{V_O}{80 \times 10^3} - 3 \times 0.026 \ln V_O / (10^3 \times 10^{-15})$ , or


$$V_I = 5 - \frac{1}{8} V_O - 0.078 \ln(10^{12} V_O). \text{ Differentiate wrt } V_I:$$

$$1 = -\frac{1}{8} \frac{dV_O}{dV_I} - 0.078 \left[ \frac{1}{10^{12} V_O} \times 10^{12} \frac{dV_O}{dV_I} \right]$$

$$1 = -\frac{1}{8} \frac{dV_O}{dV_I} - \frac{0.078}{V_O} \frac{dV_O}{dV_I} \Rightarrow \frac{dV_O}{dV_I} = \frac{1}{0.078/V_O - 1/8}$$

$$\text{For } V_O = 2.5 \text{ V, gain} = \frac{1}{0.078/2.5 - 1/8} = -10.7 \text{ V/V}$$

2.37

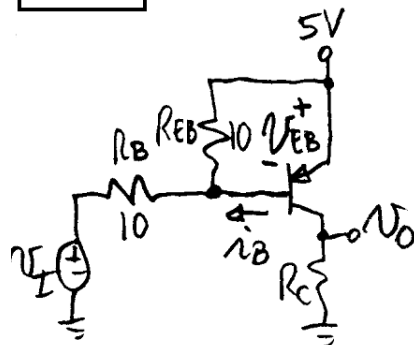

$$(a) [V, mA, k\Omega]. \quad v_I = V_{CC} - v_{EB} - R_B \left( i_B + \frac{v_{EB}}{R_{EB}} \right)$$

$$= V_{CC} - R_B i_B - (1 + R_B/R_{EB}) v_{EB}$$

$$= 5 - 10^4 i_B - 2 v_{EB}$$

$$(b) i_B = i_C / \beta_F = \frac{v_O}{R_C \beta_F} = \frac{v_O}{2 \times 10^3 \times 125} = \frac{v_O}{25 \times 10^4}$$



$$v_I = 5 - 10^4 \frac{v_O}{25 \times 10^4} - 2 \times 0.026 \ln \frac{v_O / (2 \times 10^3)}{5 \times 10^{-15}}$$

$$\Rightarrow v_I = 5 - \frac{v_O}{25} - 0.052 \ln(10^{11} v_O)$$


$$v_{I1} = 5 - \frac{2}{25} - 0.052 \ln(10^{11} \times 2) = 3.567 \text{ V}$$

$$v_{I2} = 5 - \frac{3}{25} - 0.052 \ln(10^{11} \times 3) = 3.506 \text{ V}$$
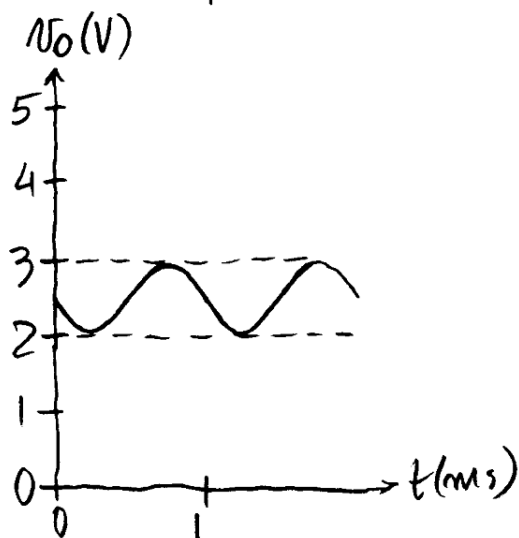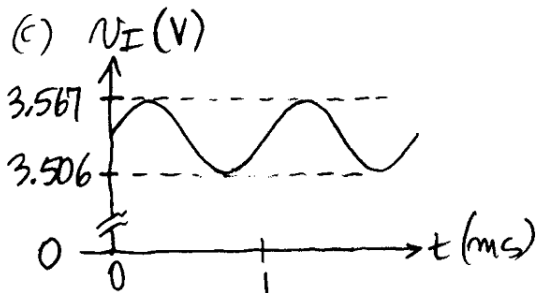
$$a = (3-2) / (3.506 - 3.567) = (1 \text{ V}) / (-61 \text{ mV}) \cong -16.4 \text{ V/V}_0$$



2.38

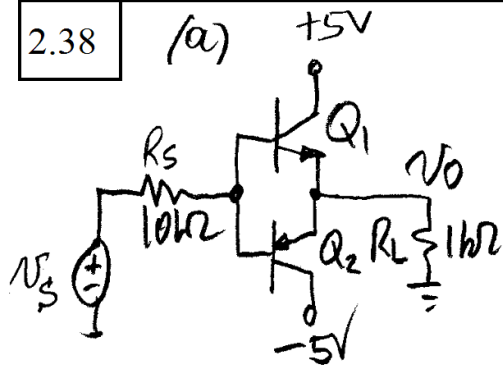

VTC is symmetric, so investigate the case  $V_I \geq 0$ . [V, mA, k $\Omega$ ].

$$0 \leq V_I < 0.6 \Rightarrow Q_1 = CO.$$

$$V_I = 0.6V \Rightarrow Q_1 = EDC.$$


$$0 < V_O < 5 - 0.2 = 4.8V \Rightarrow Q_1 = FA.$$

$$V_O = 4.8V \Rightarrow Q_1 = EOS, \text{ and}$$

$$V_I = 4.8 + 0.7 + R_S I_B \\ = 5.5 + 10 \times \frac{1}{100} \frac{4.8}{1} \\ = 5.55V.$$

$$V_I > 5.55V \Rightarrow Q_1 = \text{sat}$$

$$\Rightarrow V_O = 5 - 0.1 = 4.9V.$$

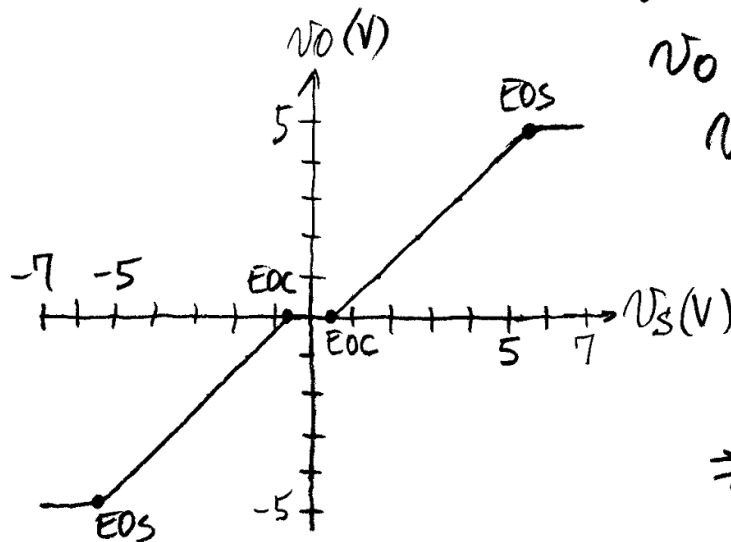

(b)  $V_O = 2.5V \Rightarrow V_I = \pm \left( 2.5 + 0.7 + 10 \frac{2.5/1}{100} \right) = \pm 3.45V.$

2.39

(a)

A	B	QA	QB	Y
L	L	CO	CO	H
L	H	CO	Sat	L
H	L	Sat	CO	L
H	H	Sat	Sat	L

(b)  $\beta_{F(\min)} > \left( \frac{5-0.1}{1} \right) / \left( \frac{5-0.8}{10} \right) \approx 12$



2.40


(a)

A	B	Q <sub>A</sub>	Q <sub>B</sub>	Y
L	L	CO	CO	H
L	H	CO	CO	H
H	L	CO	CO	H
H	H	Sat	Sat	L

$$(b) \beta_{FA} \geq \left[ \frac{5 - 2(0.1)}{1} \right] / \left[ \frac{5 - (0.8 + 0.1)}{10} \right] = 11.7$$


$$\beta_{FB} \geq \left[ \frac{5 - 2(0.1)}{1} + \frac{5 - (0.8 + 0.1)}{10} \right] / \left[ \frac{5 - 0.8}{10} \right] = 11.$$

2.41

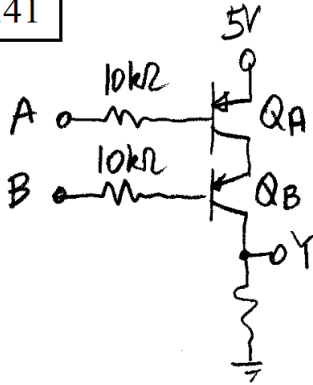

A	B	Q <sub>A</sub>	Q <sub>B</sub>	Y
L	L	Sat	Sat	H
L	H	CO	CO	L
H	L	CO	CO	L
H	H	CO	CO	L

2.42

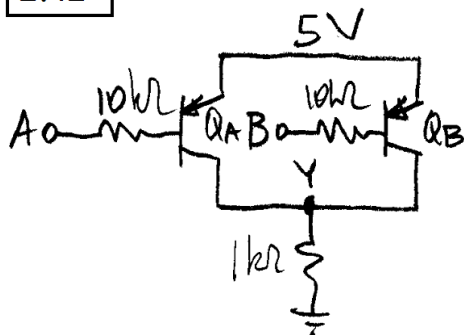

A	B	Q <sub>A</sub>	Q <sub>B</sub>	Y
L	L	Sat	Sat	H
L	H	Sat	CO	H
H	L	CO	Sat	H
H	H	CO	CO	L


2.43

$$(a) R_2 = (5 - 1.5 - 0.1) / 10 = 0.34 \text{ k}\Omega \text{ (use } 330 \Omega \text{)}.$$

$$I_D = (5 - 1.5 - 0.1) / 0.33 = 10.3 \text{ mA}$$

$$I_B(\text{min}) = 10.3 / 50 = 0.206 \text{ mA}.$$
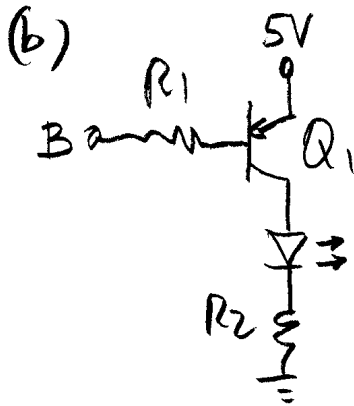
$$R_1 \leq (5 - 0.8) / 0.206 = 20 \text{ k}\Omega$$




$B = L = 0V \Rightarrow Q_1 = \text{sat} \Rightarrow \text{LED glows}.$

$B = H = 5V \Rightarrow Q_1 = \text{CO} \Rightarrow \text{LED is dark}.$

Assuming the same parameters as the BJT of part (a), use  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 330 \Omega$ .

2.44

(a) SSM:

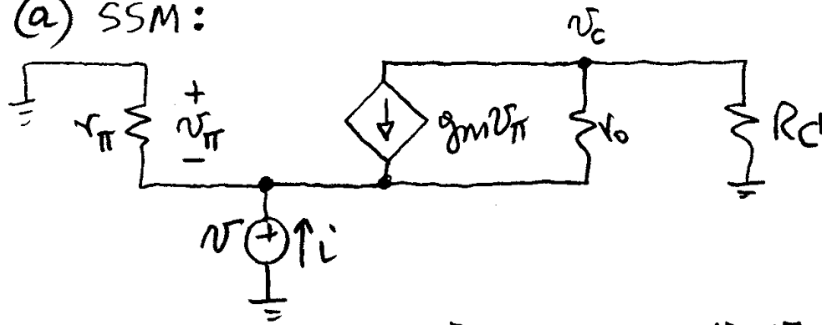

$$\text{KVL: } v_{\pi} = -v. \quad \text{KCL: } i + \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} + \frac{v_c - v}{r_o} = 0, \text{ or}$$

$$i - \frac{v}{r_{\pi}} - g_m v + \frac{v_c - v}{r_o} = 0. \quad \text{Supernode: } i = \frac{v}{r_{\pi}} + \frac{v_c}{R_C}, \text{ or}$$

$$v_c = R_C \left( i - \frac{v}{r_{\pi}} \right). \quad \text{Eliminating } v_c \text{ gives}$$

$$i \left( 1 + \frac{R_C}{r_o} \right) = v \left( \frac{1}{r_{\pi}} + g_m + \frac{1}{r_o} + \frac{R_C}{r_{\pi}} \frac{1}{r_o} \right) = v \left( \frac{1}{r_e} + \frac{1}{r_o} + \frac{R_C}{r_{\pi}} \frac{1}{r_o} \right)$$

$$R_e = \frac{v}{i} = r_e \frac{r_o + R_C}{r_o + r_e + (r_e/r_{\pi}) R_C}. \quad \text{Considering that } r_e \ll r_o$$

$$\text{and } \frac{r_e}{r_{\pi}} = \left( \frac{\beta_0}{\beta_0 + 1} \frac{1}{g_m} \right) / \left( \frac{\beta_0}{g_m} \right) = \frac{1}{\beta_0 + 1}, \text{ we get}$$

$$R_e \approx r_e \frac{r_o + R_C}{r_o + R_C / (\beta_0 + 1)} = r_e \frac{1 + R_C / r_o}{1 + R_C / [(\beta_0 + 1) r_o]}$$

$$(b) r_e = \frac{100}{101} \times \frac{26}{1} \approx 26 \Omega, \quad r_o = \frac{100}{1} = 100 \text{ k}\Omega$$


$$R_e \approx 26 \frac{1 + 10/100}{1 + 10/[101 \times 100]} \approx 28 \Omega.$$

$$(c) R_e \rightarrow r_e = 26 \Omega.$$

$$(d) R_e \rightarrow r_e \frac{R_C / r_o}{R_C / [(\beta_0 + 1) r_o]} = r_e (\beta_0 + 1) = r_{\pi} = 2.6 \text{ k}\Omega.$$

2.45

(a)

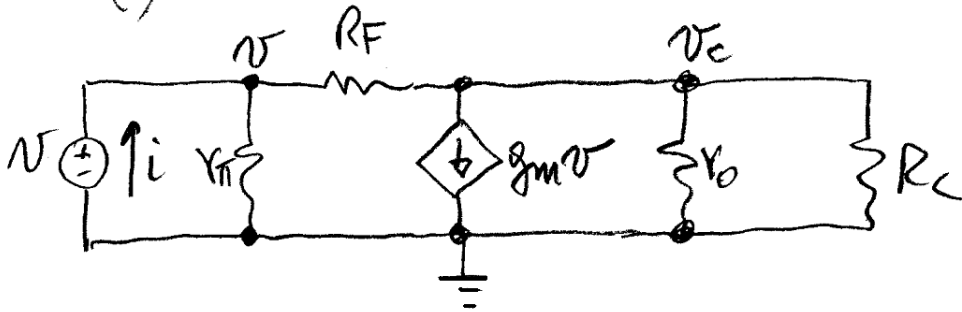

$$i = \frac{v}{r_{\pi}} + \frac{v - v_c}{R_F};$$

$$\frac{v - v_c}{R_F} = g_m v + \frac{v_c}{r_o \parallel R_C} \Rightarrow v \left( \frac{1}{R_F} - g_m \right) = \frac{v_c}{R_F \parallel R_C \parallel r_o} \Rightarrow$$

$$v_c = \frac{R_F \times (R_C \parallel r_o)}{R_F + (R_C \parallel r_o)} \frac{1 - g_m R_F}{R_F} v = \frac{R_C \parallel r_o}{R_F + (R_C \parallel r_o)} (1 - g_m R_F) v;$$

$$i = \frac{v}{r_{\pi}} + \frac{1}{R_F} \left[ 1 - \frac{R_C \parallel r_o}{R_F + (R_C \parallel r_o)} (1 - g_m R_F) \right] v$$

$$= v \left[ \frac{1}{r_{\pi}} + \frac{1}{R_F} \frac{R_F + (R_C \parallel r_o) - (R_C \parallel r_o) + g_m R_F (R_C \parallel r_o)}{R_F + (R_C \parallel r_o)} \right]$$

$$= v \left[ \frac{1}{r_{\pi}} + \frac{1 + g_m (R_C \parallel r_o)}{R_F + (R_C \parallel r_o)} \right]$$

$$R_i = \frac{v}{i} = \left( \frac{1}{r_{\pi}} + \frac{1 + g_m (R_C \parallel r_o)}{R_F + (R_C \parallel r_o)} \right)^{-1} = r_{\pi} \parallel \frac{R_F + (R_C \parallel r_o)}{1 + g_m (R_C \parallel r_o)}$$

(b)  $r_{\pi} = 100 (26/1) = 2.6 \text{ k}\Omega$ ,  $r_o = 100/1 = 100 \text{ k}\Omega$ ,  $g_m = 1/(26 \Omega)$


$$R_i = 2.6 \parallel \frac{10 + (1/100)}{1 + (1/100) 10^3/26} = 2.6 \parallel 0.281 = 254 \Omega.$$

(c)  $R_F \rightarrow 0$  and  $R_C \rightarrow \infty \Rightarrow$  BJT is diode-connected, and  $R_i = r_{\pi} \parallel \left[ \frac{r_o}{1 + g_m r_o} \right] \rightarrow r_{\pi} \parallel \frac{1}{g_m} = v_e \cong 26 \Omega.$

(d)  $R_F \rightarrow \infty \Rightarrow R_i \rightarrow r_{\pi} \parallel \infty = r_{\pi}.$

2.46

(a) SSM:

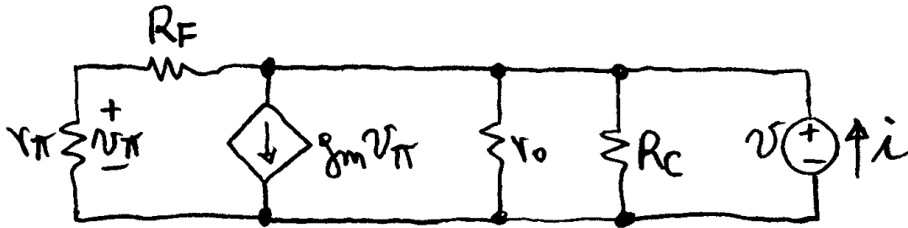

$$\text{KCL: } i = \frac{v}{r_o \parallel R_C} + g_m v_\pi + \frac{v}{R_F + r_\pi} \cdot \text{V.D.}; \quad \text{V.D.: } v_\pi = \frac{r_\pi}{R_F + r_\pi} v.$$

$$\therefore g_m v_\pi = \frac{g_m r_\pi}{R_F + r_\pi} v = \frac{g_m \beta_0 / g_m}{R_F + r_\pi} v = \frac{\beta_0}{R_F + r_\pi} v. \quad \text{Thus,}$$

$$i = \frac{v}{r_o \parallel R_C} + \frac{\beta_0 + 1}{R_F + r_\pi} v; \quad R_0 = \frac{v}{i} = (r_o \parallel R_C) \parallel \frac{R_F + r_\pi}{\beta_0 + 1}. \quad \text{But,}$$


$$\frac{r_\pi}{\beta_0 + 1} = \frac{\beta_0}{\beta_0 + 1} \frac{1}{g_m} = r_e. \quad \text{So, } R_0 = r_o \parallel R_C \parallel \left( r_e + \frac{R_F}{\beta_0 + 1} \right).$$

$$(b) \quad r_e \cong 26 \Omega, \quad r_o = 100 \text{ k}\Omega, \quad R_0 = 10^5 \parallel 10^3 \parallel \left( 26 + \frac{10^4}{101} \right) \cong 111 \Omega.$$

$$(c) \quad (R_F \rightarrow 0, R_C \rightarrow \infty) \Rightarrow R_0 = r_o \parallel r_e \cong r_e \quad (\text{BJT} = \text{diode}).$$

(d) With the base at ac ground,  $v_\pi \rightarrow 0$  and  $g_m v_\pi \rightarrow 0$ .  
By inspection,  $R_0 = R_F \parallel r_o \parallel R_C$ .

2.47

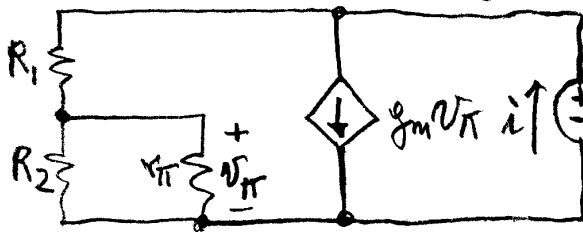Apply test voltage  $v$ :

$$v_\pi = \frac{R_2 \parallel r_\pi}{R_1 + (R_2 \parallel r_\pi)} v$$

$$i = g_m v_\pi + \frac{v}{R_1 + (R_2 \parallel r_\pi)}$$

$$= \frac{g_m (R_2 \parallel r_\pi) + 1}{R_1 + (R_2 \parallel r_\pi)} v$$


$$R = \frac{v}{i} = \frac{R_1 + (R_2 \parallel r_\pi)}{1 + g_m (R_2 \parallel r_\pi)} = \frac{[12 + (15/10)] 10^3}{1 + (15/10) 10^3 / 50} = \frac{18000}{121} = 149 \Omega.$$

2.48

(a) By inspection,  $R_i = (R_1 + R_2) \parallel R_b$ . Using Eq. (53a),

$$R_i = (R_1 + R_2) \parallel [\gamma_{\pi} + (\beta_0 + 1) R_E]$$

(b)

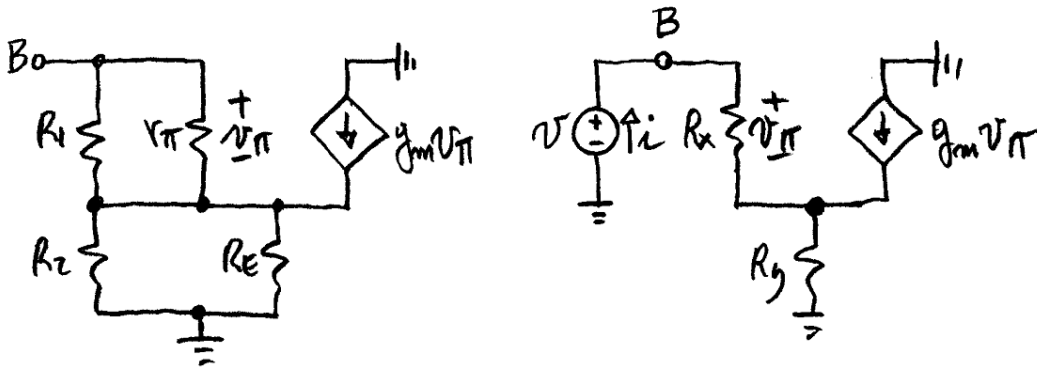

With the switch closed, we get the circuit at the left. This, in turn, is equivalent to that at the right, provided we let  $R_x = R_1 \parallel \gamma_{\pi}$  and  $R_y = R_2 \parallel R_E$ . Applying a test voltage, as shown, we get, by KCL & KVL,

$$\frac{v_{\pi}}{R_x} + g_m v_{\pi} = \frac{v - v_{\pi}}{R_y}$$

But,  $v_{\pi} = R_x i$ . Eliminating  $v_{\pi}$ , collecting, and taking the ratio  $R_i = \frac{v}{i}$  gives

$$R_i = R_x + (1 + g_m R_x) R_y$$

(c)  $g_m = 1/(26\Omega)$ ,  $\gamma_{\pi} = 2.6\text{ k}\Omega$ . For case (a) we get

$$R_i = (10 + 10) \parallel (2.6 + 101 \times 10) = 19.6\text{ k}\Omega (\cong R_1 + R_2)$$

For case (b) we get  $R_x = 10/2.6 = 2.06\text{ k}\Omega$ ,  $R_y = 10/10 = 5\text{ k}\Omega$ ;

$$R_i = 2.06 + \left(1 + \frac{5000}{26}\right) 5 = 969\text{ k}\Omega (\cong g_m R_x R_y)$$

This is much higher than (a)! The bootstrapping technique raises the input resistance dramatically!

2.49

(a)  $V_E = (2/3)9 = 6V$ ,  $V_C = (1/3)9 = 3V$ ;  $R_E = R_C = 3/2 = 1.5k\Omega$ . Let  $\beta_F = 100$ . Then,  $I_B = (2mA)/100 = 20\mu A$ . Impose  $I_{R_1} = 10I_B = 0.2mA$ . Assuming  $V_{EB(on)} = 0.7V$ , we have  $V_B = 9 - (6 - 0.7) = 5.3V$ ;  $R_1 = (9 - 5.3)/0.2 = 18.5k\Omega$  (use  $18k\Omega$ ) and  $R_2 = 5.3/(0.2 + 0.02) = 24k\Omega$ .

(b)  $R_{BB} = 18/24 = 10.3k\Omega$ ,  $V_{BB} = 9 \times 24/(18 + 24) = 5.14V$

$$I_C \cong \frac{V_{EE} - V_{BB} - V_{EB(on)}}{R_{BB}/\beta_F + R_E}$$

$$I_C(\text{nominal}) = \frac{9 - 5.14 - 0.7}{10.3/100 + 1.5} = 1.97mA$$


$$I_C(\text{max}) = \frac{9 - 5.14(0.95) - 0.7}{(10.3 \times 0.95)/150 + 1.5(0.95)} \cong 2.3mA$$

$$I_C(\text{min}) = \frac{9 - 5.14(1.05) - 0.7}{(10.3 \times 1.05)/75 + 1.5(1.05)} \cong 1.7mA$$

( $\pm 0.3/2 = \pm 15\%$  variation in  $I_C$ ).

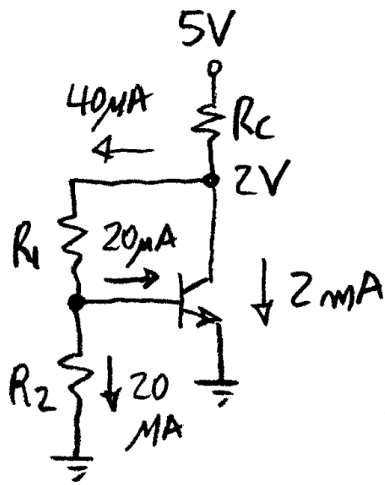2.50

$$(a) I_B = 2 \text{ mA} / 100 = 20 \mu\text{A} = I_{R_2}$$



$$R_2 = 0.7 / 0.02 = 35 \text{ k}\Omega \text{ (use } 36 \text{ k}\Omega)$$

$$R_1 = \frac{2 - 0.7}{0.02} = 32.5 \text{ k}\Omega \text{ (use } 33 \text{ k}\Omega)$$

$$R_C = \frac{5 - 2}{2 + 0.04} = 1.47 \text{ k}\Omega \text{ (use } 1.5 \text{ k}\Omega)$$

$$(b) V_C = V_{BE} + R_1 \left( I_B + \frac{V_{BE}}{R_2} \right);$$

$$V_C = 0.7 + 33 \left( I_B + \frac{0.7}{36} \right) = 1.34 \text{ V} + (33 \text{ k}\Omega) I_B$$

$$I_C = \frac{5 - V_C}{R_C} - \left( I_B + \frac{0.7}{36} \right) = \frac{5 - 1.34 - 33 I_B}{1.5} - I_B - \frac{0.7}{36}$$

$$= 2.42 - 23 I_B = 2.42 - 23 I_C / \beta_F. \text{ Solving for } I_C,$$


$$I_C = \frac{2.42}{1 + 23/\beta_F}. \text{ For } \beta_F = 50, 100, 200, \text{ we get } I_C \approx 1.66 \text{ mA},$$

$$1.97 \text{ mA}, 2.17 \text{ mA}. \text{ Not bad! Moreover, } V_{CE} = V_C =$$

$$1.34 + 33 I_C / \beta_F \approx 2.44 \text{ V}, 1.99 \text{ V}, 1.90 \text{ V}, \text{ all near the intended value of } 2 \text{ V}.$$



2.51

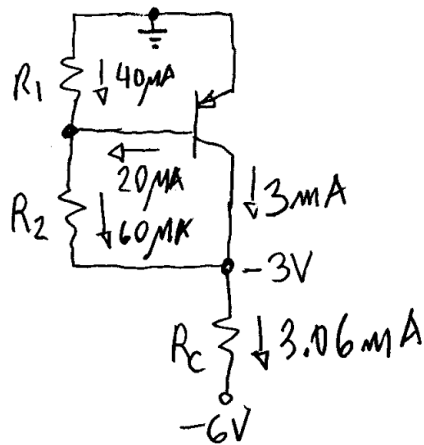

$$(a) I_B = 3/150 = 20 \mu\text{A}; I_{R_1} = 40 \mu\text{A}; R_1 = 0.7/0.04 =$$

$$17.5 \text{ k}\Omega \text{ (Use } 18 \text{ k}\Omega). I_{R_2} = I_{R_1} + I_B =$$

$$3 I_B = 60 \mu\text{A}; R_2 = [-0.7 - (-3)]/0.06$$

$$= 38.3 \text{ k}\Omega \text{ (use } 39 \text{ k}\Omega). I_{R_C} = I_C +$$

$$I_{R_2} = 3 + 0.06 = 3.06 \text{ mA}; R_C =$$

$$[-3 - (-6)]/3.06 = 0.98 \text{ k}\Omega \text{ (use } 1 \text{ k}\Omega).$$

$$(b) V_C = -0.7 - R_2 \left( I_B + \frac{0.7}{R_1} \right) = -0.7 - 39 \left( I_B + \frac{0.7}{18} \right) \Rightarrow$$

$$V_{EC} = 0 - V_C = 2.217 + 39 I_B. I_C = I_{R_C} - I_{R_2}, \text{ or}$$

$$I_C = \frac{6 - V_{EC}}{R_C} - \left( I_B + \frac{0.7}{R_1} \right) = \frac{6 - 2.217 - 39 I_B}{1} - I_B - \frac{0.7}{18}, \text{ or}$$

$$I_C = 3.74 - 40 I_B = 3.74 - \frac{40}{\beta_F} I_C \Rightarrow I_C = 3.74 / \left( 1 + \frac{40}{\beta_F} \right).$$

$$I_C(\text{min}) = \frac{3.74}{1 + 40/75} = 2.44 \text{ mA}; I_C(\text{nom}) = \frac{3.74}{1 + 40/150} = 2.96$$

$$\text{mA}; I_C(\text{max}) = \frac{3.74}{1 + 40/250} = 3.23 \text{ mA. Correspondingly,}$$

$$V_{EC}(\text{max}) = 2.217 + 39(2.44/75) = 3.49 \text{ V};$$

$$V_{EC}(\text{nom}) = 2.99 \text{ V}, V_{EC}(\text{min}) = 2.72 \text{ V.}$$

2.52

$$(a) I_{C2} = I_{C1} = (5 - 0.7) / 4.3 = 1.0 \text{ mA}$$

$$(b) I_{C2} = I_{C1} \exp(\Delta V_{BE} / V_T) = 1.0 \exp(2/26) = 1.080 \text{ mA}$$

$$(c) I_{C2} = I_{C1} \exp(2 \times 5 / 26) = 1.469 \text{ mA}$$

$$(d) V_{BE1} = 700 - 2 \times 10 = 680 \text{ mV};$$

$$I_{C1} = (5 - 0.68) / 4.3 = (4.32 / 4.3) \text{ mA};$$

$$I_{C2} = \frac{4.32}{4.3} \exp(-2 \times 10 / 26) = 0.466 \text{ mA},$$

(e) Now we must have  $T(Q_1) > T(Q_2)$ , such that

$$T(Q_1) - T(Q_2) = \frac{26}{2} \ln \frac{1.0}{0.75} = 3.74 \text{ }^\circ\text{C}.$$

2.53

$$I_{C1} = (5 - 0.7) / 4.3 = 1.0 \text{ mA}$$

(a)  $I_{C2} = 0.4 \text{ mA} = (1 \text{ mA} / 10) \times 2 \times 2$ . By the rule of thumb,

$$V_{BE2} = 700 - 60 + 18 + 18 = 700 - 24 \text{ mV} \Rightarrow \Delta V_R = 24 \text{ mV};$$

$$R = \Delta V_R / I_R = 24 / 0.4 = 60 \text{ } \Omega$$

$$(b) \Delta V_R = 60 + 18 = 78 \text{ mV}; R = 78 / 0.05 = 1560 \text{ } \Omega.$$

$$(c) \Delta V_R = (26 \text{ mV}) \ln(1000 / 123) = 54.5 \text{ mV}; R = 54.5 / 0.123 = 443 \text{ } \Omega.$$

2.54

$$(a) V_{BE1} = (26 \text{ mV}) \ln \frac{(6 - 0.7)/10^4}{2 \times 10^{-15}} \cong 684 \text{ mV}$$

$$V_{BE2} = 0.026 \ln \frac{0.684 - V_{BE2}}{10^3 \times 2 \times 10^{-15}}; \text{ start out with } V_{BE2} = 0.6 \text{ V.}$$

$$V_{BE2} = 0.026 \ln \frac{0.684 - 0.6}{2 \times 10^{-12}} = 0.636 \text{ V}$$

$$V_{BE2} = 0.026 \ln \frac{0.684 - 0.636}{2 \times 10^{-12}} = 0.620 \text{ V}$$

Iterate further, and end with  $V_{BE2} = 626 \text{ mV}$ .

$$I_{C2} = (0.684 - 0.626)/10^3 \cong 58 \mu\text{A}.$$

$$(c) \text{ With } V_{CC} = 6 \text{ V, } I_{C1} = (6 - 0.684)/10 = 0.5316;$$


$$(1/2)I_{C1} = 0.5316/2 = 0.2658; \text{ Rule of Thumb:}$$

$$V_{BE1} = 684 - 18 = 0.666 \text{ V; } V_{CC} = 0.666 + 10 \times 0.2658 = 3.324 \text{ V. Reiterate as before, and find}$$

$$V_{BE2} = 0.026 \ln \frac{0.666 - V_{BE2}}{2 \times 10^{-12}} \Rightarrow V_{BE2} = 620 \text{ mV} \Rightarrow$$

$I_{C2} = (0.666 - 0.620)/10^3 = 46 \mu\text{A}$ . While  $I_{C1}$  has dropped to  $\frac{1}{2}$  its initial value,  $I_{C2}$  has dropped from  $58 \mu\text{A}$  to  $46 \mu\text{A}$ . Not  $\frac{1}{2}$ , as  $I_{C2}$  is not linearly proportional to  $I_{C1}$ .

2.55

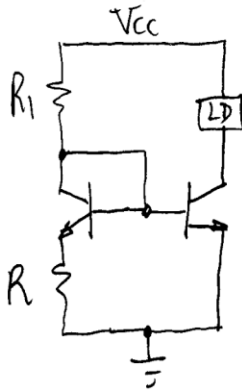

$$(a) I_S = 2 \mu A \Rightarrow V_{BE} = 700 \text{ mV} @ I_C = 1 \text{ mA.}$$

$$I_{C1} = 0.5 \text{ mA} \Rightarrow V_{BE1} = 700 - 18 = 682 \text{ mV}$$

$$I_{C2} = 2 \text{ mA} \Rightarrow V_{BE2} = 700 + 18 = 718 \text{ mV}$$

$$\therefore R = (718 - 682) / 0.5 = 72 \Omega.$$

$$R_1 = (5 - 0.718) / 0.5 = 8.564 \text{ k}\Omega.$$

(b)  $I_{C1} = 1 \text{ mA} \Rightarrow V_{BE1} = 700 \text{ mV}$ ;  $V_R = 72 \times 1 = 72 \text{ mV}$ .  
 $V_{BE2} = 700 + 72 = 772 \text{ mV} = (700 + 4 \times 18) \text{ mV} \Rightarrow I_{C2} = 1 \times 2^4 = 16 \text{ mA}$ .  
 Thus, while  $I_{C1}$  has doubled once,  $I_{C2}$  has doubled four times!

2.56

$$(a) R_1 = (12 - 5.6) / 3 = 2.1 \text{ k}\Omega \text{ (use } 2.0 \text{ k}\Omega).$$

$$R_2 = (5.6 - 0.7) / 2 = 2.45 \text{ k}\Omega \text{ (use } 2.4 \text{ k}\Omega).$$

$$g_m = 2/26 = 1/(13 \Omega); r_{\pi} = 100 \times 13 = 1.3 \text{ k}\Omega; r_o = \frac{75}{2} \approx 37 \text{ k}\Omega.$$

$$R_c = r_o [1 + g_m (R_2 / r_{\pi})] = 37 [1 + (2400 / 1300) / 13] \approx 2.5 \text{ M}\Omega.$$


(b) An increase in  $V_L$  decreases  $V_{CE}$  and thus decreases  $I_0$ . The change is such that  $\Delta I_0 / \Delta V_L = -\frac{1}{R_c} \approx -\frac{1}{2.5 \times 10^6} = -0.4 \mu\text{A/V}$ . An increase in  $|\Delta V_{EE}|$  increases both  $V_Z$  and  $V_{CE}$ , according to

$$\Delta V_Z = \frac{r_z}{R_1 + r_z} |\Delta V_{EE}| = \frac{15}{2000 + 15} |\Delta V_{EE}| \approx \frac{|\Delta V_{EE}|}{134}, \Delta V_{CE} = |\Delta V_{EE}|.$$

$$\Delta I_0 = \frac{\Delta V_Z}{R_2} + \frac{\Delta V_{CE}}{R_c} = \frac{|\Delta V_{EE}|}{134 \times 2.4 \times 10^3} + \frac{|\Delta V_{EE}|}{2.5 \times 10^6} = (3.1 + 0.4) 10^{-6} |\Delta V_{EE}|.$$

$$\therefore \frac{\Delta I_0}{|\Delta V_{EE}|} = 3.5 \mu\text{A/V}.$$

2.57

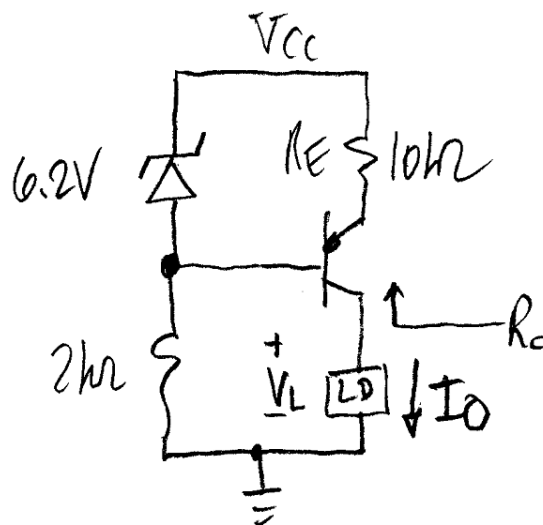

An increase in  $V_L$  decreases  $V_{EC}$  and thus decreases  $I_O$ .

$$\frac{\Delta I_O}{\Delta V_L} = -\frac{1}{R_c} = -\frac{1}{V_o [1 + g_m (R_E // r_{\pi})]}$$

$$V_o = \frac{100}{0.55}; \quad g_m = \frac{0.55}{26}; \quad r_{\pi} = 100 \frac{26}{0.55}; \quad R_c = 12.5 \text{ M}\Omega$$

$$\frac{\Delta I_O}{\Delta V_L} = -\frac{1}{12.5 \times 10^6 \text{ A}} \approx -80 \text{ mA/V.}$$

An increase in  $V_{CC}$  increases  $V_Z$  as well as  $V_{EC}$

$$\Delta V_Z = \frac{20}{2000+20} \Delta V_{CC} = \frac{\Delta V_{CC}}{101} \Rightarrow \Delta I_{O1} = \frac{\Delta V_Z}{10 \text{ k}\Omega} = \frac{\Delta V_{CC}}{101 \times 10^4}$$

$$\approx \frac{\Delta V_{CC}}{1 \text{ M}\Omega}; \quad \Delta I_{O2} \approx \frac{\Delta V_{CC}}{12.5 \text{ M}\Omega};$$

$$\Delta I_O = \Delta I_{O1} + \Delta I_{O2} = \Delta V_{CC} \left( \frac{1}{1 \text{ M}\Omega} + \frac{1}{12.5 \text{ M}\Omega} \right) = \frac{\Delta V_{CC}}{930 \text{ k}\Omega}$$

$$\frac{\Delta I_O}{\Delta V_{CC}} = \frac{1}{930 \text{ k}\Omega} \approx 1.1 \mu\text{A/V.}$$

2.58

$$(a) I_B = \frac{10 - 0.7}{33 + 151 \times 8.2} = 7.32 \mu\text{A}; I_C = 1.097 \text{ mA};$$

$$V_B = 33 \times 7.32 \times 10^{-3} = 0.241 \text{ V}$$

$$V_E = V_B + V_{EB(\text{on})} = 0.241 + 0.7 = 0.941 \text{ V}$$

$$V_C = -10 + 4.7 \times 1.097 = -4.842 \text{ V}.$$

$$\beta_m = \frac{1.097}{26} = \frac{1}{23.7 \Omega}; r_{\pi} = 3.55 \text{ k}\Omega; r_o = 45.5 \text{ k}\Omega.$$

$$R_i = 33 // 3.55 = 3.2 \text{ k}\Omega; R_o = 4.7 // 45.5 = 4.26 \text{ k}\Omega;$$

$$\frac{v_o}{v_{\text{sig}}} = \frac{3.2}{0.3 + 3.2} \left( -\frac{4260}{23.7} \right) \frac{12}{4.26 + 12} = -121 \text{ V/V}.$$

$$(b) v_B = V_B + v_b = 0.241 \text{ V} + \frac{3.2}{0.3 + 3.2} (5 \text{ mV}) \cos \omega t$$

$$= 0.241 \text{ V} + (4.57 \text{ mV}) \cos \omega t;$$


$$v_C = V_C + v_c = -4.842 \text{ V} - 121 (5 \text{ mV}) \cos \omega t;$$

$$= -4.842 \text{ V} + (0.605 \text{ V}) \cos (\omega t - 180^\circ);$$

$$v_o = 0 + (0.605 \text{ V}) \cos (\omega t - 180^\circ);$$

$$v_E = 0.941 \text{ V} + 0.$$

2.59

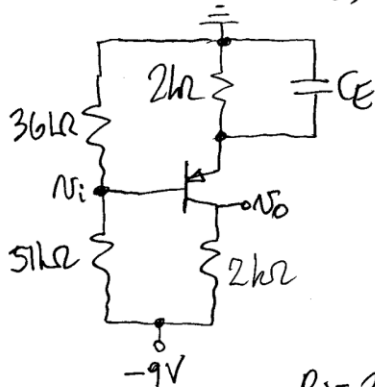

$$(a) V_{BB} = \frac{36}{36+51}(-9) = -3.72 \text{ V}$$

$$R_B = 36 // 51 = 21 \text{ k}\Omega$$

$$I_C = 150 \frac{3.72 - 0.7}{21 + 151 \times 2} = 1.4 \text{ mA}$$

$$g_m = \frac{1}{18.5 \Omega}, r_{\pi} = 2.78 \text{ k}\Omega, r_o = 43 \text{ k}\Omega$$

$$R_i = 36 // 51 // 2.78 \approx 2.5 \text{ k}\Omega, R_o = 2 // 43 = 2.46 \text{ k}\Omega,$$

$$v_o/v_i = -g_m R_o = -2.46 / 0.0185 = -133 \text{ V/V.}$$

$$(b) R_{eq} = r_e + R_{BB} / (\beta_0 + 1) = 18.5 + 21,000 / 151 = 160 \Omega.$$

$$C_E \gg 1 / (2\pi \times 160 \times 10^3) \approx 1 \mu\text{F}. \text{ Use } C_E = 10 \mu\text{F}.$$

2.60


$$[V, \text{mA}, \text{k}\Omega]. \text{ KVL: } 10 = 3.9 I_E + 68 I_E / 121 + 0.7 \Rightarrow$$

$$I_E = 2.08 \text{ mA} \Rightarrow I_C = 2.07 \text{ mA} \Rightarrow g_m = 1 / (12.6 \Omega), r_{\pi} =$$

$$1.5 \text{ k}\Omega, r_o \approx 48 \text{ k}\Omega, R_c // r_o = 3.9 // 48 = 3.6 \text{ k}\Omega$$

$$R_i = r_{\pi} // \frac{R_F + (R_c // r_o)}{1 + g_m (R_c // r_o)} = 1.5 // \frac{68 + 3.6}{1 + 3600 / 12.6} \approx 214 \Omega$$
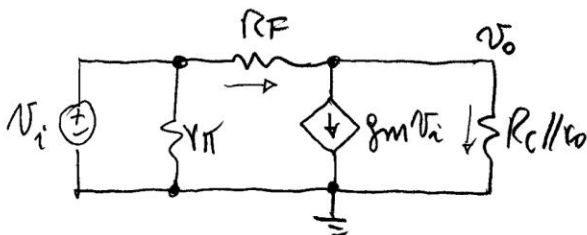
$$R_o \approx R_c // r_o // \left[ \frac{1}{g_m} + \frac{R_F}{\beta_0 + 1} \right] = 3600 // \left[ 12.6 + \frac{68,000}{121} \right] = 495 \Omega$$



KCL:

$$\frac{V_i - V_o}{R_F} = g_m V_i + \frac{V_o}{R_c // r_o}$$


$$\Rightarrow \left( \frac{1}{R_F} - g_m \right) V_i = V_o \left( \frac{1}{R_F} + \frac{1}{R_c // r_o} \right) = \frac{V_o}{R_F // R_c // r_o}$$

$$\frac{V_o}{V_i} = - \left( g_m - \frac{1}{R_F} \right) (R_F // R_c // r_o) = - \left( \frac{1}{12.6} - \frac{1}{68,000} \right) (6800 // 3600) = -271 \text{ V/V.}$$

2.61

(a)  $I_E = I_{BIAS} = 1 \text{ mA}$ ;  $I_C = \alpha_F I_E = 0.99 \text{ mA}$ ;  
 $I_B = I_E / (\beta_F + 1) = (1/101) \text{ mA}$ ;  $V_C = V_{BE} + R_F I_B = 0.7 + 100/101$   
 $\cong 1.7 \text{ V}$ .  $r_o = 100/0.99 = 101 \text{ k}\Omega$ ;  $g_m = 0.99/26 \cong 1/(26.3 \Omega)$ .

SSM:

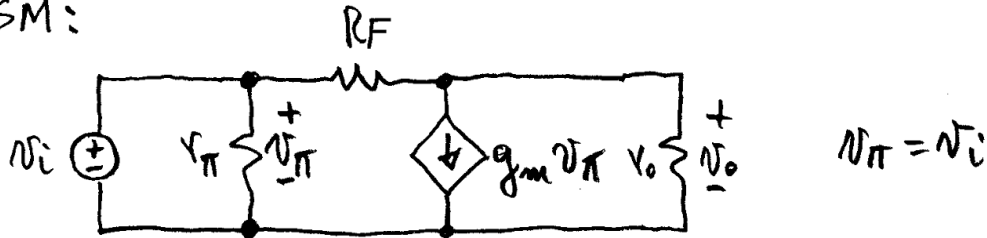

KCL:  $\frac{v_i - v_o}{R_B} = g_m v_i + \frac{v_o}{r_o}$ ;  $v_i \left( \frac{1}{R_B} - g_m \right) = \frac{v_o}{R_F} + \frac{v_o}{r_o} = \frac{v_o}{R_F // r_o}$

$$\frac{v_o}{v_i} = -g_m (R_F // r_o) \left( 1 - \frac{1}{g_m R_F} \right) = -\frac{0.99}{26} (100 // 101) 10^3 \left( 1 - \frac{1}{10^5 / 26.3} \right)$$

$$= -1913 \text{ V/V.}$$


(b)  $g_m$  doubles to  $2 \times 0.99/26$ , and  $r_o$  halves to  $50.5 \text{ k}\Omega$ .

From (a), it is apparent that  $v_o/v_i \cong -g_m (R_F // r_o)$ , so  
 $\frac{v_o}{v_i} = -\frac{1.98}{26} (100 // 50.5) 10^3 = -2555 \text{ V/V}$ . Because of the

presence of  $R_F$ , which remains unchanged, the doubling of  $g_m$  prevails over the halving of  $r_o$ , so the gain magnitude increases.



2.62

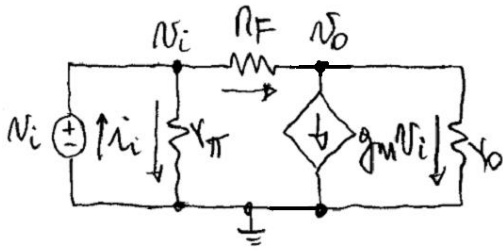(a)  $I_C = 1\text{mA} \Rightarrow g_m = 1/(26\Omega)$ ,  $r_{\pi} = 2.6\text{k}\Omega$ ,  $r_o = 100\text{k}\Omega$ .

$$\text{KCL: } i_i = \frac{v_i}{r_{\pi}} + \frac{v_i - v_o}{R_F} = \frac{v_i}{r_{\pi} // R_F} - \frac{v_o}{R_F}$$

$$\text{KCL: } \frac{v_i - v_o}{R_F} = g_m v_i + \frac{v_o}{r_o} \Rightarrow$$

$$\frac{1 - g_m R_F}{R_F} v_i = \frac{v_o}{R_F // r_o} \Rightarrow$$

$$v_o = \frac{1 - g_m R_F}{R_F} \frac{R_F // r_o}{R_F // r_o} v_i = \frac{1 - g_m R_F}{1 + R_F / r_o} v_i \Rightarrow i_i = \frac{v_i}{r_{\pi} // R_F} - \frac{1 - g_m R_F}{R_F (1 + R_F / r_o)} v_i$$


$$R_i = \frac{v_i}{i_i} = r_{\pi} // R_F // \frac{R_F (1 + R_F / r_o)}{g_m R_F - 1} = 2.6 // 100 // \frac{100 (1 + 100 / 100)}{100 / 0.026 - 1} \approx 52 \Omega.$$

If  $R_L = 100\text{k}\Omega$ , replace  $r_o$  with  $r_o // R_L = 100 // 100 = 50\text{k}\Omega$ . Then,

$$R_i = 2.6 // 100 // \frac{100 (1 + 100 / 50)}{100 / 0.026 - 1} \approx 76 \Omega. R_i \text{ is dominated by}$$

the third term, roughly representing  $R_F$  divided by the gain  $|v_o/v_i|$  (Miller effect). Loading the amplifier reduces the gain and thus increases  $R_i$ .

(b)

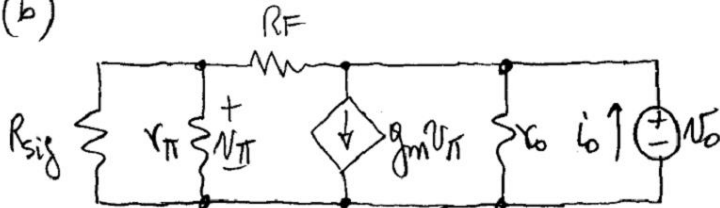


$$i_o = \frac{v_o}{r_o} + \frac{v_o}{R_F + (R_{sig} // r_{\pi})} + g_m \frac{R_{sig} // r_{\pi}}{R_F + (R_{sig} // r_{\pi})} v_o = v_o \left[ \frac{1}{r_o} + \frac{1 + g_m (R_{sig} // r_{\pi})}{R_F + (R_{sig} // r_{\pi})} \right]$$

$$R_o = \frac{v_o}{i_o} = r_o // \frac{R_F + (R_{sig} // r_{\pi})}{1 + g_m (R_{sig} // r_{\pi})}. R_o (R_{sig} = 0) = r_o // R_F = 50\text{k}\Omega.$$

$$R_o (R_{sig} = 1\text{k}\Omega) = 100 // \frac{100 + 1 // 2.6}{1 + (1 // 2.6) / 0.026} \approx 3.4\text{k}\Omega$$

With  $R_{sig} \neq 0$ ,  $v_{\pi} \neq 0$  and  $g_m v_{\pi} \neq 0$ , so  $i_o$  increases, reducing  $R_o$ . In the limit  $R_{sig} \rightarrow \infty$ , we get  $R_o \rightarrow 1\text{k}\Omega$ .

2.63

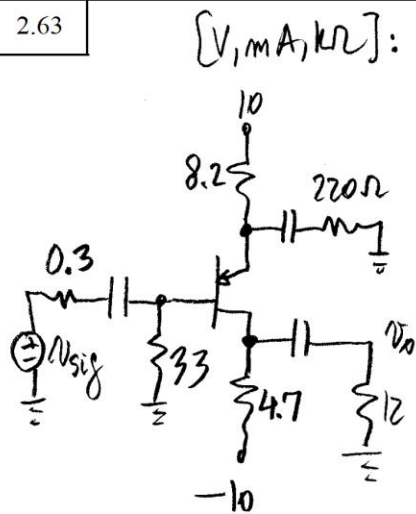

$[V, mA, k\Omega]$ : DC analysis:

$$I_B = \frac{10 - 0.7}{33 + 126 \times 8.2} = 8.72 \mu A$$

$$I_C = 125 \times 8.72 = 1.09 \text{ mA}$$

$$g_m = \frac{1.09}{26} = \frac{1}{23.8 \Omega}$$

$$r_{\pi} = 125 \times 23.8 = 2.98 \text{ k}\Omega$$

$$R_i = R_B // R_b = 33 // [2.98 + (125 + 1)(8.2 // 10.22)] = 15.9 \text{ k}\Omega$$

$$R_o \cong 8.2 \text{ k}\Omega$$

$$\frac{v_o}{v_{sig}} = \frac{15.9}{0.3 + 15.9} \left( - \frac{1/23.8}{1 + (1/23.8)(8200/120)} \right) \frac{12}{8.2 + 12}$$

$$= -17.2 \text{ V/V}$$

2.64

$$(a) I_C = 125 \frac{12 - 0.7}{100 + 126 \times 15} = 0.71 \text{ mA}; g_m = 0.71/26 \cong$$

$$1/(37 \Omega); r_{\pi} = 125 \times 37 \cong 4.6 \text{ k}\Omega.$$

$$R_i = (100 \text{ k}\Omega) // R_b = 100 // [4.6 + 126 (15 // 0.1)] = 14.6 \text{ k}\Omega; R_o = 10 \text{ k}\Omega.$$

$$\frac{v_o}{v_i} = - \frac{g_m}{1 + g_m (15 // 0.1) 10^3} R_o = - \frac{10,000/37}{1 + 99.3/37} = -74 \text{ V/V}.$$

$$(b) R_{eq} = 100 \Omega + 15 \text{ k}\Omega // R_e = 100 + [15,000 // (37 + \frac{10^5}{126})]$$

$$= 887 \Omega. C > 1 / (6.28 \times 887 \times 100) = 1.8 \mu\text{F}.$$

Use 20  $\mu\text{F}$ .

$$(c) \text{ Without } C, \text{ the gain drops to } \frac{v_o}{v_i} \cong - \frac{10 \text{ k}\Omega}{15 \text{ k}\Omega} = -0.67 \text{ V/V}.$$

2.65

$$(a) R_{BB} = 30 // 15 = 10 \text{ k}\Omega, V_{BB} = [15 / (30 + 15)] 9 = 3 \text{ V}.$$

$$I_C = 100 \frac{3 - 0.7}{10 + 101 \times 2.2} = 0.99 \text{ mA}; g_m = \frac{1}{26 \Omega}; r_{\pi} = 2.6 \text{ k}\Omega.$$

$$R_i = 10 // [2.6 + 101 \times 0.2] \cong 17 \text{ k}\Omega; R_o \cong 2.7 \text{ k}\Omega$$



$$\frac{V_o}{V_i} = - \frac{1/26}{1 + 200/26} 2700 = -11.9 \text{ V/V}$$

$$(b) R_{eq3} = 2,000 // [200 + 26 + \frac{10,000}{101}] \cong 280 \Omega$$

$$C_3 \gg 1 / (2\pi \times 10^3 \times 280) = 0.57 \mu\text{F}. \text{ Use } C_3 = 10 \mu\text{F}.$$

$$(c) \frac{V_o}{V_i} \cong - \frac{2.7}{2 + 0.2} = -1.2 \text{ V/V}, \text{ quite low!}$$

2.66

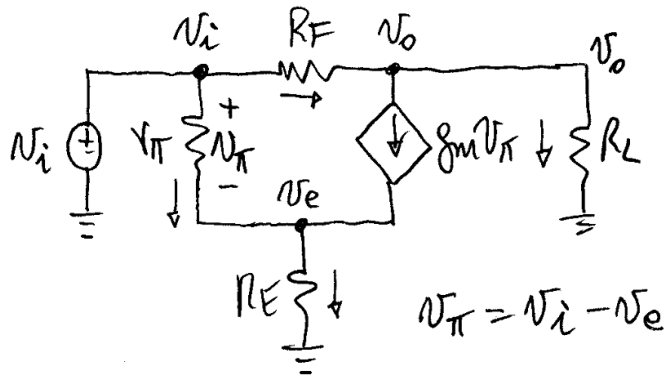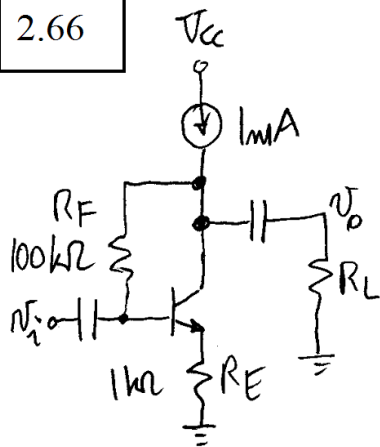

$$I_c = \alpha I_E = \frac{150}{151} I \approx 1 \text{ mA}, \quad g_m = \frac{1}{26.2 \Omega}, \quad r_\pi = 39.3 \text{ k}\Omega.$$

$$\text{kCL @ } v_e: \frac{v_i - v_e}{r_\pi} + g_m (v_i - v_e) = \frac{v_e}{R_E} \Rightarrow v_e = \frac{1}{1 + r_e/R_E} v_i$$

$$\text{kCL @ } v_o: \frac{v_i - v_o}{R_F} = g_m (v_i - v_e) + \frac{v_o}{R_L} \Rightarrow$$

$$v_i \left( \frac{1}{R_F} - g_m + \frac{g_m}{1 + r_e/R_E} \right) = v_o \left( \frac{1}{R_F} + \frac{1}{R_L} \right) = \frac{v_o}{R_F/R_L}$$

$$\frac{v_o}{v_i} = \frac{R_F R_L}{R_F + R_L} \frac{1}{R_F} \left[ 1 - g_m R_F \left( 1 - \frac{1}{1 + r_e/R_E} \right) \right] = \frac{R_L}{R_F + R_L} \left[ 1 - g_m R_F \frac{r_e}{R_E + r_e} \right]$$

But,  $g_m r_e \approx 1$ , so

$$\frac{v_o}{v_i} = \frac{1}{1 + R_F/R_L} \left( 1 - \frac{R_F}{R_E + r_e} \right) = \frac{1}{1 + 100/100} \left( 1 - \frac{100}{1 + 0.026} \right) \approx -48 \text{ V/V.}$$

For  $R_E \gg r_e$ , we can approximate

$$\frac{v_o}{v_i} \rightarrow \left( 1 - \frac{R_F}{R_E} \right) \frac{1}{1 + R_F/R_L} = -\frac{99}{2} \text{ V/V.}$$

2.67

$$(a) R_i = r_{\pi 1} + (\beta_{01} + 1)(R_E // r_{e2}) \cong r_{\pi 1} + (\beta_{01} + 1)r_{e2} = 2r_{\pi 1};$$

$$R_c = r_{o1} [1 + g_{m1}(r_{\pi 1} // R_E // r_{e2})] \cong r_{o1} [1 + g_{m1}r_{e2}] \cong 2r_{o1};$$

$$R_o = R_c // R_L \cong R_c; \quad \frac{v_o}{v_{sig}} = - \frac{g_{m1} R_o}{1 + g_{m1}(R_E // r_{e2})} \cong - \frac{g_{m1} R_o}{2}.$$

$$(b) I_{C1} \cong I_{E1} = \frac{1}{2} \frac{12 - 0.7}{7.5} \cong 0.75 \text{ mA}$$

$$g_m = \frac{0.75}{26} = \frac{1}{34.7 \Omega}, \quad r_{o1} = \frac{100}{0.75} = 133 \text{ k}\Omega; \quad r_{\pi 1} = 200 \times 34.7 = 6.9 \text{ k}\Omega$$

$$R_i \cong 2r_{\pi 1} = 13.8 \text{ k}\Omega; \quad R_c \cong 2 \times 133 = 267 \text{ k}\Omega; \quad R_o = R_c // R_L =$$

$$267 // 10 = 9.64 \text{ k}\Omega; \quad \frac{v_o}{v_{sig}} = - \frac{1}{2} \frac{9640}{34.7} \cong -140 \text{ V/V}.$$

2.68

$$\frac{v_o}{v_{sig}} = \frac{1}{1 + \frac{R_{sig} + r_{\pi}}{(\beta_0 + 1)(R_L / r_o)}} \approx \frac{1}{1 + \frac{R_{sig} + r_{\pi}}{(\beta_0 + 1)R_L}}$$

where we are assuming  $r_o \gg R_L$ .

$$0.853 = \frac{1}{1 + \frac{0 + r_{\pi}}{(\beta_0 + 1)300}} = \frac{1}{1 + r_e / 300} \Rightarrow r_e = 51.7 \Omega$$

$$\Rightarrow I_C \approx V_T / r_e = 26 / 51.7 \approx 0.5 \text{ mA.}$$

$$0.718 = \frac{1}{1 + \frac{R_{sig} + r_{\pi}}{(\beta_0 + 1)R_L}} = \frac{1}{1 + \frac{10^4}{(\beta_0 + 1)300} + \frac{r_e}{300}} = \frac{1}{1 + \frac{33.3}{\beta_0 + 1} + \frac{51.7}{300}}$$

$$\Rightarrow \beta_0 = 150 ; r_{\pi} = 151 \times 51.7 = 7.75 \text{ k}\Omega.$$

$$\frac{v_o}{v_{sig}} = \frac{1}{1 + \frac{20000 + 7755}{151 \times 1200}} = 0.867 \text{ V/V.}$$

2.69


$$V_{BB} = \frac{68}{68+47}(-12) = -7.1V; R_{BB} = 68//47 = 27.8 \text{ k}\Omega.$$

$$I_C = 125 \frac{7.1 - 0.7}{27.8 + 126 \times 3} = 1.97 \text{ mA}; r_e \approx \frac{26}{1.97} = 13.2 \Omega; r_{\pi} =$$

$$125 \times 13.2 = 1.65 \text{ k}\Omega; r_o = 80/1.97 = 40.6 \text{ k}\Omega \approx 41 \text{ k}\Omega$$

$$R_i = R_{BB} // [\ r_{\pi} + (\beta_0 + 1)(R_E // R_L // r_o) ] = 27.8 // [ 1.65 + 126(3//2//41) ] = 23.4 \text{ k}\Omega$$
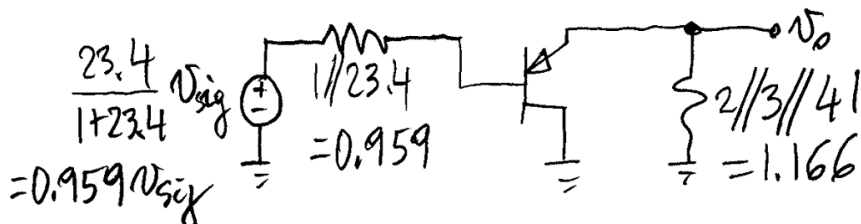
$$R_o = R_E // r_o // \left[ r_e + \frac{R_{sig} // R_{BB}}{\beta_0 + 1} \right] = 3//41 // \left[ 0.0132 + \frac{1//27.8}{126} \right] = 20.7 \Omega.$$



$$\frac{v_o}{v_{sig}} = 0.959 \frac{1}{1 + \frac{1.65 + 0.959}{126 \times 1.166}} = 0.942 \text{ V/V}.$$


2.70

$$(a) I_C = 100 \frac{6 - 0.7}{20 + 101 \times 3} = 1.64 \text{ mA}, r_e = 15.7 \Omega,$$

$$r_{\pi} \approx 1.6 \text{ k}\Omega. R_i = 20 \parallel (1.6 + 101 \times 3) \approx 19 \text{ k}\Omega$$

$$R_o = 3,000 \parallel [15.7 + (10,000 \parallel 20,000) / 101] \approx 80 \Omega.$$

Thévenize:

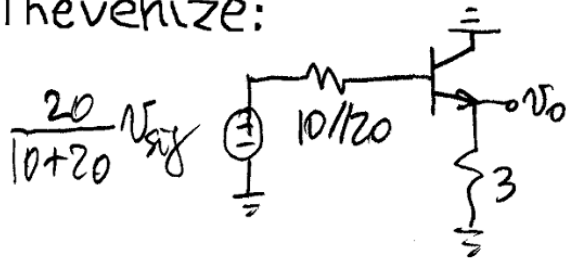

$$\frac{V_o}{\frac{2}{3} V_{sig}} = \frac{1}{1 + \frac{1.6 + (10 \parallel 20)}{101 \times 3}}$$

$$\frac{V_o}{V_{sig}} = 0.649 \text{ V/V}$$

(b) With  $C_2$  in place, the upper  $10\text{-k}\Omega$  resistance is placed in parallel with  $r_{\pi}$ , giving  $r_{\pi(eq)} = 10 \parallel 1.6 \approx 1.4 \text{ k}\Omega$ ; the lower  $10\text{-k}\Omega$  resistance is placed in parallel with  $R_E$ , giving  $R_{E(eq)} = 10 \parallel 3 = 2.3 \text{ k}\Omega$ .

We now have

$$R_i = r_{\pi(eq)} + (\beta_0 + 1) R_{E(eq)} = 1.4 + 101 \times 2.3 = 234 \text{ k}\Omega$$

$$R_o = R_{E(eq)} \parallel \left( r_e + \frac{R_{sig}}{\beta_0 + 1} \right) = 2,300 \parallel \left( 15.7 + \frac{10,000}{101} \right) = 110 \Omega$$

$$\frac{V_o}{V_{sig}} = \frac{1}{1 + \frac{r_{\pi(eq)} + R_{sig}}{(\beta_0 + 1) R_{E(eq)}}} = \frac{1}{1 + \frac{1.4 + 10}{101 \times 2.3}} = 0.953 \text{ V/V}$$

Bootstrapping increases  $R_i$  significantly, thus reducing input loading and making gain closer to unity.




$$2.71 \quad I_C = (5 - 0.7) / 4.3 = 4.3 \text{ mA}; r_e \cong 26 \Omega = 1/g_m;$$

$$r_o = 75/1 = 75 \text{ k}\Omega; r_{\pi} = 150 \times 26 = 3.9 \text{ k}\Omega$$

$$v_e = \frac{R // r_o}{r_e + (R // r_o)} v_i = \frac{4.3/75}{0.026 + (4.3/75)} (0.5) \cos \omega t$$
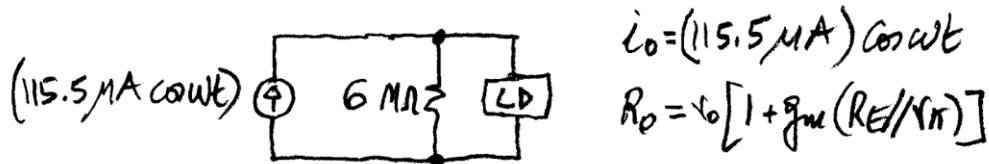
$$v_e = (496.8 \text{ mV}) \cos \omega t; i_o = \alpha_b i_e \cong i_e = v_e / R$$



$$R_o \cong 75 \text{ k}\Omega \left[ 1 + (4,300 // 3,900) / 26 \right] \cong 6 \text{ M}\Omega$$

$$2.72 \quad I_{C1} = I_{C2} \cong \frac{12 - 0.7}{10} = 1.13 \text{ mA};$$

$$r_{e1} = r_{e2} = 0.99 (26 / 1.13) = 22.8 \Omega;$$

$$r_{\pi 1} = r_{\pi 2} = 100 (26 / 1.13) = 2.3 \text{ k}\Omega$$

$$R_i = r_{\pi 1} + (\beta_{01} + 1) (R_{E1} // R_{B2}), \quad R_{B2} = r_{\pi 2} + (\beta_{02} + 1) (R_{E2} // R_L)$$

$$R_o = R_{E2} // R_{E2}, \quad R_{E2} = r_{e2} + \frac{R_{E1} // r_{e1}}{\beta_{01} + 1}$$

$$R_{B2} = 2.3 + 101 (10 // 20) = 676 \text{ k}\Omega$$


$$R_i = 2.3 + 101 (10 // 676) \cong 1 \text{ M}\Omega$$

$$R_{E2} = 22.8 + \frac{10^4 // 22.8}{101} \cong 23 \Omega; \quad R_o = 10^4 // 23 \cong 23 \Omega.$$

$$\frac{v_o}{v_i} = \frac{v_o}{v_{e1}} \times \frac{v_{e1}}{v_i} \cong \frac{R_L}{R_o + R_L} \times \frac{R_{E1}}{r_{e1} + R_{E1}} \cong \frac{29,000}{23 + 29,000} \times \frac{10,000}{23 + 10,000}$$

$$\cong 0.9965 \text{ V/V}.$$

2.73

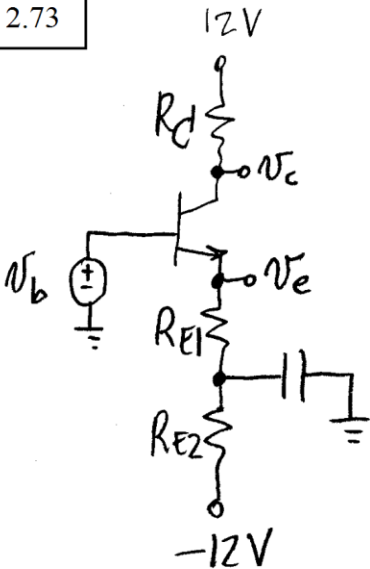

Impose  $I_C = 1 \text{ mA}$ ,  $V_{CE} = 6 \text{ V}$ .

$$\Rightarrow R_C = 6 \text{ k}\Omega \text{ (use } 6.2 \text{ k}\Omega, 5\%)$$

We know that  $v_e/v_b \approx 1 \text{ V/V}$ , so to achieve  $v_c/v_b \approx -1 \text{ V/V}$  we need  $R_{E1} = R_C = 6.2 \text{ k}\Omega$ .


Also, to ensure  $I_C = 1 \text{ mA}$ , we need  $R_{E1} + R_{E2} = (12 - 0.7)/1$ , or

$$R_{E2} = 11.3 - 6.2 = 5.1 \text{ k}\Omega, 5\%.$$

$$R_{eq} = R_{E2} // (R_{E1} + r_c) = 5.1 // (6.2 + 0.026) = 2.8 \text{ k}\Omega.$$

$$C > \frac{1}{2\pi \times 2.8 \times 10^3 \times 10^4} = 5.7 \text{ nF}. \text{ Use } C = 0.1 \mu\text{F}.$$

2.74

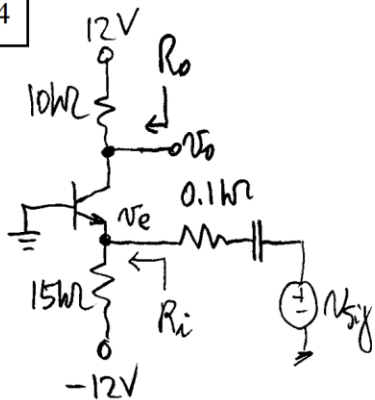

$$I_C \approx I_E = \frac{12 - 0.7}{15} = 0.753 \text{ mA}$$

$$r_e = \frac{26}{0.753} \approx 35 \Omega. R_o \approx 10 \text{ k}\Omega.$$

$$R_i = 35 // (15 \text{ k}\Omega) \approx 35 \Omega.$$

$$v_c = \frac{0.035}{0.035 + 0.1} v_{sig} = 0.26 v_{sig}.$$

$$v_o = g_m v_e R_o = \frac{1}{35} (0.26 v_{sig}) 10,000 = 74 v_{sig}. v_o/v_{sig} = 74 \text{ V/V}.$$

2.75

$$R_2 = \frac{10 - 0.7}{2} = 4.65 \text{ k}\Omega \text{ (use } 4.7 \text{ k}\Omega);$$

$$r_e \cong \frac{26}{2} = 13 \Omega, R_1 = \frac{10 - 5}{2} = 2.5 \text{ k}\Omega \text{ (use } 2.4 \text{ k}\Omega).$$

$$10 = \frac{R_1}{r_e + R_2 \parallel R_3} = \frac{2,400}{13 + (4,700 \parallel R_3)} \Rightarrow 4,700 \parallel R_3 = 227 \Omega \Rightarrow$$

$$\frac{1}{4,700} + \frac{1}{R_3} = \frac{1}{127} \Rightarrow R_3 = 238 \Omega \text{ (use } 240 \Omega).$$

2.76

$$(a) R_i = R_1 \parallel R_{e1}, R_{e1} = r_{e1} + \frac{r_{e2} \parallel R_2}{\beta_{o1} + 1} \cong r_{e1};$$

$$r_{e1} = \frac{V_T}{I_{C1}} \cong \frac{26}{10/10} = 26 \Omega; R_i = 10,000 \parallel 26 \cong 26 \Omega.$$

$$R_o \cong r_{o1} \left[ 1 + g_{m1} (R_{sig} \parallel R_1 \parallel r_{\pi 1}) \right] = \frac{80}{1} \left[ 1 + \frac{1 \parallel 10 \parallel (150 \times 0.026)}{0.026} \right]$$

$$\cong 2.35 \text{ M}\Omega. v_i = \frac{R_i}{R_{sig} + R_i} v_{sig} = \frac{26}{1000 + 26} v_{sig} = \frac{v_{sig}}{39.5}.$$

$$i_o = g_m v_i = \frac{1}{26} \frac{v_{sig}}{39.5} = \frac{v_{sig}}{1026 \Omega}.$$

$$(b) v_o = (R_L \parallel R_o) i_o \cong R_L i_o = \frac{5000}{1026} v_{sig} \Rightarrow \frac{v_o}{v_{sig}} = 4.87 \text{ V/V}.$$

(c) As long as  $R_{sig} \gg R_i$  and  $R_L \ll R_o$ , we have

$$v_o = R_L i_o = R_L v_i \cong R_L (v_{sig} / R_{sig}) \Rightarrow v_o / v_{sig} \cong R_L / R_{sig} = 5 \text{ V/V}.$$