 



Chapter 2: Introduction to Verilog®

- 2.1 (a) HDL – Hardware Description Language
FPGA – Field Programmable Logic Array
- (b) Verilog has statements that execute concurrently since it must model real hardware in which the components are all in operation at the same time.
- (c) A hardware description language allows a digital system to be designed and debugged at a higher level of abstraction than schematic capture with gates, flip-flops, and standard MSI building blocks. The details of the gates and flip-flops do not need to be handled during early phases of design. Designs are more portable when low-level library-specific details are not included in the model. HDLs allow the creation of such portable high-level behavioral models.
- 2.2 (a) Legal: A_123, _A123, c1_c2, and1; Illegal: 123A (starts with number), \$A123_ (starts with \$), and (reserved word).
- (b) None of the Verilog identifiers are equivalent since Verilog is case sensitive.

- 2.3 (a)



- (b)

 

- 2.4
- ```

module Gate(A, B, C, D, Z);
 input A, B, C, D;
 output Z;

 wire E, F, G, H, I;

 assign #5 H = A & B & C;
 assign #5 E = H | D;
 assign #5 G = ~(B | C);
 assign #5 F = ~(G & A);
 assign #2 I = ~F;
 assign #5 Z = E ^ I;
endmodule

```

- 2.5 (a)
- ```

module one_bit_sub(x, y, bin, diff, bout);
  input x, y, bin;
  output diff, bout;

  assign diff = x ^ y ^ bin;
  assign bout = (~x & bin) | (~x & y) | (bin & y);
endmodule

```
- (b)
- ```

module four_bit_sub(a, b, bin, d, bout);
 input[3:0] a, b;

```

```

 input bin;
 output[3:0] d;
 output bout;

 wire[3:0] bo;

 one_bit_sub s1(a[0], b[0], bin, d[0], bo[1]);
 one_bit_sub s2(a[1], b[1], bo[1], d[1], bo[2]);
 one_bit_sub s3(a[2], b[2], bo[2], d[2], bo[3]);
 one_bit_sub s4(a[3], b[3], bo[3], d[3], bout);
endmodule

```

2.6 (a) `module circuit(A, B, C, D, G);`

```

 input A, B, C, D;
 output G;

```

```

 wire E, F;

```

```

 assign E = A & B;
 assign F = E | C;
 assign G = D & F;

```

```

endmodule

```

(b) `module circuit(A, B, C, D, G);`

```

 input A, B, C, D;
 output reg G;

```

```

 reg E, F;

```

```

 initial begin

```

```

 E <= 0;
 F <= 0;
 G <= 0;

```

```

 end

```

```

 always @(*)

```

```

 begin

```

```

 E <= A & B;
 F <= E | C;
 G <= F & D;

```

```

 end

```

```

endmodule

```

2.7 (a) *A* changes to 1 at 25 ns, *B* changes to 1 at 25 ns, *C* change to 1 at 35 ns

(b) *A* changes to 1 at 25 ns, *B* changes to 1 at  $20 + \Delta$  ns, *C* does not change

2.8 (a) A falling-edge triggered D flip-flop with asynchronous active high clear and set

(b)  $Q = '0'$ , because  $Clr = 1$  has priority.

2.9 `module SR_Latch(S, R, Q, Qn);`

```

 input S, R;
 output reg Q;
 output Qn;

```

```

 initial begin

```

```

 Q <= 0;

```

```

 end

```

```

always @(S, R)
begin
 if(S == 1'b1)
 Q <= 1'b1;
 if(R == 1'b1)
 Q <= 1'b0;
end

assign Qn = ~Q;
endmodule

```

**2.10** module MNFF(M, N, CLK, CLRn, Q, Qn);

```

input M, N, CLK, CLRn;
output reg Q;
output Qn;

initial begin
 Q <= 0;
end

always @(CLK, CLRn)
begin
 if(CLRn == 1'b0)
 begin
 Q <= 0;
 end
 else if(CLK == 0)
 begin
 if(M == 0 && N == 0)
 Q <= ~Q;
 else if(M == 0 && N == 1)
 Q <= 1;
 else if(M == 1 && N == 0)
 Q <= 0;
 else if(M == 1 && N == 1)
 Q <= Q;
 end
 end

assign Qn = ~Q;
endmodule

```

**2.11** module DDFE(R, S, D, Clk, Q);

```

input R, S, D, Clk;
output reg Q;

initial begin
 Q <= 0;
end

always @(Clk, R, S)
begin
 if(R == 1'b0)
 Q <= 0;
 else if(S == 1'b0)
 Q <= 1;
 else
 Q <= D;
end
endmodule

```

**2.12 (a)** `module ITFF(I0, I1, T, R, Q, QN);`  
`input I0, I1, T, R;`  
`output reg Q;`  
`output QN;`  
  
`initial begin`  
`Q <= 0;`  
`end`  
  
`always @(T, R)`  
`begin`  
`if(R == 1'b1)`  
`#5 Q <= 0;`  
`else begin`  
`if((I0 == 1'b1 && T == 1'b1) || (I1 == 1'b1 && T == 1'b0))`  
`#8 Q <= QN;`  
`end`  
`end`  
  
`assign QN = ~Q;`  
`endmodule`

**(b)** `add list *`  
`add wave *`  
`force T 0 0, 1 100 -repeat 200`  
`force I1 0 0, 1 50, 0 450`  
`force I0 0 0, 1 450`  
`run 750 ns`

**2.13**

| ns | $\Delta$ | a | b | c | d | e |
|----|----------|---|---|---|---|---|
| 10 | +0       | 0 | 0 | 0 | 0 | 0 |
| 20 | +0       | 0 | 0 | 0 | 0 | 1 |
| 20 | +1       | 0 | 7 | 0 | 0 | 1 |
| 25 | +0       | 1 | 7 | 0 | 0 | 1 |
| 35 | +0       | 5 | 7 | 0 | 0 | 1 |

**2.14**

| ns | $\Delta$ | a | b | c | d | e |
|----|----------|---|---|---|---|---|
| 10 | +0       | 0 | 0 | 0 | 0 | 0 |
| 20 | +0       | 0 | 0 | 0 | 0 | 1 |
| 20 | +1       | 0 | 7 | 0 | 0 | 1 |
| 25 | +0       | 1 | 7 | 0 | 0 | 1 |
| 35 | +0       | 5 | 7 | 0 | 0 | 1 |

**2.15** i. 5'b10101  
 ii. 8'b11010101  
 iii. 3'b100

**2.16** i. 4'b0000  
 ii. 8'b00001010  
 iii. 7'b0000101

- 2.17**
- i. 8'h0D
  - ii. 8'hFD
  - iii. 8'h50
  - iv. 8'h50
  - v. 8'h0D
  - vi. 8'hFD
  - vii. 8'h50
  - viii. 8'h50

- 2.18 (a)**
- $A \gg 4 == 2'h0C$
  - $A \ggg 4 == 2'hFC$
  - $A \ll 4 == 8'h70$
  - $A \lll 4 == 8'h70$
- (b)**
- $A \gg 4 == 2'h0C$
  - $A \ggg 4 == 2'h0C$
  - $A \ll 4 == 8'h70$
  - $A \lll 4 == 8'h70$
- (c)**
- $A \gg 4 == 2'h0C$
  - $A \ggg 4 == 2'h0C$
  - $A \ll 4 == 8'h70$
  - $A \lll 4 == 8'h70$
- (d)**
- $A \gg 4 == 8'h0C$
  - $A \ggg 4 == 8'h0C$
  - $A \ll 4 == 8'h70$
  - $A \lll 4 == 8'h70$
- (e)**
- $A \gg 4 == 8'h0C$
  - $A \ggg 4 == 8'h0C$
  - $A \ll 4 == 8'h70$
  - $A \lll 4 == 8'h70$
- (f)**
- $A \gg 4 == 8'h0C$
  - $A \ggg 4 == 8'hFC$
  - $A \ll 4 == 8'h70$
  - $A \lll 4 == 8'h70$
- (g)**
- $A \gg 4 == 8'h0C$
  - $A \ggg 4 == 8'hFC$
  - $A \ll 4 == 8'h70$
  - $A \lll 4 == 8'h70$
- (h)**
- $A \gg 4 == 32'h0FFFFFFC$
  - $A \ggg 4 == 32'hFFFFFFFC$
  - $A \ll 4 == 32'hFFFFFFC70$
  - $A \lll 4 == 32'hFFFFFFC70$

- 2.19**
- i. 8'h0D
  - ii. 8'h0D
  - iii. 8'h50
  - iv. 8'h50
  - v. 8'h0D

- vi. 8'h0D
- vii. 8'h50
- viii. 8'h50

- 2.20**
- i. 8'h0D
  - ii. 8'h0D
  - iii. 8'h50
  - iv. 8'h50
  - v. 8'h0D
  - vi. 8'h0D
  - vii. 8'h50
  - viii. 8'h50

**2.21** The synthesized hardware is a 4-bit shift register.

**2.22** The synthesized hardware is a single flip-flop.

**2.23** Both modules are synthesized to 4-bit shift registers. There are no differences between the two shift registers.

**2.24 (a)** D1 = 5, D2 = 1. The values of D1 and D2 swap.

**(b)** D1 = 1, D2 = 1. The values of D1 and D2 do not swap.


**(c)** iii

**2.25** a; y must be in the sensitivity list, otherwise *sum* and *carry* will not update from changes to y


**2.26**

| ns | $\Delta$ | a | b | c | d | e | f |
|----|----------|---|---|---|---|---|---|
| 0  | +0       | 0 | 0 | 0 | 0 | 0 | 0 |
| 5  | +0       | 0 | 0 | 0 | 1 | 0 | 0 |
| 5  | +1       | 1 | 0 | 0 | 1 | 0 | 0 |
| 5  | +2       | 1 | 1 | 1 | 1 | 0 | 0 |
| 6  | +0       | 1 | 1 | 1 | 0 | 0 | 0 |
| 10 | +0       | 1 | 1 | 1 | 0 | 1 | 0 |
| 10 | +1       | 0 | 1 | 1 | 0 | 1 | 0 |
| 10 | +2       | 0 | 0 | 0 | 0 | 1 | 0 |

**2.27**

 

2.28

 

2.29 (a)

| ns | a | b | c |
|----|---|---|---|
| 0  | 1 | 0 | 0 |
| 4  | 1 | 1 | 0 |
| 5  | 1 | 1 | 1 |
| 10 | 1 | 0 | 1 |
| 15 | 1 | 1 | 0 |
| 20 | 1 | 0 | 1 |
| 25 | 1 | 0 | 0 |
| 30 | 1 | 1 | 0 |
| 35 | 1 | 1 | 1 |
| 40 | 1 | 0 | 1 |
| 45 | 1 | 0 | 0 |

(b)

| ns | a | b | c |
|----|---|---|---|
| 0  | 1 | 0 | 0 |
| 4  | 1 | 1 | 0 |
| 5  | 1 | 1 | 1 |
| 10 | 1 | 0 | 1 |
| 15 | 1 | 1 | 0 |
| 20 | 1 | 0 | 1 |
| 25 | 1 | 0 | 0 |
| 30 | 1 | 1 | 0 |
| 35 | 1 | 1 | 1 |
| 40 | 1 | 0 | 1 |
| 45 | 1 | 0 | 0 |


(c)

| ns | a | b | c |
|----|---|---|---|
| 0  | 1 | 0 | 0 |
| 4  | 1 | 1 | 0 |
| 9  | 1 | 1 | 1 |
| 10 | 1 | 0 | 1 |
| 15 | 1 | 1 | 0 |
| 20 | 1 | 0 | 1 |
| 25 | 1 | 0 | 0 |
| 30 | 1 | 1 | 0 |
| 35 | 1 | 1 | 1 |
| 40 | 1 | 0 | 1 |
| 45 | 1 | 0 | 0 |


(d)

| ns | a | b | c |
|----|---|---|---|
| 0  | 1 | 0 | 0 |
| 4  | 1 | 1 | 0 |
| 10 | 1 | 0 | 0 |
| 15 | 1 | 1 | 0 |
| 20 | 1 | 0 | 1 |
| 25 | 1 | 0 | 0 |
| 30 | 1 | 1 | 0 |
| 35 | 1 | 1 | 1 |
| 40 | 1 | 0 | 1 |
| 45 | 1 | 0 | 0 |

2.30

 

2.31

 


2.32

| ns | $\Delta$ | a | b | c | d |
|----|----------|---|---|---|---|
| 4  | +0       | 0 | 0 | 0 | 0 |
| 5  | +0       | 1 | 0 | 0 | 0 |
| 10 | +0       | 1 | 1 | 0 | 0 |
| 10 | +1       | 0 | 1 | 0 | 0 |
| 11 | +0       | 0 | 1 | 0 | 1 |
| 12 | +0       | 0 | 1 | 1 | 1 |
| 15 | +0       | 0 | 0 | 1 | 1 |




- 2.33 (a) 6'b111011  
 (b) 3'b001  
 (c) 3'b001  
 (d) 1'b0  
 (e) 3'b111


2.34 (a)

 


(b)

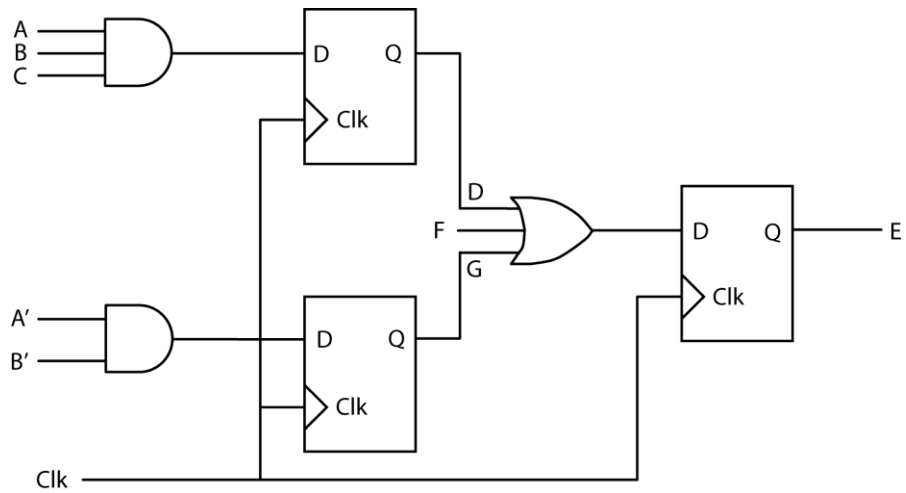

2.35

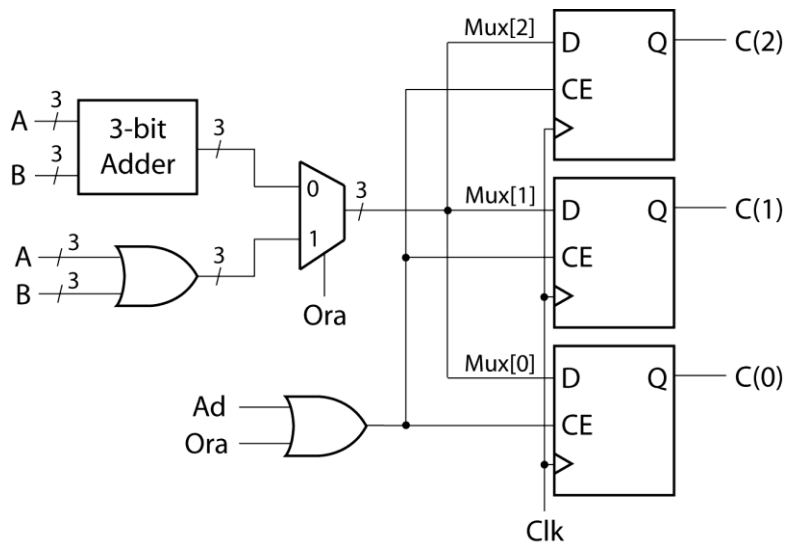

2.36

 

Clr is asynchronous, whereas C affects a synchronous input to the D flip-flop.

2.37 (a) `assign #10 F = (C == 0) ? ((D==0)? ~A: B) : ((D==0)? ~B: 0);`


(b) `always @(*)  
begin  
  if(C==0 && D==0)  
    #10 F = ~A;  
  else if(C==0 && D==1)  
    #10 F = B;  
  else if(C==1 && D==0)  
    #10 F = ~B;  
  else  
    #10 F = 0;  
end`

(c) `always @(*)  
begin  
  case(sel)  
    0: #10 F = ~A;  
    1: #10 F = B;  
    2: #10 F = ~B;  
    3: #10 F = 0;  
  endcase  
end`

2.38 (a) `module 1:  
  always @(C, B1, B2, B3)  
  begin  
    if (C == 1)  
      A <= B1;  
    else if (C == 2)  
      A <= B2;  
    else if (C == 3)  
      A <= B3;  
    else  
      A <= 0;  
  end`

`module 2:  
  assign A = (C==1)? B1 : ((C==2)? B2 : ((C==3)? B3 : 0));`

(b)

 

2.39 (a) 

```
module SR_Latch(S, R, P, Q);
 input S, R;
 output P, Q;

 assign Q = (S)? 1 : ((R)? 0 : Q);
 assign P = ~Q;

endmodule
```

(b) 

```
assign Q = S | (~R & Q);
assign P = ~Q;
```


(c) 

```
assign Q = ~(R | P);
assign P = ~(S | Q);
```


- 2.40
- i. 8'b00010100
  - ii. 8'b00010100
  - iii. 8'b11111100
  - iv. 8'b11111100
  - v. 8'b00010100
  - vi. 8'b00010100

- 2.41
- i. 32'hFFFFFF5B
  - ii. 32'hFFFFFF5B
  - iii. 32'h0000015B
  - iv. 32'h0000015B
  - v. 32'h0000005B
  - vi. 32'h0000005B

2.42 (a)

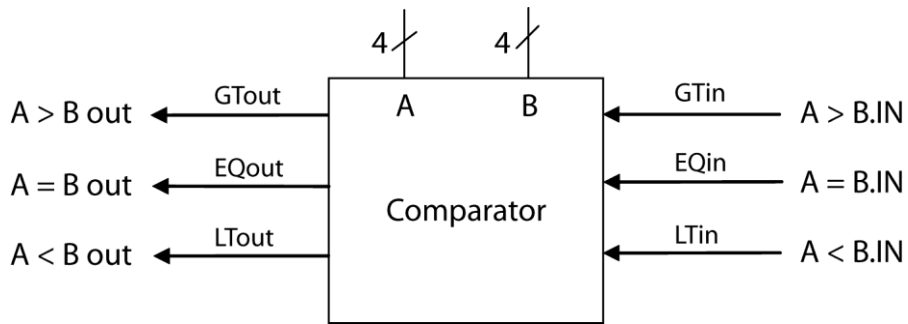

(b)

 

(c) 

```
module comp4bit(A, B, EQin, GTin, LTin, EQout, GTout, LTout);
 input[3:0] A, B;
 input EQin, GTin, LTin;
 output reg EQout, GTout, LTout;
```

```
 initial begin
 EQout = 0;
 GTout = 0;
 LTout = 0;
 end

 always @(A, B, EQin, GTin, LTin)
 begin
 if(A > B) begin
 EQout <= 0;
 GTout <= 1;
 LTout <= 0;
 end
 else if(A < B) begin
 EQout <= 0;
 GTout <= 0;
 LTout <= 1;
 end
 else if(GTin == 1) begin
 EQout <= 0;
 GTout <= 1;
 LTout <= 0;
 end
 else if(LTin == 1) begin
 EQout <= 0;
 GTout <= 0;
 LTout <= 1;
 end
 else begin
 EQout <= 1;
 GTout <= 0;
 LTout <= 0;
 end
 end
end
endmodule
```

(d) 

```
module comp8bit(A, B, EQi, GTi, LTi, EQ, GT, LT);
 input[7:0] A, B;
 input EQi, GTi, LTi;
 output EQ, GT, LT;

 wire LowEQ, LowGT, LowLT;

 comp4bit C1(A[3:0], B[3:0], EQi, GTi, LTi, LowEQ, LowGT, LowLT);
 comp4bit C2(A[7:4], B[7:4], LowEQ, LowGT, LowLT, EQ, GT, LT);
endmodule
```

```

2.43 module shift_reg(SI, EN, CK, SO);
 input SI, EN, CK;
 output SO;
 reg[15:0] register;

 initial begin
 register <= 0;
 end

 always @(posedge CK)
 begin
 if(EN == 1)
 register <= {SI, register[15:1]};
 end

 assign SO = register[0];
endmodule

```


```

2.44 (a) module shift74194(D, S, SDR, SDL, CLRb, CLK, Q);
 input[3:0] D;
 input[1:0] S;
 input SDR, SDL, CLRb, CLK;
 output reg [3:0] Q;

 initial begin
 Q <= 0;
 end

 always @(CLK, CLRb)
 begin
 if(CLRb == 0)
 Q <= 4'b0000;
 else if(CLK == 1)
 begin
 case(S)
 0: Q <= Q;
 1: Q <= {Q[2:0],SDL};
 2: Q <= {SDR, Q[3:1]};
 3: Q <= D;
 endcase
 end
 end
endmodule

```

 

```

module bit8shift(X, S, RSD, LSD, CLRb, CLK, Y);
 input[7:0] X;
 input[1:0] S;
 input RSD, LSD, CLRb, CLK;
 output[7:0] Y;

 shift74194 S1(X[3:0], S, Y[4], LSD, CLRb, CLK, Y[3:0]);
 shift74194 S2(X[7:4], S, RSD, Y[3], CLRb, CLK, Y[7:4]);
endmodule

```

2.45 (a)

```

module Counter(D, CLK, CLR, ENT, ENP, UP, LOAD, Q, CO);
 input[3:0] D;
 input CLK, CLR, ENT, ENP, UP, LOAD;
 output reg[3:0] Q;
 output CO;

 initial begin
 Q = 0;
 end

 assign CO = ((ENT == 1) && ((UP == 1 && (Q == 4'b1001)) ||
 (UP == 0 && (Q == 4'b0000))));

 always @(CLK, CLR)
 begin
 if(CLR == 0)
 Q <= 0;
 else if(CLK == 1)
 begin
 if(LOAD == 0)
 Q <= D;
 else if(ENT == 1 && ENP == 1 && UP == 0) begin
 if(Q == 0)
 Q <= 4'b1001;
 else
 Q <= Q - 1;
 end
 else if(ENT == 1 && ENP == 1 && UP == 1) begin
 if(Q == 4'b1001)
 Q <= 0;
 else
 Q <= Q + 1;
 end
 end
 end
 endmodule

```

(b)

```

module Century_Counter(Din1, Din2, CLK, CLR, ENT, ENP, UP, LOAD,
Count, CO);
 input [3:0] Din1, Din2;
 input CLK, CLR, ENT, ENP, UP, LOAD;
 output [7:0] Count;
 output CO;

 wire [3:0] Qout1, Qout2;
 wire Carry1, Carry2;

 Counter ct1(Din1, CLK, CLR, ENT, ENP, UP, LOAD, Qout1, Carry1);
 Counter ct2(Din2, CLK, CLR, ENT, Carry1, UP, LOAD, Qout2,
Carry2);

```

```

 assign Count = {Qout2, Qout1};
 assign CO = Carry2;
endmodule

```

The block diagram is similar to Figure 2-45 with an "Up" input added to each counter.

```

(c) add wave *
 force Din2 4'b1001
 force Din1 4'b1000
 force CLK 0 0 ns, 1 50 ns -repeat 100 ns
 force CLR 1 0 ns, 0 1000 ns
 force LOAD 0 0 ns, 1 100 ns
 force ENT 1 0 ns, 0 400 ns, 1 600 ns
 force ENP 1
 force UP 1 0 ns, 0 500 ns
 run 1200 ns

```

- 2.46** Students should look on the web for 74HC192 data sheet. CLR is active high. LOADB is active low. Counting up happens when UP has a rising edge and DOWN=1. Counting down happens when DOWN has a rising edge and UP=1. CARRY indicates terminal count in the up direction, i.e. 9. BORROW indicates terminal count in the down direction, i.e. 0.

| Operating Mode | CLR | LOADB | UP | DOWN | D    | Q         | Borrow | Carry |
|----------------|-----|-------|----|------|------|-----------|--------|-------|
| Clear          | 1   | X     | X  | 0    | XXXX | 0000      | 0      | 1     |
|                | 1   | X     | X  | 1    | XXXX | 0000      | 1      | 1     |
| Load           | 0   | 0     | X  | X    | XXXX | Q = D     | 1*     | 1*    |
| Count Up       | 0   | 1     | ↑  | 1    | XXXX | Q = Q + 1 | 1      | 1**   |
| Count Down     | 0   | 1     | 1  | ↑    | XXXX | Q = Q - 1 | 1**    | 1     |

\* when loading, if the input is 0 and down = 0, borrow will be 0. If the input is 9 and up = 0, carry will be 0

\*\* Borrow = 0 when the counter is in state 0 and down = 0. Carry = 0 when the counter is in state 9 and up = 0.

```

module count74HC192(DOWN, UP, CLR, LOADB, BORROW, CARRY, D, Q);
 input DOWN, UP, CLR, LOADB;
 input[3:0] D;
 output BORROW, CARRY;
 output reg[3:0] Q;

 initial begin
 Q = 0;
 end

 always @(DOWN, UP, CLR, LOADB)
 begin
 if(CLR == 1)
 Q <= 0;
 else if(LOADB == 0)
 Q <= D;
 else if(DOWN == 1) begin
 @(posedge UP)
 if(Q == 4'b1001)
 Q <= 0;
 else
 Q <= Q + 1;
 end
 else if(UP == 1) begin
 @(posedge DOWN)

```

```

 if(Q == 0)
 Q <= 4'b1001;
 else
 Q <= Q - 1;
 end
end
end

assign BORROW = (DOWN == 0 && Q == 0)? 0 : 1;
assign CARRY = (UP == 0 && Q == 4'b1001)? 0 : 1;
endmodule

```

2.47 (a)


```

module shift8(Q, D, CLR, CLK, S0, S1, LSI, RSI);
 input[7:0] D;
 output reg[7:0] Q;
 input CLR, CLK, S0, S1, LSI, RSI;

 initial begin
 Q = 0;
 end

 always @(CLK, CLR)
 begin
 if(CLR == 1)
 Q <= 0;
 else if(CLK == 1) begin
 if(S0 == 1 && S1 == 1)
 Q <= D;
 else if(S0 == 0 && S1 == 1)
 Q <= {RSI, Q[7:1]};
 else if(S0 == 1 && S1 == 0)
 Q <= {Q[6:0], LSI};
 else
 Q <= Q;
 end
 end
endmodule

```

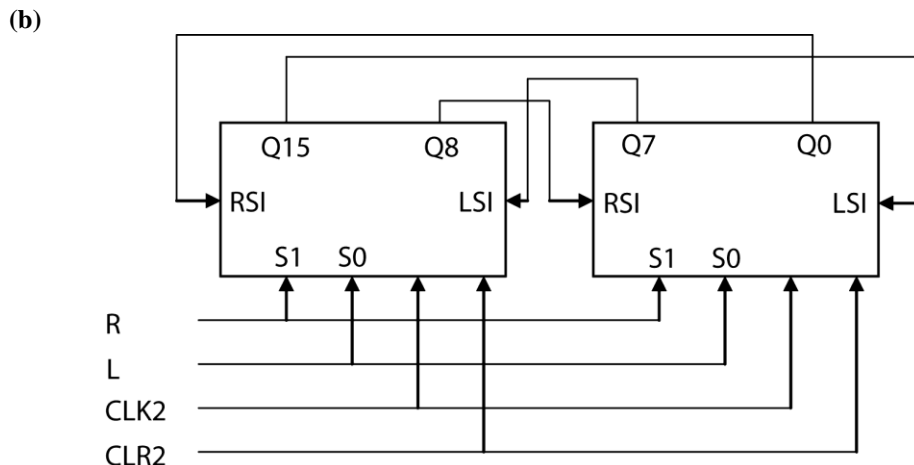

Note: D is not shown in the diagram.

(c)

```

module shiftreg(QQ, DD, CLK2, CLR2, L, R);
 input[15:0] DD;
 input CLK2, CLR2, L, R;

```



```

 output[15:0] QQ;

 shift8 SR1(QQ[15:8], DD[15:8], CLR2, CLK2, L, R, QQ[7], QQ[0]);
 shift8 SR2(QQ[7:0], DD[7:0], CLR2, CLK2, L, R, QQ[15], QQ[8]);
 endmodule

```

**2.48**

```

module countQ1(clk, Ld8, Enable, S5, Q);
 input clk, Ld8, Enable;
 output S5;
 output[3:0] Q;

 reg[3:0] Qint;

 initial begin
 Qint = 0;
 end

 always @(posedge clk)
 begin
 if(Ld8 == 1)
 Qint <= 4'b1000;
 else if(Enable == 1)
 begin
 if(Qint == 4'b0011)
 Qint <= 4'b1000;
 else
 Qint <= Qint - 1;
 end
 end

 assign S5 = (Qint == 4'b0101)? 1 : 0;
 assign Q = Qint;
 endmodule

```

**2.49 (a)**

```


module up_down(CLK, CLR, LD, UP, D, Q);
 input CLK, CLR, LD, UP;
 input[3:0] D;
 output reg[3:0] Q;

 initial begin
 Q = 0;
 end

 always @(negedge CLK)
 begin
 if(CLR == 1)
 Q <= 4'b0000;
 else if(LD == 1)
 Q <= D;
 else if(UP == 1)
 Q <= Q + 1;
 else
 Q <= Q - 1;
 end
 endmodule

```

(b)

 

(c)

```


module modulo6(CLK, Reset, CNT, Q);
 input CLK, Reset, CNT;
 output[3:0] Q;
 wire load, clock;

 assign load = Reset | (~Q[0] & Q[1] & Q[2] & ~Q[3]);
 assign clock = CLK & CNT;

 up_down U1(clock, 1'b0, load, 1'b1, 4'b0001, Q);
endmodule

```

2.50 (a)

 

(b)

| Present State | Next State |       | X = 0 |    | X = 1 |    |
|---------------|------------|-------|-------|----|-------|----|
|               | X = 0      | X = 1 | Z1    | Z2 | Z1    | Z2 |
| S0            | S0         | S1    | 1     | 0  | 0     | 0  |
| S1            | S1         | S2    | 0     | 1  | 0     | 1  |
| S2            | S2         | S3    | 0     | 1  | 0     | 1  |
| S3            | S0         | S1    | 0     | 0  | 1     | 0  |

2.51 The following solutions utilize the solution for 1.13.

```

(a) module P2_51a(X, CLK, S, V);
 input X, CLK;
 output S, V;

 reg [2:0] StateTable0 [5:0];
 reg [2:0] StateTable1 [5:0];
 reg [1:0] OutTable0 [5:0];
 reg [1:0] OutTable1 [5:0];

 reg [2:0] State;
 wire [2:0] NextState;

```

```

initial begin
 StateTable0[0] <= 1; StateTable1[0] <= 1;
 StateTable0[1] <= 2; StateTable1[1] <= 4;
 StateTable0[2] <= 3; StateTable1[2] <= 3;
 StateTable0[3] <= 0; StateTable1[3] <= 0;
 StateTable0[4] <= 3; StateTable1[4] <= 5;
 StateTable0[5] <= 0; StateTable1[5] <= 0;
 OutTable0[0] <= 2'b00; OutTable1[0] <= 2'b10;
 OutTable0[1] <= 2'b10; OutTable1[1] <= 2'b00;
 OutTable0[2] <= 2'b00; OutTable1[2] <= 2'b10;
 OutTable0[3] <= 2'b00; OutTable1[3] <= 2'b10;
 OutTable0[4] <= 2'b10; OutTable1[4] <= 2'b00;
 OutTable0[5] <= 2'b10; OutTable1[5] <= 2'b01;
 State <= 0;
end

 assign NextState = (X==0)? StateTable0[State] :
StateTable1[State];
 assign S = (X==0)? OutTable0[State][1] : OutTable1[State][1];
 assign V = (X==0)? OutTable0[State][0] : OutTable1[State][0];

 always @(negedge CLK)
 begin
 State <= NextState;
 end
endmodule

```

example simulation commands:

```

add wave *
force CLK 1 0 ns, 0 10 ns -repeat 20 ns
force X 1 0 ns, 0 15 ns, 1 35 ns, 0 75 ns, 1 95 ns, 0 175 ns
run 240 ns

```

```

(b) module P2_51b(X, CLK, S, V);
 input X, CLK;
 output S, V;

 reg Q1, Q2, Q3;

 initial begin
 Q1 <= 0;
 Q2 <= 0;
 Q3 <= 0;
 end

 always @(negedge CLK)
 begin
 Q1 <= (~Q1 & Q3);
 Q2 <= (~Q2 & ~Q3) | (X & ~Q1 & Q2);
 Q3 <= (~Q1 & Q3) | (Q2 & ~Q3);
 end

 assign S = (X & ~Q2) | (~X & Q2);
 assign V = (X & Q1 & Q2);
endmodule

```

Read each set of outputs after 1/4 clock period before the falling edge of the clock but no later than the falling edge of the clock.

```

(c) module P2_51c(X, CLK, S, V);
 input X, CLK;
 output S, V;

 wire Q1, Q2, Q3;
 wire XN, Q1N, Q2N, Q3N;
 wire D1, D2, D3;
 wire A1, A2, A3, A4, A5, A6;

 Inverter I1(X, XN);
 And2 G1(Q1N, Q3, D1);
 And2 G2(Q2N, Q3N, A1);
 And3 G3(X, Q1N, Q2, A2);
 Or2 G4(A1, A2, D2);
 And2 G5(Q1N, Q3, A3);
 And2 G6(Q2, Q3N, A4);
 Or2 G7(A3, A4, D3);
 And2 G8(X, Q2N, A5);
 And2 G9(XN, Q2, A6);
 Or2 G10(A5, A6, S);
 And3 G11(X, Q1, Q2, V);
 DFF DFF1(D1, CLK, Q1, Q1N);
 DFF DFF2(D2, CLK, Q2, Q2N);
 DFF DFF3(D3, CLK, Q3, Q3N);
endmodule

```

See Section 2.15 for the definition of the DFF component. The And3, And2, Or2, and Inverter components are all similar to the Nand3 component given on pages 109-110 (section 2.15).

**2.52** The following solutions utilize the solution for 1.14.

```

(a) module P2_52a(X, CLK, D, B);
 input X, CLK;
 output reg D, B;
 reg[2:0] State, NextState;

 initial begin
 State <= 0;
 NextState <= 0;
 end

 always @(State, X)
 begin
 case(State)
 0:begin
 if(X == 0)
 begin
 D <= 0;
 B <= 0;
 NextState <= 1;
 end
 else begin
 D <= 1;
 B <= 0;
 NextState <= 1;
 end
 end
 1:begin
 if(X == 0)
 begin
 D <= 1;

```

```

 B <= 0;
 NextState <= 2;
 end
 else begin
 D <= 0;
 B <= 0;
 NextState <= 3;
 end
end
2: begin
 if(X == 0)
 begin
 D <= 1;
 B <= 0;
 NextState <= 4;
 end
 else begin
 D <= 0;
 B <= 0;
 NextState <= 5;
 end
end
3: begin
 if(X == 0)
 begin
 D <= 0;
 B <= 0;
 NextState <= 5;
 end
 else begin
 D <= 1;
 B <= 0;
 NextState <= 5;
 end
end
4: begin
 if(X == 0)
 begin
 D <= 1;
 B <= 1;
 NextState <= 0;
 end
 else begin
 D <= 0;
 B <= 0;
 NextState <= 0;
 end
end
5: begin
 if(X == 0)
 begin
 D <= 0;
 B <= 0;
 NextState <= 0;
 end
 else begin
 D <= 1;
 B <= 0;
 NextState <= 0;
 end
end
endcase
end

```

```

always @(negedge CLK)
begin
 State <= NextState;
end
endmodule

```

example simulation commands:

```

add wave *
force CLK 1 0 ns, 0 10 ns -repeat 20 ns
force X 1 0 ns, 0 15 ns, 1 35 ns, 0 75 ns, 1 95 ns, 0 175 ns
run 240 ns

```

(b)

```

module P2_52b(X, CLK, D, B);
input X, CLK;
output D, B;

reg Q1, Q2, Q3;

initial begin
 Q1 <= 0;
 Q2 <= 0;
 Q3 <= 0;
end

always @(negedge CLK)
begin
 Q1 <= (~Q1 & ~Q3) | (~X & Q1 & ~Q2);
 Q2 <= (~Q2 & Q3);
 Q3 <= ~Q2 & (Q3 | Q1);
end

assign D = (~X & Q1) | (X & ~Q1 & Q3);
assign B = ~X & Q1 & Q2;
endmodule

```

Read each set of outputs after 3/4 clock period before the falling edge of the clock but no later than the falling edge of the clock.

(c)

```

module PC_52c(X, CLK, D, B);
input X, CLK;
output D, B;
wire A1, A2, A3;
wire Q1, Q2, Q3;
wire Q1N, Q2N, Q3N, XN, One;
parameter I = 1;

Inverter I1(X, XN);
Nand2 G1(XN, Q2N, A1);
JKFF FF1(I, I, Q3N, A1, CLK, Q1, Q1N);
JKFF FF2(I, I, Q3, I, CLK, Q2, Q2N);
JKFF FF3(I, I, Q1, Q2, CLK, Q3, Q3N);
Nand2 G2(XN, Q1, A2);
Nand3 G3(X, Q1N, Q3, A3);
Nand2 G4(A2, A3, D);
And3 G5(XN, Q1, Q2, B);
endmodule

```

The Nand2, And3, and Inverter components are similar to the Nand3 component in Section 2.15. The JKFF component is similar to the DFF component in Section 2.15.

```

2.53 module moore_mach(X1, X2, Clk, Z);
 input X1, X2;
 input Clk;
 output Z;

 reg[1:0] state;

 initial begin
 state <= 1;
 end

 always @(negedge Clk)
 begin
 case(state)
 1: begin
 if((X1 ^ X2) == 1)begin
 #10 state <= 2;
 end
 end
 2: begin
 if(X2 == 1)begin
 #10 state <= 1;
 end
 end
 default: begin
 end
 endcase
 end

 assign #10 Z = state[1];
endmodule

```

```

2.54 module P_54(x1, x2, clk, z1, z2);
 input x1, x2, clk;
 output z1, z2;

 reg[1:0] state, next_state;

 initial begin
 state <= 1;
 next_state <= 1;
 end

 always @(state, x1, x2)
 begin
 case(state)
 1: begin
 if({x1,x2} == 2'b00)
 #10 next_state <= 3;
 else if({x1,x2} == 2'b01)
 #10 next_state <= 2;
 else
 #10 next_state <= 1;
 end
 2: begin
 if({x1,x2} == 2'b00)
 #10 next_state <= 2;
 else if({x1,x2} == 2'b01)
 #10 next_state <= 1;
 else
 #10 next_state <= 3;
 end
 end
endmodule

```

```

end
3: begin
 if({x1,x2} == 2'b00)
 #10 next_state <= 1;
 else if({x1,x2} == 2'b01)
 #10 next_state <= 2;
 else
 #10 next_state <= 3;
 end
endcase
end

always @(negedge clk)
begin
 #5 state <= next_state;
end

assign #10 z1 = (state == 2)? 1: 0;
assign #10 z2 = (state == 3)? 1: 0;
endmodule

```

2.55 (a) *nextstate* is not always assigned a new value in the conditional statements, i.e. else clauses are not specified. Therefore, a latch will be created to hold *nextstate* to its old value.

(b) The latch output would have the most recent value of *nextstate*.

(c)

```

always @(state, X)
begin
 case(state)
 0: begin
 if(X == 1)
 nextstate <= 1;
 else
 nextstate <= 0;
 end
 1: begin
 if(X == 0)
 nextstate <= 2;
 else
 nextstate <= 1;
 end
 2: begin
 if(X == 1)
 nextstate <= 0;
 else
 nextstate <= 2;
 end
 endcase
 end
end

```

(d) Yes, unconditionally set *nextstate* to a default value at the beginning of the always block

2.56 The nonblocking assignments must be changed to blocking assignments. Otherwise *sel* will not update for current use. *sel* updates only at the end of the process so the case statement will get the wrong value.



2.57

| ns | $\Delta$ | A | B | D |
|----|----------|---|---|---|
| 0  | +0       | 0 | 0 | 0 |
| 5  | +0       | 1 | 0 | 0 |
| 15 | +0       | 1 | 0 | 1 |
| 15 | +1       | 1 | 1 | 1 |
| 25 | +0       | 1 | 1 | 0 |
| 25 | +1       | 1 | 0 | 0 |
| 35 | +0       | 1 | 0 | 1 |
| 35 | +1       | 1 | 1 | 1 |
| 40 | +0       | 0 | 1 | 1 |

2.58 Rising-edge triggered toggle flip-flop (T-flip-flop), with asynchronous active-high clear signal

2.59 (a) `module ROM4_3(ROMin, ROMout);`  
`input[3:0] ROMin;`  
`output[2:0] ROMout;`  
  
`reg[2:0] ROM16X3 [15:0];`  
  
`initial begin`  
`ROM16X3[0] <= 3'b000;`  
`ROM16X3[1] <= 3'b001;`  
`ROM16X3[2] <= 3'b001;`  
`ROM16X3[3] <= 3'b010;`  
`ROM16X3[4] <= 3'b001;`  
`ROM16X3[5] <= 3'b010;`  
`ROM16X3[6] <= 3'b010;`  
`ROM16X3[7] <= 3'b011;`  
`ROM16X3[8] <= 3'b001;`  
`ROM16X3[9] <= 3'b010;`  
`ROM16X3[10] <= 3'b010;`  
`ROM16X3[11] <= 3'b011;`  
`ROM16X3[12] <= 3'b010;`  
`ROM16X3[13] <= 3'b011;`  
`ROM16X3[14] <= 3'b011;`  
`ROM16X3[15] <= 3'b100;`  
`end`  
  
`assign ROMout = ROM16X3[ROMin];`  
`endmodule`

(b) `module P_59(A, count);`  
`input[11:0] A;`  
`output[3:0] count;`  
  
`wire[2:0] B,C,D;`  
  
`ROM4_3 R1(A[11:8], B);`  
`ROM4_3 R2(A[7:4], C);`  
`ROM4_3 R3(A[3:0], D);`  
  
`assign count = {1'b0, B} + C + D;`  
`endmodule`

(c)

| A            | Count | D   | C   | B   |
|--------------|-------|-----|-----|-----|
| 111111111111 | 1100  | 100 | 100 | 100 |
| 010110101101 | 0111  | 011 | 010 | 010 |
| 100001011100 | 0101  | 010 | 010 | 001 |

2.60

| a | b | c | y <sub>7</sub> | y <sub>6</sub> | y <sub>5</sub> | y <sub>4</sub> | y <sub>3</sub> | y <sub>2</sub> | y <sub>1</sub> | y <sub>0</sub> |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              |
| 0 | 0 | 1 | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              |
| 0 | 1 | 0 | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              |
| 0 | 1 | 1 | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              |
| 1 | 0 | 0 | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              |
| 1 | 0 | 1 | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              |
| 1 | 1 | 0 | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              |
| 1 | 1 | 1 | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 0              |

```
module decoder(A, B, C, Y);
 input A,B,C;
 output[7:0] Y;
 wire[2:0] index;
 reg[7:0] ROM[0:7];

 initial begin
 ROM[0] <= 8'b00000001;
 ROM[1] <= 8'b00000010;
 ROM[2] <= 8'b00000100;
 ROM[3] <= 8'b00001000;
 ROM[4] <= 8'b00010000;
 ROM[5] <= 8'b00100000;
 ROM[6] <= 8'b01000000;
 ROM[7] <= 8'b10000000;
 end

 assign index = {A,B,C};
 assign Y = ROM[index];
endmodule
```

2.61

```
(a) always
begin
 MAX = A[0];
 for (i = 0; i < 20; i = i + 1) begin
 if(A[i] > MAX)
 MAX = A[i];
 end
end
```

```
(b) always
begin
 MAX = A[0];
 i = 1;
 while (i < 20) begin
 if(A[i] > MAX)
 MAX = A[i];
 i = i + 1;
 end
end
```

```

2.62 module tester;
 reg CLK;
 reg [0:11] X;
 reg [0:11] Z;

 initial begin
 X = 12'b011011011100;
 Z = 12'b100110110110;
 CLK = 1;
 end

 reg Xin;
 wire Zout;
 integer i;

 always
 #50 CLK = ~CLK;

 Mealy M1(Xin, CLK, Zout);

 always
 begin
 for(i = 0; i < 12; i = i + 1) begin
 @(posedge CLK)
 #10 Xin = X[i];
 #80 // wait to read output
 if(Zout != Z[i]) begin
 $display("Error");
 $stop;
 end
 end
 $display("sequence correct");
 $stop;
 end
 end
endmodule

```

```

2.63 module TestExcess3;
 reg[3:0] XA[1:10];
 reg[3:0] ZA[1:10];
 reg X, CLK;
 wire Z;
 integer i;
 integer j;

 initial begin
 X = 0;
 CLK = 0;
 XA[1] = 4'b0000;
 XA[2] = 4'b0001;
 XA[3] = 4'b0010;
 XA[4] = 4'b0011;
 XA[5] = 4'b0100;
 XA[6] = 4'b0101;
 XA[7] = 4'b0110;
 XA[8] = 4'b0111;
 XA[9] = 4'b1000;
 XA[10] = 4'b1001;
 ZA[1] = 4'b0011;
 ZA[2] = 4'b0100;
 ZA[3] = 4'b0101;
 ZA[4] = 4'b0110;
 ZA[5] = 4'b0111;
 ZA[6] = 4'b1000;
 end

```

```

 ZA[7] = 4'b1001;
 ZA[8] = 4'b1010;
 ZA[9] = 4'b1011;
 ZA[10] = 4'b1100;
end

always
 #50 CLK <= ~CLK;

Code_Converter C1(X, CLK, Z);

always
begin
 for(i = 1 ; i <= 10; i = i + 1)
 begin
 for(j= 0; j <= 3; j = j + 1)
 begin
 X = XA[i][j];
 @(posedge CLK);
 #(25);
 if(ZA[i][j] != Z) begin
 $display("sequence incorrect");
 $stop;
 end
 end
 end
 $display("all sequences correct");
 $stop;
end
endmodule

```

```

2.64 module testbench;
 wire S5;
 reg clk, Ld8, Enable;
 wire[3:0] Q;

 initial begin
 clk = 1;
 Ld8 = 1;
 Enable = 0;
 #100
 Ld8 = 0;
 Enable = 1;
 #500 Enable = 0;
 #200 Enable = 1;
 #1000 Enable = 0;
 end

 always
 #50 clk <= ~clk;

 always @(posedge S5)
 $display($time);

 countQ1 C1(clk, Ld8, Enable, S5, Q);
endmodule

```

```

2.65 module testSMQ1(correct);
 output reg correct;
 reg clk, X;
 integer i;
 wire Z;
 reg[1:5] answer;

```

```

initial begin
 answer[1] = 1;
 answer[2] = 1;
 answer[3] = 0;
 answer[4] = 1;
 answer[5] = 0;
 clk = 0;
 X = 1;
 #100 X = 0;
 #200 X = 1;
end

always
 #50 clk <= ~clk;

SMQ1 S1(X, clk, Z);

always
begin
 for(i = 1; i <= 5; i = i + 1)
 begin
 @(posedge clk);
 correct = (answer[i] == Z);
 if(correct == 0)
 $display($time);
 #10;
 end
 end
 $stop;
end
endmodule

```

