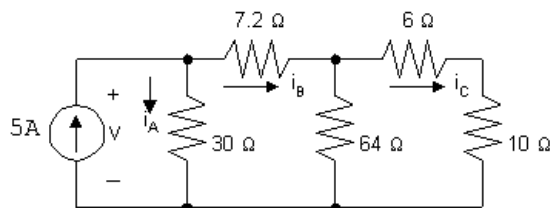


Simple Resistive Circuits

Assessment Problems

AP 3.1



Start from the right hand side of the circuit and make series and parallel combinations of the resistors until one equivalent resistor remains. Begin by combining the $6\ \Omega$ resistor and the $10\ \Omega$ resistor in series:

$$6\ \Omega + 10\ \Omega = 16\ \Omega$$

Now combine this $16\ \Omega$ resistor in parallel with the $64\ \Omega$ resistor:

$$16\ \Omega \parallel 64\ \Omega = \frac{(16)(64)}{16 + 64} = \frac{1024}{80} = 12.8\ \Omega$$


This equivalent $12.8\ \Omega$ resistor is in series with the $7.2\ \Omega$ resistor:

$$12.8\ \Omega + 7.2\ \Omega = 20\ \Omega$$

Finally, this equivalent $20\ \Omega$ resistor is in parallel with the $30\ \Omega$ resistor:

$$20\ \Omega \parallel 30\ \Omega = \frac{(20)(30)}{20 + 30} = \frac{600}{50} = 12\ \Omega$$

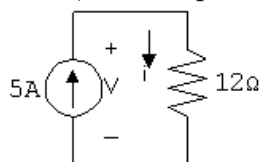Thus, the simplified circuit is as shown:



- [a] With the simplified circuit we can use Ohm's law to find the voltage across both the current source and the $12\ \Omega$ equivalent resistor:

$$v = (12\ \Omega)(5\ \text{A}) = 60\ \text{V}$$

- [b] Now that we know the value of the voltage drop across the current source, we can use the formula $p = -vi$ to find the power associated with the source:

$$p = -(60\ \text{V})(5\ \text{A}) = -300\ \text{W}$$

Thus, the source delivers 300 W of power to the circuit.

- [c] We now can return to the original circuit, shown in the first figure. In this circuit, $v = 60\ \text{V}$, as calculated in part (a). This is also the voltage drop across the $30\ \Omega$ resistor, so we can use Ohm's law to calculate the current through this resistor:

$$i_A = \frac{60\ \text{V}}{30\ \Omega} = 2\ \text{A}$$

Now write a KCL equation at the upper left node to find the current i_B :

$$-5\ \text{A} + i_A + i_B = 0 \quad \text{so} \quad i_B = 5\ \text{A} - i_A = 5\ \text{A} - 2\ \text{A} = 3\ \text{A}$$

Next, write a KVL equation around the outer loop of the circuit, using Ohm's law to express the voltage drop across the resistors in terms of the current through the resistors:

$$-v + 7.2i_B + 6i_C + 10i_C = 0$$


$$\text{So} \quad 16i_C = v - 7.2i_B = 60\ \text{V} - (7.2)(3) = 38.4\ \text{V}$$

$$\text{Thus} \quad i_C = \frac{38.4}{16} = 2.4\ \text{A}$$

Now that we have the current through the $10\ \Omega$ resistor we can use the formula $p = Ri^2$ to find the power:

$$p_{10\ \Omega} = (10)(2.4)^2 = 57.6\ \text{W}$$

AP 3.2

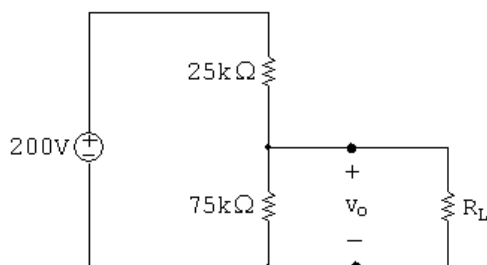

- [a] We can use voltage division to calculate the voltage v_o across the $75\ \text{k}\Omega$ resistor:

$$v_o(\text{no load}) = \frac{75,000}{75,000 + 25,000}(200\ \text{V}) = 150\ \text{V}$$

- [b] When we have a load resistance of $150\text{ k}\Omega$ then the voltage v_o is across the parallel combination of the $75\text{ k}\Omega$ resistor and the $150\text{ k}\Omega$ resistor. First, calculate the equivalent resistance of the parallel combination:

$$75\text{ k}\Omega \parallel 150\text{ k}\Omega = \frac{(75,000)(150,000)}{75,000 + 150,000} = 50,000\ \Omega = 50\text{ k}\Omega$$

Now use voltage division to find v_o across this equivalent resistance:

$$v_o = \frac{50,000}{50,000 + 25,000}(200\text{ V}) = 133.3\text{ V}$$

- [c] If the load terminals are short-circuited, the $75\text{ k}\Omega$ resistor is effectively removed from the circuit, leaving only the voltage source and the $25\text{ k}\Omega$ resistor. We can calculate the current in the resistor using Ohm's law:

$$i = \frac{200\text{ V}}{25\text{ k}\Omega} = 8\text{ mA}$$


Now we can use the formula $p = Ri^2$ to find the power dissipated in the $25\text{ k}\Omega$ resistor:

$$p_{25k} = (25,000)(0.008)^2 = 1.6\text{ W}$$

- [d] The power dissipated in the $75\text{ k}\Omega$ resistor will be maximum at no load since v_o is maximum. In part (a) we determined that the no-load voltage is 150 V , so we can use the formula $p = v^2/R$ to calculate the power:

$$p_{75k}(\text{max}) = \frac{(150)^2}{75,000} = 0.3\text{ W}$$

AP 3.3

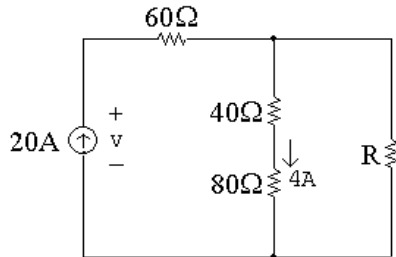

- [a] We will write a current division equation for the current through the 80Ω resistor and use this equation to solve for R :

$$i_{80\Omega} = \frac{R}{R + 40\ \Omega + 80\ \Omega}(20\text{ A}) = 4\text{ A} \quad \text{so} \quad 20R = 4(R + 120)$$

$$\text{Thus} \quad 16R = 480 \quad \text{and} \quad R = \frac{480}{16} = 30\ \Omega$$

- [b] With $R = 30\ \Omega$ we can calculate the current through R using current division, and then use this current to find the power dissipated by R , using the formula $p = Ri^2$:

$$i_R = \frac{40 + 80}{40 + 80 + 30}(20\text{ A}) = 16\text{ A} \quad \text{so} \quad p_R = (30)(16)^2 = 7680\text{ W}$$


- [c] Write a KVL equation around the outer loop to solve for the voltage v , and then use the formula $p = -vi$ to calculate the power delivered by the current source:

$$-v + (60\ \Omega)(20\ \text{A}) + (30\ \Omega)(16\ \text{A}) = 0 \quad \text{so} \quad v = 1200 + 480 = 1680\ \text{V}$$

$$\text{Thus, } p_{\text{source}} = -(1680\ \text{V})(20\ \text{A}) = -33,600\ \text{W}$$

Thus, the current source generates 33,600 W of power.

AP 3.4

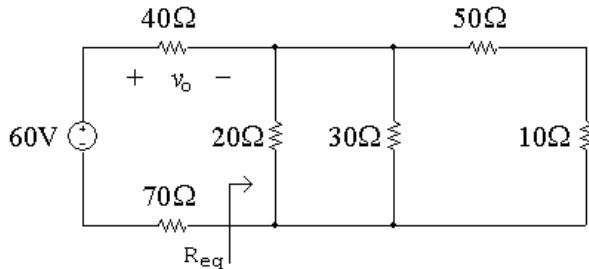

- [a] First we need to determine the equivalent resistance to the right of the $40\ \Omega$ and $70\ \Omega$ resistors:

$$R_{\text{eq}} = 20\ \Omega \parallel 30\ \Omega \parallel (50\ \Omega + 10\ \Omega) \quad \text{so} \quad \frac{1}{R_{\text{eq}}} = \frac{1}{20\ \Omega} + \frac{1}{30\ \Omega} + \frac{1}{60\ \Omega} = \frac{1}{10\ \Omega}$$

$$\text{Thus, } R_{\text{eq}} = 10\ \Omega$$

Now we can use voltage division to find the voltage v_o :

$$v_o = \frac{40}{40 + 10 + 70}(60\ \text{V}) = 20\ \text{V}$$

- [b] The current through the $40\ \Omega$ resistor can be found using Ohm's law:

$$i_{40\ \Omega} = \frac{v_o}{40} = \frac{20\ \text{V}}{40\ \Omega} = 0.5\ \text{A}$$

This current flows from left to right through the $40\ \Omega$ resistor. To use current division, we need to find the equivalent resistance of the two parallel branches containing the $20\ \Omega$ resistor and the $50\ \Omega$ and $10\ \Omega$ resistors:

$$20\ \Omega \parallel (50\ \Omega + 10\ \Omega) = \frac{(20)(60)}{20 + 60} = 15\ \Omega$$

Now we use current division to find the current in the $30\ \Omega$ branch:

$$i_{30\ \Omega} = \frac{15}{15 + 30}(0.5\ \text{A}) = 0.16667\ \text{A} = 166.67\ \text{mA}$$

- [c] We can find the power dissipated by the $50\ \Omega$ resistor if we can find the current in this resistor. We can use current division to find this current

from the current in the $40\ \Omega$ resistor, but first we need to calculate the equivalent resistance of the $20\ \Omega$ branch and the $30\ \Omega$ branch:


$$20\ \Omega \parallel 30\ \Omega = \frac{(20)(30)}{20 + 30} = 12\ \Omega$$

Current division gives:

$$i_{50\ \Omega} = \frac{12}{12 + 50 + 10}(0.5\ \text{A}) = 0.08333\ \text{A}$$

$$\text{Thus, } p_{50\ \Omega} = (50)(0.08333)^2 = 0.34722\ \text{W} = 347.22\ \text{mW}$$


AP 3.5 [a]

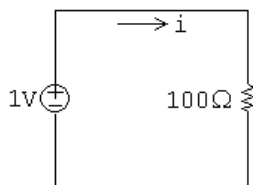

We can find the current i using Ohm's law:

$$i = \frac{1\ \text{V}}{100\ \Omega} = 0.01\ \text{A} = 10\ \text{mA}$$

[b]

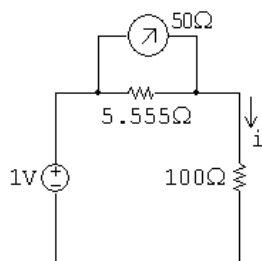


$$R_m = 50\ \Omega \parallel 5.555\ \Omega = 5\ \Omega$$

We can use the meter resistance to find the current using Ohm's law:

$$i_{\text{meas}} = \frac{1\ \text{V}}{100\ \Omega + 5\ \Omega} = 0.009524 = 9.524\ \text{mA}$$


AP 3.6 [a]

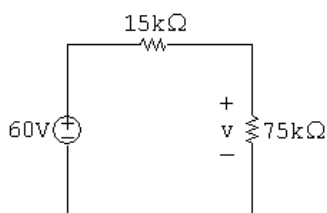

Use voltage division to find the voltage v :

$$v = \frac{75,000}{75,000 + 15,000}(60\ \text{V}) = 50\ \text{V}$$

[b]

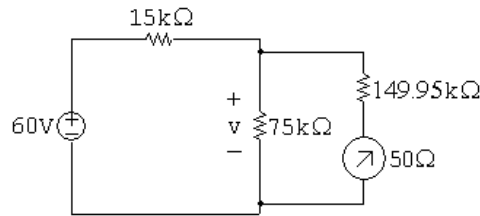

The meter resistance is a series combination of resistances:

$$R_m = 149,950 + 50 = 150,000 \Omega$$

We can use voltage division to find v , but first we must calculate the equivalent resistance of the parallel combination of the $75 \text{ k}\Omega$ resistor and the voltmeter:

$$75,000 \Omega \parallel 150,000 \Omega = \frac{(75,000)(150,000)}{75,000 + 150,000} = 50 \text{ k}\Omega$$

$$\text{Thus, } v_{\text{meas}} = \frac{50,000}{50,000 + 15,000}(60 \text{ V}) = 46.15 \text{ V}$$

AP 3.7 [a] Using the condition for a balanced bridge, the products of the opposite resistors must be equal. Therefore,

$$100R_x = (1000)(150) \quad \text{so} \quad R_x = \frac{(1000)(150)}{100} = 1500 \Omega = 1.5 \text{ k}\Omega$$

[b] When the bridge is balanced, there is no current flowing through the meter, so the meter acts like an open circuit. This places the following branches in parallel: The branch with the voltage source, the branch with the series combination R_1 and R_3 and the branch with the series combination of R_2 and R_x . We can find the current in the latter two branches using Ohm's law:

$$i_{R_1, R_3} = \frac{5 \text{ V}}{100 \Omega + 150 \Omega} = 20 \text{ mA}; \quad i_{R_2, R_x} = \frac{5 \text{ V}}{1000 + 1500} = 2 \text{ mA}$$

We can calculate the power dissipated by each resistor using the formula $p = Ri^2$:

$$p_{100\Omega} = (100 \Omega)(0.02 \text{ A})^2 = 40 \text{ mW}$$


$$p_{150\Omega} = (150 \Omega)(0.02 \text{ A})^2 = 60 \text{ mW}$$

$$p_{1000\Omega} = (1000 \Omega)(0.002 \text{ A})^2 = 4 \text{ mW}$$

$$p_{1500\Omega} = (1500 \Omega)(0.002 \text{ A})^2 = 6 \text{ mW}$$

Since none of the power dissipation values exceeds 250 mW , the bridge can be left in the balanced state without exceeding the power-dissipating capacity of the resistors.

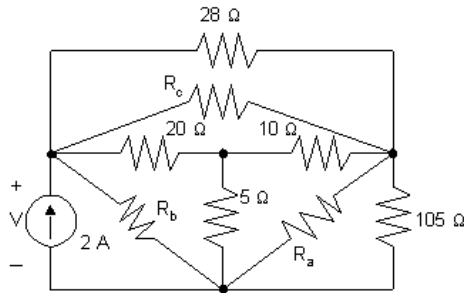AP 3.8 Convert the three Y-connected resistors, 20 Ω, 10 Ω, and 5 Ω to three Δ-connected resistors R_a , R_b , and R_c . To assist you the figure below has both the Y-connected resistors and the Δ-connected resistors




$$R_a = \frac{(5)(10) + (5)(20) + (10)(20)}{20} = 17.5 \Omega$$

$$R_b = \frac{(5)(10) + (5)(20) + (10)(20)}{10} = 35 \Omega$$

$$R_c = \frac{(5)(10) + (5)(20) + (10)(20)}{5} = 70 \Omega$$

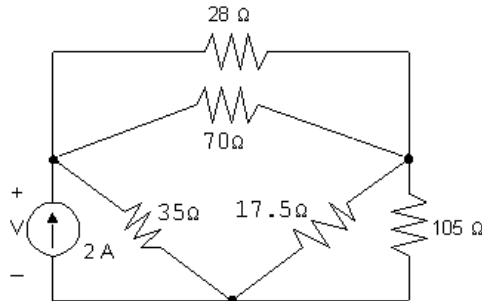The circuit with these new Δ-connected resistors is shown below:



From this circuit we see that the 70 Ω resistor is parallel to the 28 Ω resistor:

$$70 \Omega \parallel 28 \Omega = \frac{(70)(28)}{70 + 28} = 20 \Omega$$

Also, the 17.5 Ω resistor is parallel to the 105 Ω resistor:

$$17.5 \Omega \parallel 105 \Omega = \frac{(17.5)(105)}{17.5 + 105} = 15 \Omega$$

Once the parallel combinations are made, we can see that the equivalent 20 Ω resistor is in series with the equivalent 15 Ω resistor, giving an equivalent resistance of $20 \Omega + 15 \Omega = 35 \Omega$. Finally, this equivalent 35 Ω resistor is in parallel with the other 35 Ω resistor:


$$35 \Omega \parallel 35 \Omega = \frac{(35)(35)}{35 + 35} = 17.5 \Omega$$

Thus, the resistance seen by the 2 A source is $17.5\ \Omega$, and the voltage can be calculated using Ohm's law:


$$v = (17.5\ \Omega)(2\ \text{A}) = 35\ \text{V}$$

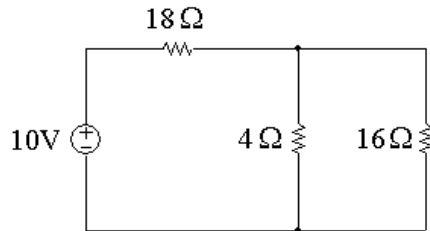Problems


- P 3.1 [a] The $6\text{ k}\Omega$ and $12\text{ k}\Omega$ resistors are in series, as are the $9\text{ k}\Omega$ and $7\text{ k}\Omega$ resistors. The simplified circuit is shown below:



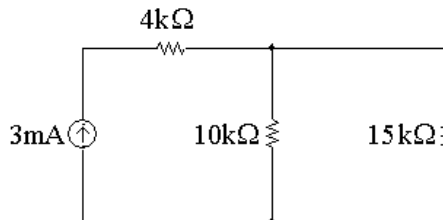
- [b] The $3\text{ k}\Omega$, $5\text{ k}\Omega$, and $7\text{ k}\Omega$ resistors are in series. The simplified circuit is shown below:



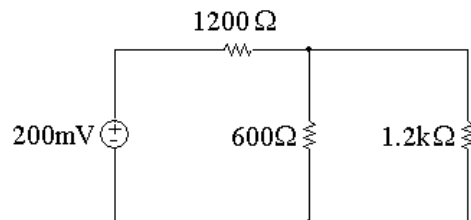
- [c] The 300Ω , 400Ω , and 500Ω resistors are in series. The simplified circuit is shown below:



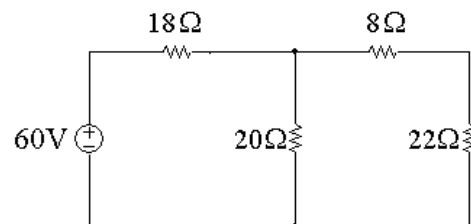
- P 3.2 [a] The 10Ω and 40Ω resistors are in parallel, as are the 100Ω and 25Ω resistors. The simplified circuit is shown below:



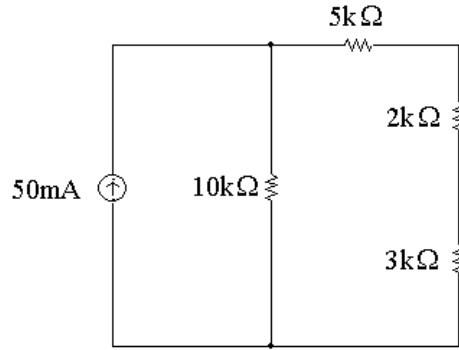- [b] The $9\text{ k}\Omega$, $18\text{ k}\Omega$, and $6\text{ k}\Omega$ resistors are in parallel. The simplified circuit is shown below:



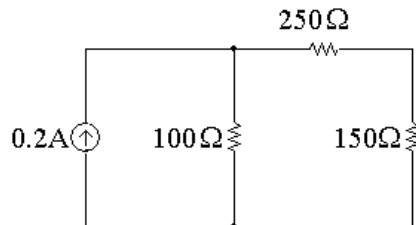- [c] The $600\ \Omega$, $200\ \Omega$, and $300\ \Omega$ resistors are in parallel. The simplified circuit is shown below:



- P 3.3 Always work from the side of the circuit furthest from the source. Remember that the current in all series-connected circuits is the same, and that the voltage drop across all parallel-connected resistors is the same.

$$[\mathbf{a}] R_{\text{eq}} = 6 + 12 + [4 \parallel (9 + 7)] = 6 + 12 + 4 \parallel 16 = 6 + 12 + 3.2 = 21.2\ \Omega$$

$$[\mathbf{b}] R_{\text{eq}} = 4\ \text{k} + [10\ \text{k} \parallel (3\ \text{k} + 5\ \text{k} + 7\ \text{k})] = 4\ \text{k} + 10\ \text{k} \parallel 15\ \text{k} = 4\ \text{k} + 6\ \text{k} = 10\ \text{k}\ \Omega$$

$$[\mathbf{c}] R_{\text{eq}} = 300 + 400 + 500 + (600 \parallel 1200) = 300 + 400 + 500 + 400 = 1600\ \Omega$$

- P 3.4 Always work from the side of the circuit furthest from the source. Remember that the current in all series-connected circuits is the same, and that the voltage drop across all parallel-connected resistors is the same.

$$[\mathbf{a}] R_{\text{eq}} = 18 + [100 \parallel 25 \parallel (10 \parallel 40 + 22)] = 18 + [100 \parallel 25 \parallel (8 + 22)]$$

$$= 18 + [100 \parallel 25 \parallel 30] = 18 + 12 = 30\ \Omega$$

$$[\mathbf{b}] R_{\text{eq}} = 10\ \text{k} \parallel [5\ \text{k} + 2\ \text{k} + (9\ \text{k} \parallel 18\ \text{k} \parallel 6\ \text{k})] = 10\ \text{k} \parallel [5\ \text{k} + 2\ \text{k} + 3\ \text{k}]$$

$$= 10\ \text{k} \parallel 10\ \text{k} = 5\ \text{k}\ \Omega$$

$$[\mathbf{c}] R_{\text{eq}} = 600 \parallel 200 \parallel 300 \parallel (250 + 150) = 600 \parallel 200 \parallel 300 \parallel 400 = 80\ \Omega$$

- P 3.5 [a] $R_{\text{ab}} = 10 + (5 \parallel 20) + 6 = 10 + 4 + 6 = 20\ \Omega$

$$[\mathbf{b}] R_{\text{ab}} = 30\ \text{k} \parallel 60\ \text{k} \parallel [20\ \text{k} + (200\ \text{k} \parallel 50\ \text{k})] = 30\ \text{k} \parallel 60\ \text{k} \parallel (20\ \text{k} + 40\ \text{k})$$

$$= 30\ \text{k} \parallel 60\ \text{k} \parallel 60\ \text{k} = 15\ \text{k}\ \Omega$$

P 3.6 [a] $60 \parallel 20 = 1200/80 = 15 \Omega$ $12 \parallel 24 = 288/36 = 8 \Omega$
 $15 + 8 + 7 = 30 \Omega$ $30 \parallel 120 = 3600/150 = 24 \Omega$
 $R_{ab} = 15 + 24 + 25 = 64 \Omega$

[b] $35 + 40 = 75 \Omega$ $75 \parallel 50 = 3750/125 = 30 \Omega$
 $30 + 20 = 50 \Omega$ $50 \parallel 75 = 3750/125 = 30 \Omega$
 $30 + 10 = 40 \Omega$ $40 \parallel 60 + 9 \parallel 18 = 24 + 6 = 30 \Omega$
 $30 \parallel 30 = 15 \Omega$ $R_{ab} = 10 + 15 + 5 = 30 \Omega$

[c] $50 + 30 = 80 \Omega$ $80 \parallel 20 = 16 \Omega$
 $16 + 14 = 30 \Omega$ $30 + 24 = 54 \Omega$
 $54 \parallel 27 = 18 \Omega$ $18 + 12 = 30 \Omega$
 $30 \parallel 30 = 15 \Omega$ $R_{ab} = 3 + 15 + 2 = 20 \Omega$

P 3.7 [a] For circuit (a)

$$R_{ab} = 4 \parallel (3 + 7 + 2) = 4 \parallel 12 = 3 \Omega$$

For circuit (b)

$$R_{ab} = 6 + 2 + [8 \parallel (7 + 5 \parallel 2.5 \parallel 7.5 \parallel 5 \parallel (9 + 6))] = 6 + 2 + 8 \parallel (7 + 1)$$

$$= 6 + 2 + 4 = 12 \Omega$$

For circuit (c)

$$144 \parallel (4 + 12) = 14.4 \Omega$$

$$14.4 + 5.6 = 20 \Omega$$

$$20 \parallel 12 = 7.5 \Omega$$

$$7.5 + 2.5 = 10 \Omega$$

$$10 \parallel 15 = 6 \Omega$$

$$14 + 6 + 10 = 30 \Omega$$

$$R_{ab} = 30 \parallel 60 = 20 \Omega$$

[b] $P_a = \frac{15^2}{3} = 75 \text{ W}$

$$P_b = \frac{48^2}{12} = 192 \text{ W}$$


$$P_c = 5^2(20) = 500 \text{ W}$$

P 3.8 [a] $p_{4\Omega} = i_s^2 4 = (12)^2 4 = 576 \text{ W}$ $p_{18\Omega} = (4)^2 18 = 288 \text{ W}$
 $p_{3\Omega} = (8)^2 3 = 192 \text{ W}$ $p_{6\Omega} = (8)^2 6 = 384 \text{ W}$

[b] $p_{120\text{V}}(\text{delivered}) = 120i_s = 120(12) = 1440 \text{ W}$

[c] $p_{\text{diss}} = 576 + 288 + 192 + 384 = 1440 \text{ W}$

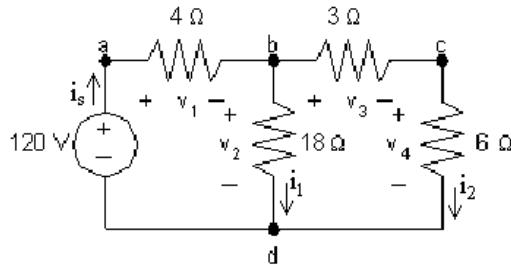P 3.9 [a] From Ex. 3-1: $i_1 = 4 \text{ A}$, $i_2 = 8 \text{ A}$, $i_s = 12 \text{ A}$
 at node b: $-12 + 4 + 8 = 0$, at node d: $12 - 4 - 8 = 0$



[b] $v_1 = 4i_s = 48 \text{ V}$ $v_3 = 3i_2 = 24 \text{ V}$
 $v_2 = 18i_1 = 72 \text{ V}$ $v_4 = 6i_2 = 48 \text{ V}$
 loop abda: $-120 + 48 + 72 = 0$,
 loop bcd b: $-72 + 24 + 48 = 0$,
 loop abcda: $-120 + 48 + 24 + 48 = 0$

P 3.10 $R_{\text{eq}} = 10 \parallel [6 + 5 \parallel (8 + 12)] = 10 \parallel (6 + 5 \parallel 20) = 10 \parallel (6 + 4) = 5 \Omega$


$v_{10\text{A}} = v_{10\Omega} = (10 \text{ A})(5 \Omega) = 50 \text{ V}$

Using voltage division:

$$v_{5\Omega} = \frac{5 \parallel (8 + 12)}{6 + 5 \parallel (8 + 12)} (50) = \frac{4}{6 + 4} (50) = 20 \text{ V}$$

Thus, $p_{5\Omega} = \frac{v_{5\Omega}^2}{5} = \frac{20^2}{5} = 80 \text{ W}$

P 3.11 [a]

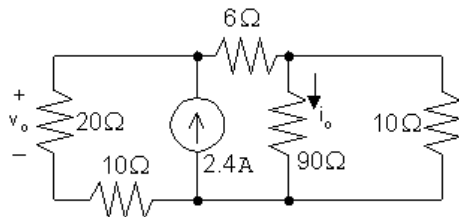

$R_{\text{eq}} = (10 + 20) \parallel [12 + (90 \parallel 10)] = 30 \parallel 15 = 10 \Omega$

$v_{2.4\text{A}} = 10(2.4) = 24 \text{ V}$

$$v_o = v_{20\Omega} = \frac{20}{10 + 20}(24) = 16 \text{ V}$$

$$v_{90\Omega} = \frac{90 \parallel 10}{6 + (90 \parallel 10)}(24) = \frac{9}{15}(24) = 14.4 \text{ V}$$

$$i_o = \frac{14.4}{90} = 0.16 \text{ A}$$

$$[\mathbf{b}] \quad p_{6\Omega} = \frac{(v_{2.4A} - v_{90\Omega})^2}{6} = \frac{(24 - 14.4)^2}{6} = 15.36 \text{ W}$$

$$[\mathbf{c}] \quad p_{2.4A} = -(2.4)(24) = -57.6 \text{ W}$$

Thus the power developed by the current source is 57.6 W.

P 3.12 [a] $R + R = 2R$

[b] $R + R + R + \cdots + R = nR$

[c] $R + R = 2R = 3000$ so $R = 1500 = 1.5 \text{ k}\Omega$

This is a resistor from Appendix H.

[d] $nR = 4000$; so if $n = 4$, $R = 1 \text{ k}\Omega$

This is a resistor from Appendix H.

P 3.13 [a] $R_{\text{eq}} = R \parallel R = \frac{R^2}{2R} = \frac{R}{2}$

[b] $R_{\text{eq}} = R \parallel R \parallel R \parallel \cdots \parallel R \quad (n \text{ R's})$
 $= R \parallel \frac{R}{n-1}$
 $= \frac{R^2/(n-1)}{R + R/(n-1)} = \frac{R^2}{nR} = \frac{R}{n}$

[c] $\frac{R}{2} = 5000$ so $R = 10 \text{ k}\Omega$
This is a resistor from Appendix H.

[d] $\frac{R}{n} = 4000$ so $R = 4000n$
If $n = 3$ $r = 4000(3) = 12 \text{ k}\Omega$
This is a resistor from Appendix H. So put three 12k resistors in parallel to get 4k Ω .

P 3.14 $4 = \frac{20R_2}{R_2 + 40}$ so $R_2 = 10 \Omega$

$$3 = \frac{20R_e}{40 + R_e} \quad \text{so} \quad R_e = \frac{120}{17} \Omega$$

Thus, $\frac{120}{17} = \frac{10R_L}{10 + R_L}$ so $R_L = 24 \Omega$

P 3.15 [a] $v_o = \frac{160(3300)}{(4700 + 3300)} = 66 \text{ V}$

[b] $i = 160/8000 = 20 \text{ mA}$

$$P_{R_1} = (400 \times 10^{-6})(4.7 \times 10^3) = 1.88 \text{ W}$$

$$P_{R_2} = (400 \times 10^{-6})(3.3 \times 10^3) = 1.32 \text{ W}$$

[c] Since R_1 and R_2 carry the same current and $R_1 > R_2$ to satisfy the voltage requirement, first pick R_1 to meet the 0.5 W specification

$$i_{R_1} = \frac{160 - 66}{R_1}, \quad \text{Therefore, } \left(\frac{94}{R_1}\right)^2 R_1 \leq 0.5$$

$$\text{Thus, } R_1 \geq \frac{94^2}{0.5} \quad \text{or} \quad R_1 \geq 17,672 \Omega$$

Now use the voltage specification:

$$\frac{R_2}{R_2 + 17,672}(160) = 66$$

$$\text{Thus, } R_2 = 12,408 \Omega$$

P 3.16 [a] $v_o = \frac{40R_2}{R_1 + R_2} = 8 \quad \text{so} \quad R_1 = 4R_2$

$$\text{Let } R_e = R_2 \parallel R_L = \frac{R_2 R_L}{R_2 + R_L}$$

$$v_o = \frac{40R_e}{R_1 + R_e} = 7.5 \quad \text{so} \quad R_1 = 4.33R_e$$

$$\text{Then, } 4R_2 = 4.33R_e = \frac{4.33(3600R_2)}{3600 + R_2}$$

$$\text{Thus, } R_2 = 300 \Omega \quad \text{and} \quad R_1 = 4(300) = 1200 \Omega$$

[b] The resistor that must dissipate the most power is R_1 , as it has the largest resistance and carries the same current as the parallel combination of R_2 and the load resistor. The power dissipated in R_1 will be maximum when the voltage across R_1 is maximum. This will occur when the voltage divider has a resistive load. Thus,

$$v_{R_1} = 40 - 7.5 = 32.5 \text{ V}$$

$$p_{R_1} = \frac{32.5^2}{1200} = 880.2 \text{ m W}$$

Thus the minimum power rating for all resistors should be 1 W.

- P 3.17 Refer to the solution to Problem 3.16. The voltage divider will reach the maximum power it can safely dissipate when the power dissipated in R_1 equals 1 W. Thus,

$$\frac{v_{R_1}^2}{1200} = 1 \quad \text{so} \quad v_{R_1} = 34.64 \text{ V}$$

$$v_o = 40 - 34.64 = 5.36 \text{ V}$$

$$\text{So, } \frac{40R_e}{1200 + R_e} = 5.36 \quad \text{and} \quad R_e = 185.68 \Omega$$

$$\text{Thus, } \frac{(300)R_L}{300 + R_L} = 185.68 \quad \text{and} \quad R_L = 487.26 \Omega$$

The minimum value for R_L from Appendix H is 560Ω .

- P 3.18 Begin by using the relationships among the branch currents to express all branch currents in terms of i_4 :

$$i_1 = 2i_2 = 2(2i_3) = 4(2i_4)$$

$$i_2 = 2i_3 = 2(2i_4)$$

$$i_3 = 2i_4$$

Now use KCL at the top node to relate the branch currents to the current supplied by the source.

$$i_1 + i_2 + i_3 + i_4 = 1 \text{ mA}$$

Express the branch currents in terms of i_4 and solve for i_4 :

$$1 \text{ mA} = 8i_4 + 4i_4 + 2i_4 + i_4 = 15i_4 \quad \text{so} \quad i_4 = \frac{0.001}{15} \text{ A}$$

Since the resistors are in parallel, the same voltage, 1 V appears across each of them. We know the current and the voltage for R_4 so we can use Ohm's law to calculate R_4 :

$$R_4 = \frac{v_g}{i_4} = \frac{1 \text{ V}}{(1/15) \text{ mA}} = 15 \text{ k}\Omega$$

Calculate i_3 from i_4 and use Ohm's law as above to find R_3 :

$$i_3 = 2i_4 = \frac{0.002}{15} \text{ A} \quad \therefore R_3 = \frac{v_g}{i_3} = \frac{1 \text{ V}}{(2/15) \text{ mA}} = 7.5 \text{ k}\Omega$$


Calculate i_2 from i_4 and use Ohm's law as above to find R_2 :

$$i_2 = 4i_4 = \frac{0.004}{15} \text{ A} \quad \therefore R_2 = \frac{v_g}{i_2} = \frac{1 \text{ V}}{(4/15) \text{ mA}} = 3750 \Omega$$


Calculate i_1 from i_4 and use Ohm's law as above to find R_1 :

$$i_1 = 8i_4 = \frac{0.008}{15} \text{ A} \quad \therefore R_1 = \frac{v_g}{i_1} = \frac{1 \text{ V}}{(8/15) \text{ mA}} = 1875 \Omega$$

The resulting circuit is shown below:

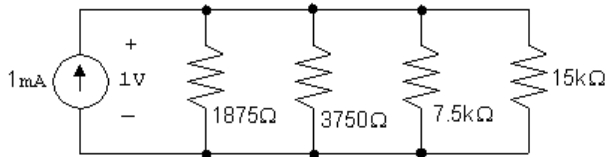

P 3.19 [a]

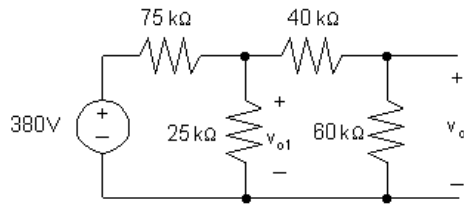


$$40 \text{ k}\Omega + 60 \text{ k}\Omega = 100 \text{ k}\Omega$$

$$25 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 20 \text{ k}\Omega$$

$$v_{o1} = \frac{20,000}{(75,000 + 20,000)}(380) = 80 \text{ V}$$

$$v_o = \frac{60,000}{(100,000)}(v_{o1}) = 48 \text{ V}$$

[b]

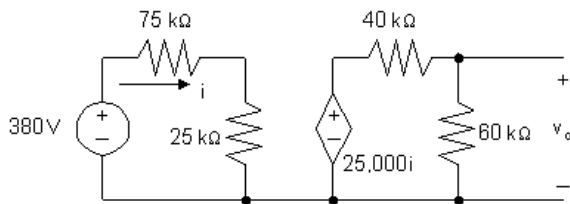

$$i = \frac{380}{100,000} = 3.8 \text{ mA}$$

$$25,000i = 95 \text{ V}$$

$$v_o = \frac{60,000}{100,000}(95) = 57 \text{ V}$$

[c] It removes loading effect of second voltage divider on the first voltage divider. Observe that the open circuit voltage of the first divider is

$$v'_{o1} = \frac{25,000}{(100,000)}(380) = 95 \text{ V}$$

Now note this is the input voltage to the second voltage divider when the current controlled voltage source is used.

$$\text{P 3.20} \quad \frac{(24)^2}{R_1 + R_2 + R_3} = 80, \quad \text{Therefore, } R_1 + R_2 + R_3 = 7.2 \Omega$$

$$\frac{(R_1 + R_2)24}{(R_1 + R_2 + R_3)} = 12$$

$$\text{Therefore, } 2(R_1 + R_2) = R_1 + R_2 + R_3$$

$$\text{Thus, } R_1 + R_2 = R_3; \quad 2R_3 = 7.2; \quad R_3 = 3.6 \Omega$$

$$\frac{R_2(24)}{R_1 + R_2 + R_3} = 5$$

$$4.8R_2 = R_1 + R_2 + 3.6 = 7.2$$

$$\text{Thus, } R_2 = 1.5 \Omega; \quad R_1 = 7.2 - R_2 - R_3 = 2.1 \Omega$$

P 3.21 [a] Let v_o be the voltage across the parallel branches, positive at the upper terminal, then

$$i_g = v_o G_1 + v_o G_2 + \cdots + v_o G_N = v_o (G_1 + G_2 + \cdots + G_N)$$

$$\text{It follows that } v_o = \frac{i_g}{(G_1 + G_2 + \cdots + G_N)}$$

The current in the k^{th} branch is $i_k = v_o G_k$; Thus,

$$i_k = \frac{i_g G_k}{[G_1 + G_2 + \cdots + G_N]}$$

$$\text{[b]} \quad i_5 = \frac{40(0.2)}{2 + 0.2 + 0.125 + 0.1 + 0.05 + 0.025} = 3.2 \text{ A}$$

$$\text{P 3.22 [a] At no load: } v_o = kv_s = \frac{R_2}{R_1 + R_2} v_s.$$

$$\text{At full load: } v_o = \alpha v_s = \frac{R_e}{R_1 + R_e} v_s, \quad \text{where } R_e = \frac{R_o R_2}{R_o + R_2}$$

$$\text{Therefore } k = \frac{R_2}{R_1 + R_2} \quad \text{and} \quad R_1 = \frac{(1-k)}{k}R_2$$

$$\alpha = \frac{R_e}{R_1 + R_e} \quad \text{and} \quad R_1 = \frac{(1-\alpha)}{\alpha}R_e$$

$$\text{Thus } \left(\frac{1-\alpha}{\alpha}\right) \left[\frac{R_2 R_o}{R_o + R_2}\right] = \frac{(1-k)}{k}R_2$$


$$\text{Solving for } R_2 \text{ yields } R_2 = \frac{(k-\alpha)}{\alpha(1-k)}R_o$$

$$\text{Also, } R_1 = \frac{(1-k)}{k}R_2 \quad \therefore \quad R_1 = \frac{(k-\alpha)}{\alpha k}R_o$$

[b] $R_1 = \left(\frac{0.05}{0.68}\right) R_o = 2.5 \text{ k}\Omega$

$R_2 = \left(\frac{0.05}{0.12}\right) R_o = 14.167 \text{ k}\Omega$

[c]

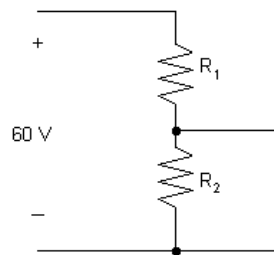


Maximum dissipation in R_2 occurs at no load, therefore,

$$P_{R_2(\max)} = \frac{[(60)(0.85)]^2}{14,167} = 183.6 \text{ mW}$$

Maximum dissipation in R_1 occurs at full load.

$$P_{R_1(\max)} = \frac{[60 - 0.80(60)]^2}{2500} = 57.60 \text{ mW}$$

[d]

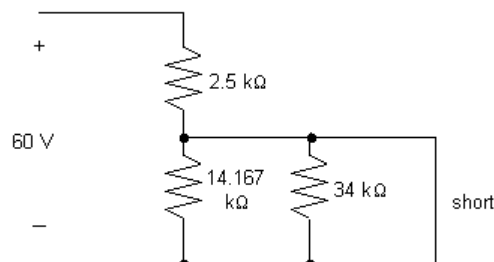

$$P_{R_1} = \frac{(60)^2}{2500} = 1.44 \text{ W} = 1440 \text{ mW}$$

$$P_{R_2} = \frac{(0)^2}{14,167} = 0 \text{ W}$$

P 3.23 [a] The equivalent resistance of the circuit to the right of the $18\ \Omega$ resistor is

$$100\|25\|[(40\|10) + 22] = 100\|25\|30 = 12\ \Omega$$

Thus by voltage division,

$$v_{18} = \frac{18}{18 + 12}(60) = 36\ \text{V}$$

[b] The current in the $18\ \Omega$ resistor can be found from its voltage using Ohm's law:

$$i_{18} = \frac{36}{18} = 2\ \text{A}$$

[c] The current in the $18\ \Omega$ resistor divides among three branches – one containing $100\ \Omega$, one containing $25\ \Omega$ and one containing $(22 + 40\|10) = 30\ \Omega$. Using current division,

$$i_{25} = \frac{100\|25\|30}{25}(i_{18}) = \frac{12}{25}(2) = 0.96\ \text{A}$$

[d] The voltage drop across the $25\ \Omega$ resistor can be found using Ohm's law:

$$v_{25} = 25i_{25} = 25(0.96) = 24\ \text{V}$$

[e] The voltage v_{25} divides across the $22\ \Omega$ resistor and the equivalent resistance $40\|10 = 8\ \Omega$. Using voltage division,

$$v_{10} = \frac{8}{8 + 22}(24) = 6.4\ \text{V}$$

P 3.24 [a] The equivalent resistance to the right of the $10\ \text{k}\Omega$ resistor is $5\ \text{k} + 2\ \text{k} + [9\ \text{k}\|18\ \text{k}\|6\ \text{k}] = 10\ \text{k}\Omega$. Therefore,

$$i_{10\text{k}} = \frac{10\ \text{k}\|10\ \text{k}}{10\ \text{k}}(0.050) = 25\ \text{mA}$$

[b] The voltage drop across the $10\ \text{k}\Omega$ resistor can be found using Ohm's law:

$$v_{10\text{k}} = (10,000)i_{10\text{k}} = (10,000)(0.025) = 250\ \text{V}$$

[c] The voltage $v_{10\text{k}}$ drops across the $5\ \text{k}\Omega$ resistor, the $2\ \text{k}\Omega$ resistor and the equivalent resistance of the $9\ \text{k}\Omega$, $18\ \text{k}\Omega$ and $6\ \text{k}\Omega$ resistors in parallel. Thus, using voltage division,

$$v_{6\text{k}} = \frac{2\ \text{k}}{5\ \text{k} + 2\ \text{k} + [9\ \text{k}\|18\ \text{k}\|6\ \text{k}]}(250) = \frac{2}{10}(250) = 50\ \text{V}$$

[d] The current through the $2\ \text{k}\Omega$ resistor can be found from its voltage using Ohm's law:

$$i_{2\text{k}} = \frac{v_{2\text{k}}}{2000} = \frac{50}{2000} = 25\ \text{mA}$$

[e] The current through the 2 k Ω resistor divides among the 9 k Ω , 18 k Ω , and 6 k Ω . Using current division,

$$i_{18\text{k}} = \frac{9\text{ k}\|18\text{ k}\|6\text{ k}}{18\text{ k}}(0.025) = \frac{3}{18}(0.025) = 4.167\text{ mA}$$

P 3.25 The equivalent resistance of the circuit to the right of the 90 Ω resistor is

$$R_{\text{eq}} = [(150\|75) + 40]\|(30 + 60) = 90\|90 = 45\ \Omega$$

Use voltage division to find the voltage drop between the top and bottom nodes:

$$v_{\text{Req}} = \frac{45}{45 + 90}(3) = 1\text{ V}$$

Use voltage division again to find v_1 from v_{Req} :

$$v_1 = \frac{150\|75}{150\|75 + 40}(1) = \frac{50}{90}(1) = \frac{5}{9}\text{ V}$$

Use voltage division one more time to find v_2 from v_{Req} :

$$v_2 = \frac{30}{30 + 60}(1) = \frac{1}{3}\text{ V}$$

P 3.26 $i_{10\text{k}} = \frac{(18)(15\text{ k})}{40\text{ k}} = 6.75\text{ mA}$

$$v_{15\text{k}} = -(6.75\text{ m})(15\text{ k}) = -101.25\text{ V}$$

$$i_{3\text{k}} = 18\text{ m} - 6.75\text{ m} = 11.25\text{ mA}$$

$$v_{12\text{k}} = -(12\text{ k})(11.25\text{ m}) = -135\text{ V}$$

$$v_o = -101.25 - (-135) = 33.75\text{ V}$$

P 3.27 [a] $v_{6\text{k}} = \frac{6}{6 + 2}(18) = 13.5\text{ V}$

$$v_{3\text{k}} = \frac{3}{3 + 9}(18) = 4.5\text{ V}$$

$$v_x = v_{6\text{k}} - v_{3\text{k}} = 13.5 - 4.5 = 9\text{ V}$$

$$[\mathbf{b}] \quad v_{6k} = \frac{6}{8}(V_s) = 0.75V_s$$

$$v_{3k} = \frac{3}{12}(V_s) = 0.25V_s$$

$$v_x = (0.75V_s) - (0.25V_s) = 0.5V_s$$

$$\text{P 3.28} \quad 5\Omega \parallel 20\Omega = 4\Omega; \quad 4\Omega + 6\Omega = 10\Omega; \quad 10\Omega \parallel (15 + 12 + 13) = 8\Omega;$$

$$\text{Therefore, } i_g = \frac{125}{2 + 8} = 12.5 \text{ A}$$

$$i_{6\Omega} = \frac{8}{6 + 4}(12.5) = 10 \text{ A}; \quad i_o = \frac{5 \parallel 20}{20}(10) = 2 \text{ A}$$

P 3.29 [a] The equivalent resistance seen by the voltage source is

$$60 \parallel [8 + 30 \parallel (4 + 80 \parallel 20)] = 60 \parallel [8 + 30 \parallel 20] = 60 \parallel 20 = 15\Omega$$

Thus,

$$i_g = \frac{300}{15} = 20 \text{ A}$$

[b] Use current division to find the current in the 8Ω division:

$$\frac{15}{20}(20) = 15 \text{ A}$$

Use current division again to find the current in the 30Ω resistor:

$$i_{30} = \frac{12}{30}(15) = 6 \text{ A}$$

Thus,

$$p_{30} = (6)^2(30) = 1080 \text{ W}$$

P 3.30 [a] The voltage across the 9Ω resistor is $1(12 + 6) = 18 \text{ V}$.

The current in the 9Ω resistor is $18/9 = 2 \text{ A}$. The current in the 2Ω resistor is $1 + 2 = 3 \text{ A}$. Therefore, the voltage across the 24Ω resistor is $(2)(3) + 18 = 24 \text{ V}$.

The current in the 24Ω resistor is 1 A . The current in the 3Ω resistor is $1 + 2 + 1 = 4 \text{ A}$. Therefore, the voltage across the 72Ω resistor is $24 + 3(4) = 36 \text{ V}$.

The current in the 72Ω resistor is $36/72 = 0.5 \text{ A}$.

The $20\Omega \parallel 5\Omega$ resistors are equivalent to a 4Ω resistor. The current in this equivalent resistor is $0.5 + 1 + 3 = 4.5 \text{ A}$. Therefore the voltage across the 108Ω resistor is $36 + 4.5(4) = 54 \text{ V}$.

The current in the 108Ω resistor is $54/108 = 0.5 \text{ A}$. The current in the 1.2Ω resistor is $4.5 + 0.5 = 5 \text{ A}$. Therefore,

$$v_g = (1.2)(5) + 54 = 60 \text{ V}$$

[b] The current in the $20\ \Omega$ resistor is

$$i_{20} = \frac{(4.5)(4)}{20} = \frac{18}{20} = 0.9\ \text{A}$$

Thus, the power dissipated by the $20\ \Omega$ resistor is

$$p_{20} = (0.9)^2(20) = 16.2\ \text{W}$$

P 3.31 For all full-scale readings the total resistance is

$$R_V + R_{\text{movement}} = \frac{\text{full-scale reading}}{10^{-3}}$$

We can calculate the resistance of the movement as follows:

$$R_{\text{movement}} = \frac{20\ \text{mV}}{1\ \text{mA}} = 20\ \Omega$$

Therefore, $R_V = 1000 (\text{full-scale reading}) - 20$

$$\text{[a]} \quad R_V = 1000(50) - 20 = 49,980\ \Omega$$

$$\text{[b]} \quad R_V = 1000(5) - 20 = 4980\ \Omega$$

$$\text{[c]} \quad R_V = 1000(0.25) - 20 = 230\ \Omega$$

$$\text{[d]} \quad R_V = 1000(0.025) - 20 = 5\ \Omega$$

P 3.32 [a] $v_{\text{meas}} = (50 \times 10^{-3})[15 \parallel 45 \parallel (4980 + 20)] = 0.5612\ \text{V}$

$$\text{[b]} \quad v_{\text{true}} = (50 \times 10^{-3})(15 \parallel 45) = 0.5625\ \text{V}$$

$$\% \text{ error} = \left(\frac{0.5612}{0.5625} - 1 \right) \times 100 = -0.224\%$$

P 3.33 The measured value is $60 \parallel 20.1 = 15.05618\ \Omega$.

$$i_g = \frac{50}{(15.05618 + 10)} = 1.995526\ \text{A}; \quad i_{\text{meas}} = \frac{60}{80.1}(1.996) = 1.494768\ \text{A}$$

The true value is $60 \parallel 20 = 15\ \Omega$.

$$i_g = \frac{50}{(15 + 10)} = 2\ \text{A}; \quad i_{\text{true}} = \frac{60}{80}(2) = 1.5\ \text{A}$$

$$\% \text{error} = \left[\frac{1.494768}{1.5} - 1 \right] \times 100 = -0.34878\% \approx -0.35\%$$

P 3.34 Begin by using current division to find the actual value of the current i_o :

$$i_{\text{true}} = \frac{15}{15 + 45}(50 \text{ mA}) = 12.5 \text{ mA}$$

$$i_{\text{meas}} = \frac{15}{15 + 45 + 0.1}(50 \text{ mA}) = 12.4792 \text{ mA}$$

$$\% \text{ error} = \left[\frac{12.4792}{12.5} - 1 \right] 100 = -0.166389\% \approx -0.17\%$$

P 3.35 [a] The model of the ammeter is an ideal ammeter in parallel with a resistor whose resistance is given by

$$R_m = \frac{100 \text{ mV}}{2 \text{ mA}} = 50 \Omega.$$

We can calculate the current through the real meter using current division:

$$i_m = \frac{(25/12)}{50 + (25/12)}(i_{\text{meas}}) = \frac{25}{625}(i_{\text{meas}}) = \frac{1}{25}i_{\text{meas}}$$


[b] At full scale, $i_{\text{meas}} = 5 \text{ A}$ and $i_m = 2 \text{ mA}$ so $5 - 0.002 = 4998 \text{ mA}$ flows through the resistor R_A :

$$R_A = \frac{100 \text{ mV}}{4998 \text{ mA}} = \frac{100}{4998} \Omega$$

$$i_m = \frac{(100/4998)}{50 + (100/4998)}(i_{\text{meas}}) = \frac{1}{2500}(i_{\text{meas}})$$

[c] Yes

P 3.36

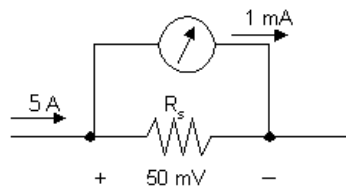


$$\text{Original meter: } R_e = \frac{50 \times 10^{-3}}{5} = 0.01 \Omega$$

$$\text{Modified meter: } R_e = \frac{(0.02)(0.01)}{0.03} = 0.00667 \Omega$$

$$\therefore (I_{\text{fs}})(0.00667) = 50 \times 10^{-3}$$

$$\therefore I_{\text{fs}} = 7.5 \text{ A}$$

P 3.37 [a]

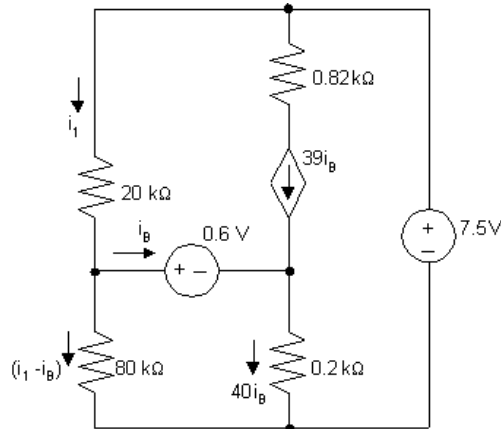

$$20 \times 10^3 i_1 + 80 \times 10^3 (i_1 - i_B) = 7.5$$

$$80 \times 10^3 (i_1 - i_B) = 0.6 + 40i_B(0.2 \times 10^3)$$

$$\therefore 100i_1 - 80i_B = 7.5 \times 10^{-3}$$

$$80i_1 - 88i_B = 0.6 \times 10^{-3}$$

Calculator solution yields $i_B = 225 \mu\text{A}$

[b] With the insertion of the ammeter the equations become

$$100i_1 - 80i_B = 7.5 \times 10^{-3} \quad (\text{no change})$$

$$80 \times 10^3 (i_1 - i_B) = 10^3 i_B + 0.6 + 40i_B(200)$$

$$80i_1 - 89i_B = 0.6 \times 10^{-3}$$

Calculator solution yields $i_B = 216 \mu\text{A}$

$$[\text{c}] \quad \% \text{ error} = \left(\frac{216}{225} - 1 \right) 100 = -4\%$$

P 3.38 The current in the shunt resistor at full-scale deflection is

$i_A = i_{\text{fullscale}} = 2 \times 10^{-3} \text{ A}$. The voltage across R_A at full-scale deflection is always 50 mV; therefore,

$$R_A = \frac{50 \times 10^{-3}}{i_{\text{fullscale}} - 2 \times 10^{-3}} = \frac{50}{1000i_{\text{fullscale}} - 2}$$

$$[\text{a}] \quad R_A = \frac{50}{10,000 - 2} = 5.001 \text{ m}\Omega$$

$$[\text{b}] \quad R_A = \frac{50}{1000 - 2} = 50.1 \text{ m}\Omega$$

$$[\text{c}] \quad R_A = \frac{50}{50 - 2} = 1.042 \text{ m}\Omega$$

$$[\mathbf{d}] \quad R_A = \frac{50}{2-2} = \infty \quad (\text{open circuit})$$

P 3.39 At full scale the voltage across the shunt resistor will be 50 mV; therefore the power dissipated will be

$$P_A = \frac{(50 \times 10^{-3})^2}{R_A}$$

$$\text{Therefore } R_A \geq \frac{(50 \times 10^{-3})^2}{0.5} = 5 \text{ m}\Omega$$

Otherwise the power dissipated in R_A will exceed its power rating of 0.5 W
When $R_A = 5 \text{ m}\Omega$, the shunt current will be

$$i_A = \frac{50 \times 10^{-3}}{5 \times 10^{-3}} = 10 \text{ A}$$

The measured current will be $i_{\text{meas}} = 10 + 0.001 = 10.001 \text{ A}$
 \therefore Full-scale reading for practical purposes is 10 A.

$$\text{P 3.40} \quad R_{\text{meter}} = R_m + R_{\text{movement}} = \frac{750 \text{ V}}{1.5 \text{ mA}} = 500 \text{ k}\Omega$$


$$v_{\text{meas}} = (25 \text{ k}\Omega \parallel 125 \text{ k}\Omega \parallel 50 \text{ k}\Omega)(30 \text{ mA}) = (20 \text{ k}\Omega)(30 \text{ mA}) = 600 \text{ V}$$

$$v_{\text{true}} = (25 \text{ k}\Omega \parallel 125 \text{ k}\Omega)(30 \text{ mA}) = (20.83 \text{ k}\Omega)(30 \text{ mA}) = 625 \text{ V}$$

$$\% \text{ error} = \left(\frac{600}{625} - 1 \right) 100 = -4\%$$

P 3.41 [a] Since the unknown voltage is greater than either voltmeter's maximum reading, the only possible way to use the voltmeters would be to connect them in series.

[b]

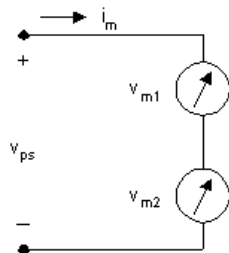

$$R_{m1} = (300)(900) = 270 \text{ k}\Omega; \quad R_{m2} = (150)(1200) = 180 \text{ k}\Omega$$

$$\therefore R_{m1} + R_{m2} = 450 \text{ k}\Omega$$

$$i_{1 \max} = \frac{300}{270} \times 10^{-3} = 1.11 \text{ mA}; \quad i_{2 \max} = \frac{150}{180} \times 10^{-3} = 0.833 \text{ mA}$$

$\therefore i_{\max} = 0.833 \text{ mA}$ since meters are in series

$$v_{\max} = (0.833 \times 10^{-3})(270 + 180)10^3 = 375 \text{ V}$$

Thus the meters can be used to measure the voltage.

$$[\text{c}] \quad i_m = \frac{320}{450 \times 10^3} = 0.711 \text{ mA}$$

$$v_{m1} = (0.711)(270) = 192 \text{ V}; \quad v_{m2} = (0.711)(180) = 128 \text{ V}$$

P 3.42 The current in the series-connected voltmeters is

$$i_m = \frac{205.2}{270,000} = \frac{136.8}{180,000} = 0.76 \text{ mA}$$

$$v_{50 \text{ k}\Omega} = (0.76 \times 10^{-3})(50,000) = 38 \text{ V}$$

$$V_{\text{power supply}} = 205.2 + 136.8 + 38 = 380 \text{ V}$$

P 3.43 [a] $v_{\text{meter}} = 180 \text{ V}$

$$[\text{b}] \quad R_{\text{meter}} = (100)(200) = 20 \text{ k}\Omega$$

$$20 \parallel 70 = 15.555556 \text{ k}\Omega$$

$$v_{\text{meter}} = \frac{180}{35.555556} \times 15.555556 = 78.75 \text{ V}$$

$$[\text{c}] \quad 20 \parallel 20 = 10 \text{ k}\Omega$$

$$v_{\text{meter}} = \frac{180}{80}(10) = 22.5 \text{ V}$$

$$[\text{d}] \quad v_{\text{meter a}} = 180 \text{ V}$$

$$v_{\text{meter b}} + v_{\text{meter c}} = 101.26 \text{ V}$$

No, because of the loading effect.

P 3.44 From the problem statement we have

$$50 = \frac{V_s(10)}{10 + R_s} \quad (1) \quad V_s \text{ in mV}; R_s \text{ in M}\Omega$$

$$48.75 = \frac{V_s(6)}{6 + R_s} \quad (2)$$

[a] From Eq (1) $10 + R_s = 0.2V_s$

$$\therefore R_s = 0.2V_s - 10$$

Substituting into Eq (2) yields

$$48.75 = \frac{6V_s}{0.2V_s - 4} \quad \text{or} \quad V_s = 52 \text{ mV}$$

[b] From Eq (1)

$$50 = \frac{520}{10 + R_s} \quad \text{or} \quad 50R_s = 20$$

$$\text{So } R_s = 400 \text{ k}\Omega$$

P 3.45 [a] $R_1 = (100/2)10^3 = 50 \text{ k}\Omega$

$$R_2 = (10/2)10^3 = 5 \text{ k}\Omega$$

$$R_3 = (1/2)10^3 = 500 \Omega$$

[b] Let $i_a =$ actual current in the movement

$$i_d = \text{design current in the movement}$$

$$\text{Then \% error} = \left(\frac{i_a}{i_d} - 1 \right) 100$$

For the 100 V scale:

$$i_a = \frac{100}{50,000 + 25} = \frac{100}{50,025}, \quad i_d = \frac{100}{50,000}$$

$$\frac{i_a}{i_d} = \frac{50,000}{50,025} = 0.9995 \quad \% \text{ error} = (0.9995 - 1)100 = -0.05\%$$

For the 10 V scale:

$$\frac{i_a}{i_d} = \frac{5000}{5025} = 0.995 \quad \% \text{ error} = (0.995 - 1.0)100 = -0.4975\%$$

For the 1 V scale:

$$\frac{i_a}{i_d} = \frac{500}{525} = 0.9524 \quad \% \text{ error} = (0.9524 - 1.0)100 = -4.76\%$$

P 3.46 [a] $R_{\text{movement}} = 50 \Omega$


$$R_1 + R_{\text{movement}} = \frac{30}{1 \times 10^{-3}} = 30 \text{ k}\Omega \quad \therefore R_1 = 29,950 \Omega$$

$$R_2 + R_1 + R_{\text{movement}} = \frac{150}{1 \times 10^{-3}} = 150 \text{ k}\Omega \quad \therefore R_2 = 120 \text{ k}\Omega$$

$$R_3 + R_2 + R_1 + R_{\text{movement}} = \frac{300}{1 \times 10^{-3}} = 300 \text{ k}\Omega$$

$$\therefore R_3 = 150 \text{ k}\Omega$$

[b]

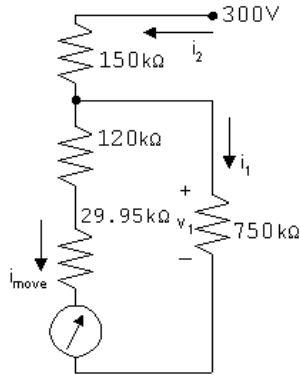

$$v_1 = (0.96 \text{ m})(150 \text{ k}) = 144 \text{ V}$$

$$i_{\text{move}} = \frac{144}{120 + 29.95 + 0.05} = 0.96 \text{ mA}$$

$$i_1 = \frac{144}{750 \text{ k}} = 0.192 \text{ mA}$$

$$i_2 = i_{\text{move}} + i_1 = 0.96 \text{ m} + 0.192 \text{ m} = 1.152 \text{ mA}$$

$$v_{\text{meas}} = v_x = 144 + 150i_2 = 316.8 \text{ V}$$

[c] $v_1 = 150 \text{ V}; \quad i_2 = 1 \text{ m} + 0.20 \text{ m} = 1.20 \text{ mA}$

$$i_1 = 150/750,000 = 0.20 \text{ mA}$$

$$\therefore v_{\text{meas}} = v_x = 150 + (150 \text{ k})(1.20 \text{ m}) = 330 \text{ V}$$

P 3.47 [a] $R_{\text{meter}} = 300 \text{ k}\Omega + 600 \text{ k}\Omega \parallel 200 \text{ k}\Omega = 450 \text{ k}\Omega$

$$450 \parallel 360 = 200 \text{ k}\Omega$$


$$V_{\text{meter}} = \frac{200}{240}(600) = 500 \text{ V}$$

[b] What is the percent error in the measured voltage?

$$\text{True value} = \frac{360}{400}(600) = 540 \text{ V}$$

$$\% \text{ error} = \left(\frac{500}{540} - 1 \right) 100 = -7.41\%$$

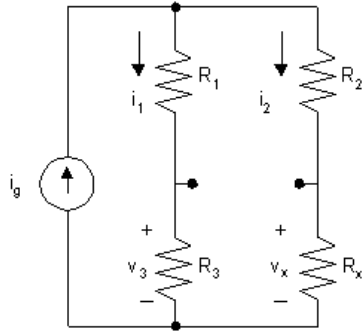- P 3.48 Since the bridge is balanced, we can remove the detector without disturbing the voltages and currents in the circuit.



It follows that

$$i_1 = \frac{i_g(R_2 + R_x)}{R_1 + R_2 + R_3 + R_x} = \frac{i_g(R_2 + R_x)}{\sum R}$$

$$i_2 = \frac{i_g(R_1 + R_3)}{R_1 + R_2 + R_3 + R_x} = \frac{i_g(R_1 + R_3)}{\sum R}$$

$$v_3 = R_3 i_1 = v_x = i_2 R_x$$

$$\therefore \frac{R_3 i_g (R_2 + R_x)}{\sum R} = \frac{R_x i_g (R_1 + R_3)}{\sum R}$$

$$\therefore R_3 (R_2 + R_x) = R_x (R_1 + R_3)$$

$$\text{From which } R_x = \frac{R_2 R_3}{R_1}$$

- P 3.49 Note the bridge structure is balanced, that is $15 \times 5 = 3 \times 25$, hence there is no current in the $5 \text{ k}\Omega$ resistor. It follows that the equivalent resistance of the circuit is

$$R_{\text{eq}} = 750 + (15,000 + 3000) \parallel (25,000 + 5000) = 750 + 11,250 = 12 \text{ k}\Omega$$


The source current is $192/12,000 = 16 \text{ mA}$.

The current down through the branch containing the $15 \text{ k}\Omega$ and $3 \text{ k}\Omega$ resistors is

$$i_{3\text{k}} = \frac{11,250}{18,000} (0.016) = 10 \text{ mA}$$

$$\therefore p_{3\text{k}} = 3000(0.01)^2 = 0.3 \text{ W}$$

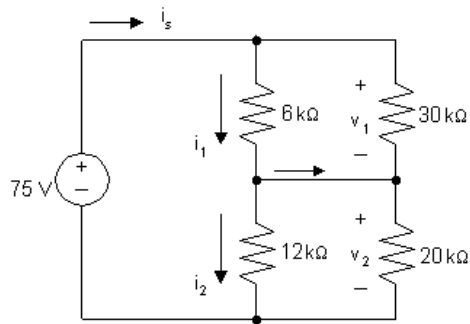P 3.50 Redraw the circuit, replacing the detector branch with a short circuit.



$$6 \text{ k}\Omega \parallel 30 \text{ k}\Omega = 5 \text{ k}\Omega$$

$$12 \text{ k}\Omega \parallel 20 \text{ k}\Omega = 7.5 \text{ k}\Omega$$

$$i_s = \frac{75}{12,500} = 6 \text{ mA}$$

$$v_1 = 0.006(5000) = 30 \text{ V}$$


$$v_2 = 0.006(7500) = 45 \text{ V}$$

$$i_1 = \frac{30}{6000} = 5 \text{ mA}$$

$$i_2 = \frac{45}{12,000} = 3.75 \text{ mA}$$

$$i_d = i_1 - i_2 = 1.25 \text{ mA}$$

P 3.51 [a]

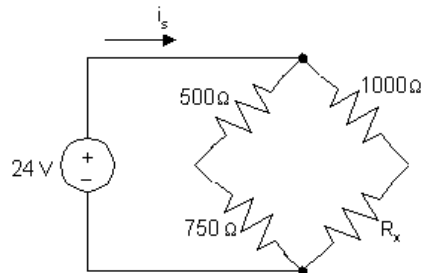

The condition for a balanced bridge is that the product of the opposite resistors must be equal:

$$(500)(R_x) = (1000)(750) \quad \text{so} \quad R_x = \frac{(1000)(750)}{500} = 1500 \Omega$$

- [b] The source current is the sum of the two branch currents. Each branch current can be determined using Ohm's law, since the resistors in each branch are in series and the voltage drop across each branch is 24 V:

$$i_s = \frac{24 \text{ V}}{500 \Omega + 750 \Omega} + \frac{24 \text{ V}}{1000 \Omega + 1500 \Omega} = 28.8 \text{ mA}$$

- [c] We can use Ohm's law to find the current in each branch:

$$i_{\text{left}} = \frac{24}{500 + 750} = 19.2 \text{ mA}$$

$$i_{\text{right}} = \frac{24}{1000 + 1500} = 9.6 \text{ mA}$$

Now we can use the formula $p = Ri^2$ to find the power dissipated by each resistor:

$$p_{500} = (500)(0.0192)^2 = 184.32 \text{ mW} \quad p_{750} = (750)(0.0192)^2 = 276.18 \text{ mW}$$


$$p_{1000} = (1000)(0.0096)^2 = 92.16 \text{ mW} \quad p_{1500} = (1500)(0.0096)^2 = 138.24 \text{ mW}$$

Thus, the 750Ω resistor absorbs the most power; it absorbs 276.48 mW of power.

- [d] From the analysis in part (c), the 1000Ω resistor absorbs the least power; it absorbs 92.16 mW of power.

P 3.52 In order that all four decades (1, 10, 100, 1000) that are used to set R_3 contribute to the balance of the bridge, the ratio R_2/R_1 should be set to 0.001.

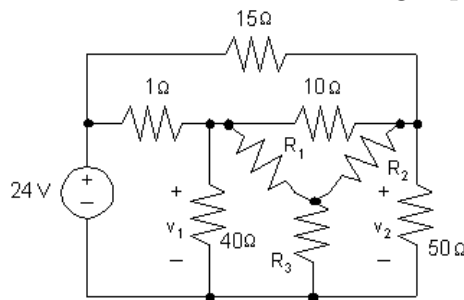
P 3.53 Begin by transforming the Δ -connected resistors (10Ω , 40Ω , 50Ω) to Y-connected resistors. Both the Y-connected and Δ -connected resistors are shown below to assist in using Eqs. 3.44 – 3.46:



Now use Eqs. 3.44 – 3.46 to calculate the values of the Y-connected resistors:

$$R_1 = \frac{(40)(10)}{10 + 40 + 50} = 4 \Omega; \quad R_2 = \frac{(10)(50)}{10 + 40 + 50} = 5 \Omega; \quad R_3 = \frac{(40)(50)}{10 + 40 + 50} = 20 \Omega$$

The transformed circuit is shown below:

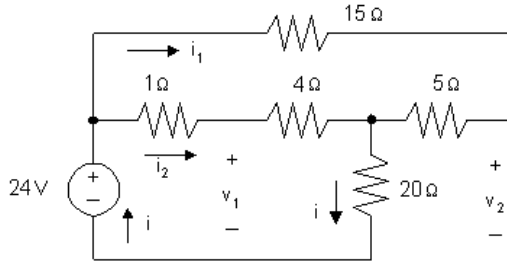

The equivalent resistance seen by the 24 V source can be calculated by making series and parallel combinations of the resistors to the right of the 24 V source:

$$R_{\text{eq}} = (15 + 5) \parallel (1 + 4) + 20 = 20 \parallel 5 + 20 = 4 + 20 = 24 \Omega$$

Therefore, the current i in the 24 V source is given by

$$i = \frac{24 \text{ V}}{24 \Omega} = 1 \text{ A}$$

Use current division to calculate the currents i_1 and i_2 . Note that the current i_1 flows in the branch containing the 15Ω and 5Ω series connected resistors, while the current i_2 flows in the parallel branch that contains the series connection of the 1Ω and 4Ω resistors:

$$i_1 = \frac{4}{15 + 5}(i) = \frac{4}{20}(1 \text{ A}) = 0.2 \text{ A}, \quad \text{and} \quad i_2 = 1 \text{ A} - 0.2 \text{ A} = 0.8 \text{ A}$$


Now use KVL and Ohm's law to calculate v_1 . Note that v_1 is the sum of the voltage drop across the 4Ω resistor, $4i_2$, and the voltage drop across the 20Ω resistor, $20i$:

$$v_1 = 4i_2 + 20i = 4(0.8 \text{ A}) + 20(1 \text{ A}) = 3.2 + 20 = 23.2 \text{ V}$$


Finally, use KVL and Ohm's law to calculate v_2 . Note that v_2 is the sum of the voltage drop across the 5Ω resistor, $5i_1$, and the voltage drop across the 20Ω resistor, $20i$:

$$v_2 = 5i_1 + 20i = 5(0.2 \text{ A}) + 20(1 \text{ A}) = 1 + 20 = 21 \text{ V}$$

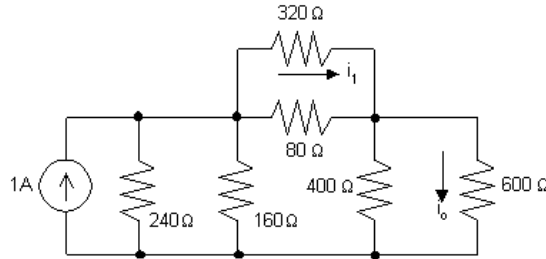P 3.54 [a] After the $20\ \Omega$ — $100\ \Omega$ — $50\ \Omega$ wye is replaced by its equivalent delta, the circuit reduces to



Now the circuit can be reduced to

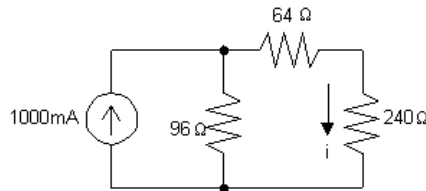


$$i = \frac{96}{400}(1000) = 240\ \text{mA}$$

$$i_o = \frac{400}{1000}(240) = 96\ \text{mA}$$

[b] $i_1 = \frac{80}{400}(240) = 48\ \text{mA}$

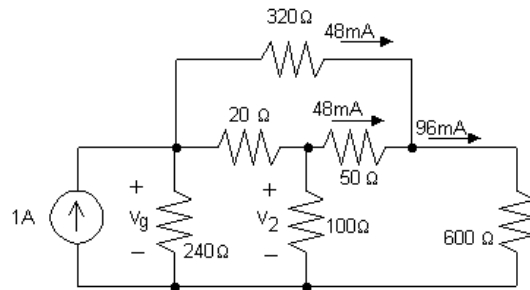[c] Now that i_o and i_1 are known return to the original circuit



$$v_2 = (50)(0.048) + (600)(0.096) = 60\ \text{V}$$

$$i_2 = \frac{v_2}{100} = \frac{60}{100} = 600\ \text{mA}$$

[d] $v_g = v_2 + 20(0.6 + 0.048) = 60 + 12.96 = 72.96\ \text{V}$


$$p_g = -(v_g)(1) = -72.96\ \text{W}$$

Thus the current source delivers 72.96 W.

P 3.55 The top of the pyramid can be replaced by a resistor equal to

$$R_1 = \frac{(18)(9)}{27} = 6\ \text{k}\Omega$$

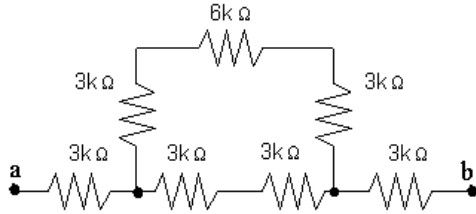The lower left and right deltas can be replaced by wyes. Each resistance in the wye equals 3 k Ω . Thus our circuit can be reduced to



Now the 12 k Ω in parallel with 6 k Ω reduces to 4 k Ω .


$$\therefore R_{ab} = 3 \text{ k} + 4 \text{ k} + 3 \text{ k} = 10 \text{ k}\Omega$$

- P 3.56 [a] Calculate the values of the Y-connected resistors that are equivalent to the 10 Ω , 40 Ω , and 50 Ω Δ -connected resistors:

$$R_X = \frac{(10)(50)}{10 + 40 + 50} = 5 \Omega; \quad R_Y = \frac{(50)(40)}{10 + 40 + 50} = 20 \Omega;$$

$$R_Z = \frac{(10)(40)}{10 + 40 + 50} = 4 \Omega$$

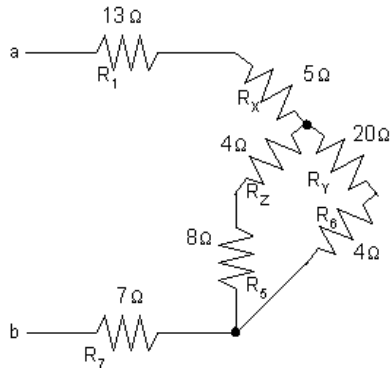Replacing the R_2 — R_3 — R_4 delta with its equivalent Y gives



Now calculate the equivalent resistance R_{ab} by making series and parallel combinations of the resistors:

$$R_{ab} = 13 + 5 + [(8 + 4) \parallel (20 + 4)] + 7 = 33 \Omega$$


- [b] Calculate the values of the Δ -connected resistors that are equivalent to the 10 Ω , 8 Ω , and 40 Ω Y-connected resistors:

$$R_X = \frac{(10)(8) + (8)(40) + (10)(40)}{8} = \frac{800}{8} = 100 \Omega$$

$$R_Y = \frac{(10)(8) + (8)(40) + (10)(40)}{10} = \frac{800}{10} = 80 \Omega$$

$$R_Z = \frac{(10)(8) + (8)(40) + (10)(40)}{40} = \frac{800}{40} = 20 \Omega$$

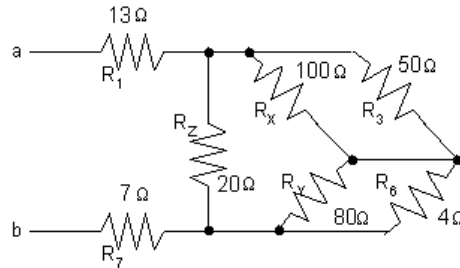Replacing the R_2, R_4, R_5 wye with its equivalent Δ gives



Make series and parallel combinations of the resistors to find the equivalent resistance R_{ab} :

$$100\ \Omega \parallel 50\ \Omega = 33.33\ \Omega; \quad 80\ \Omega \parallel 4\ \Omega = 3.81\ \Omega$$

$$\therefore 20 \parallel (33.33 + 3.81) = 13\ \Omega$$

$$\therefore R_{ab} = 13 + 13 + 7 = 33\ \Omega$$

- [c] Convert the delta connection R_4 — R_5 — R_6 to its equivalent wye.
Convert the wye connection R_3 — R_4 — R_6 to its equivalent delta.

P 3.57 [a] Convert the upper delta to a wye.

$$R_1 = \frac{(50)(50)}{200} = 12.5\ \Omega$$

$$R_2 = \frac{(50)(100)}{200} = 25\ \Omega$$

$$R_3 = \frac{(100)(50)}{200} = 25\ \Omega$$


Convert the lower delta to a wye.

$$R_4 = \frac{(60)(80)}{200} = 24\ \Omega$$

$$R_5 = \frac{(60)(60)}{200} = 18\ \Omega$$

$$R_6 = \frac{(80)(60)}{200} = 24\ \Omega$$

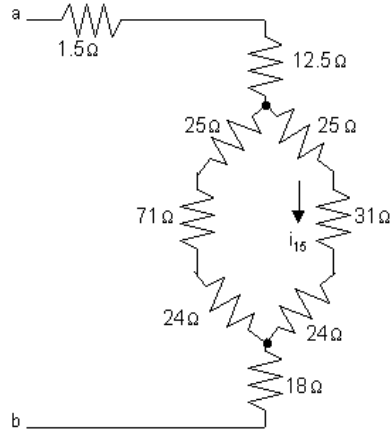Now redraw the circuit using the wye equivalents.



$$R_{ab} = 1.5 + 12.5 + \frac{(120)(80)}{200} + 18 = 14 + 48 + 18 = 80 \Omega$$

[b] When $v_{ab} = 400$ V

$$i_g = \frac{400}{80} = 5 \text{ A}$$

$$i_{31\Omega} = \frac{48}{80}(5) = 3 \text{ A}$$


$$p_{31\Omega} = (31)(3)^2 = 279 \text{ W}$$

P 3.58 Replace the upper and lower deltas with the equivalent wyes:

$$R_{1U} = \frac{(10)(50)}{100} = 5 \Omega; R_{2U} = \frac{(50)(40)}{100} = 20 \Omega; R_{3U} = \frac{(10)(40)}{100} = 4 \Omega$$

$$R_{1L} = \frac{(10)(60)}{100} = 6 \Omega; R_{2L} = \frac{(60)(30)}{100} = 18 \Omega; R_{3L} = \frac{(10)(30)}{100} = 3 \Omega$$

The resulting circuit is shown below:

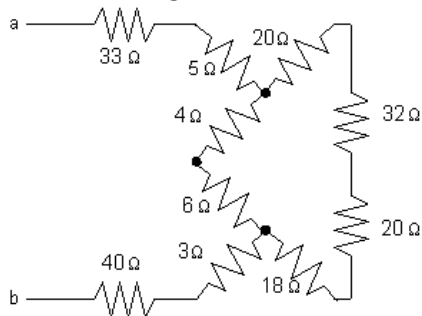

Now make series and parallel combinations of the resistors:

$$(4 + 6) \parallel (20 + 32 + 20 + 18) = 10 \parallel 90 = 9 \Omega$$

$$R_{ab} = 33 + 5 + 9 + 3 + 40 = 90 \Omega$$

P 3.59 $8 + 12 = 20 \Omega$

$$20 \parallel 60 = 15 \Omega$$

$$15 + 20 = 35 \Omega$$

$$35 \parallel 140 = 28 \Omega$$

$$28 + 22 = 50 \Omega$$

$$50 \parallel 75 = 30 \Omega$$

$$30 + 10 = 40 \Omega$$


$$i_g = 240/40 = 6 \text{ A}$$

$$i_o = (6)(50)/125 = 2.4 \text{ A}$$

$$i_{140\Omega} = (6 - 2.4)(35)/175 = 0.72 \text{ A}$$

$$p_{140\Omega} = (0.72)^2(140) = 72.576 \text{ W}$$

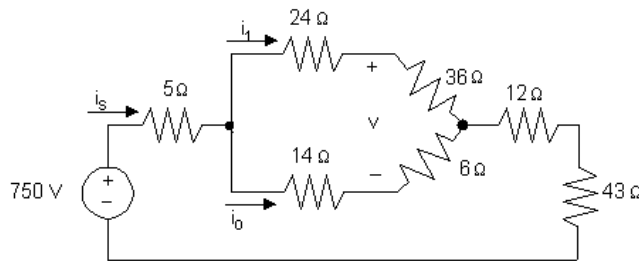P 3.60 [a] Replace the 60—120—20 Ω delta with a wye equivalent to get



$$i_s = \frac{750}{5 + (24 + 36) \parallel (14 + 6) + 12 + 43} = \frac{750}{75} = 10 \text{ A}$$

$$i_1 = \frac{(24 + 36) \parallel (14 + 6)}{24 + 36} (10) = \frac{15}{60} (10) = 2.5 \text{ A}$$


[b] $i_o = 10 - 2.5 = 7.5 \text{ A}$

$$v = 36i_1 - 6i_o = 36(2.5) - 6(7.5) = 45 \text{ V}$$


[c] $i_2 = i_o + \frac{v}{60} = 7.5 + \frac{45}{60} = 8.25 \text{ A}$

[d] $P_{\text{supplied}} = (750)(10) = 7500 \text{ W}$

P 3.61

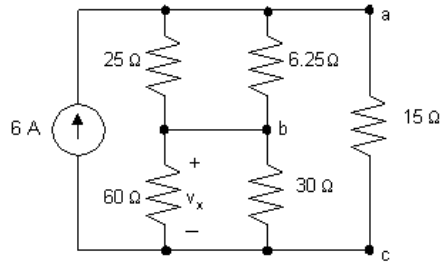
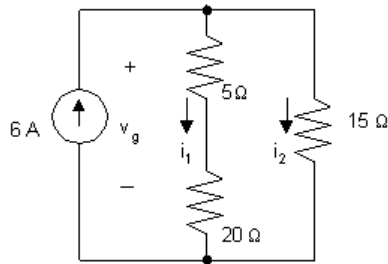
$$25 \parallel 6.25 = 5 \Omega \quad 60 \parallel 30 = 20 \Omega$$



$$i_1 = \frac{(6)(15)}{(40)} = 2.25 \text{ A}; \quad v_x = 20i_1 = 45 \text{ V}$$

$$v_g = 25i_1 = 56.25 \text{ V}$$

$$v_{6.25} = v_g - v_x = 11.25 \text{ V}$$

$$P_{\text{device}} = \frac{11.25^2}{6.25} + \frac{45^2}{30} + \frac{56.25^2}{15} = 298.6875 \text{ W}$$

P 3.62 [a] Subtracting Eq. 3.42 from Eq. 3.43 gives

$$R_1 - R_2 = (R_c R_b - R_c R_a) / (R_a + R_b + R_c).$$

Adding this expression to Eq. 3.41 and solving for R_1 gives

$$R_1 = R_c R_b / (R_a + R_b + R_c).$$

To find R_2 , subtract Eq. 3.43 from Eq. 3.41 and add this result to Eq. 3.42. To find R_3 , subtract Eq. 3.41 from Eq. 3.42 and add this result to Eq. 3.43.

[b] Using the hint, Eq. 3.43 becomes

$$R_1 + R_3 = \frac{R_b [(R_2/R_3)R_b + (R_2/R_1)R_b]}{(R_2/R_1)R_b + R_b + (R_2/R_3)R_b} = \frac{R_b (R_1 + R_3) R_2}{(R_1 R_2 + R_2 R_3 + R_3 R_1)}$$

Solving for R_b gives $R_b = (R_1 R_2 + R_2 R_3 + R_3 R_1) / R_2$. To find R_a : First use Eqs. 3.44–3.46 to obtain the ratios $(R_1/R_3) = (R_c/R_a)$ or

$R_c = (R_1/R_3)R_a$ and $(R_1/R_2) = (R_b/R_a)$ or $R_b = (R_1/R_2)R_a$. Now use these relationships to eliminate R_b and R_c from Eq. 3.42. To find R_c , use Eqs. 3.44–3.46 to obtain the ratios $R_b = (R_3/R_2)R_c$ and $R_a = (R_3/R_1)R_c$. Now use the relationships to eliminate R_b and R_a from Eq. 3.41.

$$\begin{aligned} \text{P 3.63} \quad G_a &= \frac{1}{R_a} = \frac{R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1} \\ &= \frac{1/G_1}{(1/G_1)(1/G_2) + (1/G_2)(1/G_3) + (1/G_3)(1/G_1)} \\ &= \frac{(1/G_1)(G_1 G_2 G_3)}{G_1 + G_2 + G_3} = \frac{G_2 G_3}{G_1 + G_2 + G_3} \end{aligned}$$

Similar manipulations generate the expressions for G_b and G_c .

$$\text{P 3.64} \quad [\text{a}] \quad R_{ab} = 2R_1 + \frac{R_2(2R_1 + R_L)}{2R_1 + R_2 + R_L} = R_L$$

$$\text{Therefore} \quad 2R_1 - R_L + \frac{R_2(2R_1 + R_L)}{2R_1 + R_2 + R_L} = 0$$

$$\text{Thus} \quad R_L^2 = 4R_1^2 + 4R_1 R_2 = 4R_1(R_1 + R_2)$$

When $R_{ab} = R_L$, the current into terminal a of the attenuator will be v_i/R_L

Using current division, the current in the R_L branch will be

$$\frac{v_i}{R_L} \cdot \frac{R_2}{2R_1 + R_2 + R_L}$$

$$\text{Therefore} \quad v_o = \frac{v_i}{R_L} \cdot \frac{R_2}{2R_1 + R_2 + R_L} R_L$$

$$\text{and} \quad \frac{v_o}{v_i} = \frac{R_2}{2R_1 + R_2 + R_L}$$

$$[\text{b}] \quad (600)^2 = 4(R_1 + R_2)R_1$$

$$9 \times 10^4 = R_1^2 + R_1 R_2$$

$$\frac{v_o}{v_i} = 0.6 = \frac{R_2}{2R_1 + R_2 + 600}$$

$$\therefore 1.2R_1 + 0.6R_2 + 360 = R_2$$

$$0.4R_2 = 1.2R_1 + 360$$

$$R_2 = 3R_1 + 900$$

$$\therefore 9 \times 10^4 = R_1^2 + R_1(3R_1 + 900) = 4R_1^2 + 900R_1$$

$$\therefore R_1^2 + 225R_1 - 22,500 = 0$$

$$R_1 = -112.5 \pm \sqrt{(112.5)^2 + 22,500} = -112.5 \pm 187.5$$

$$\therefore R_1 = 75 \Omega$$

$$\therefore R_2 = 3(75) + 900 = 1125 \Omega$$

[c] From Appendix H, choose $R_1 = 68 \Omega$ and $R_2 = 1.2 \text{ k}\Omega$. For these values,


$$R_{ab} = R_L = \sqrt{(4)(68)(68 + 1200)} = 587.3 \Omega$$

$$\% \text{ error} = \left(\frac{587.3}{600} - 1 \right) 100 = -2.1\%$$


$$\frac{v_o}{v_i} = \frac{1200}{2(68) + 1200 + 587.3} = 0.624$$

$$\% \text{ error} = \left(\frac{0.624}{0.6} - 1 \right) 100 = 4\%$$

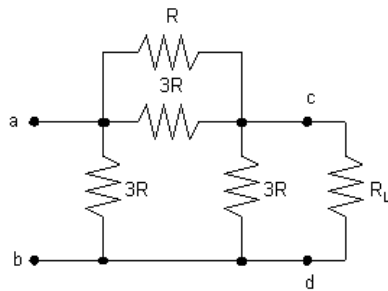P 3.65 [a] After making the Y-to- Δ transformation, the circuit reduces to



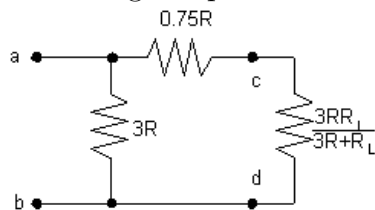Combining the parallel resistors reduces the circuit to




$$\text{Now note: } 0.75R + \frac{3RR_L}{3R + R_L} = \frac{2.25R^2 + 3.75RR_L}{3R + R_L}$$

$$\text{Therefore } R_{ab} = \frac{3R \left(\frac{2.25R^2 + 3.75RR_L}{3R + R_L} \right)}{3R + \left(\frac{2.25R^2 + 3.75RR_L}{3R + R_L} \right)} = \frac{3R(3R + 5R_L)}{15R + 9R_L}$$

$$\text{If } R = R_L, \text{ we have } R_{ab} = \frac{3R_L(8R_L)}{24R_L} = R_L$$

$$\text{Therefore } R_{ab} = R_L$$

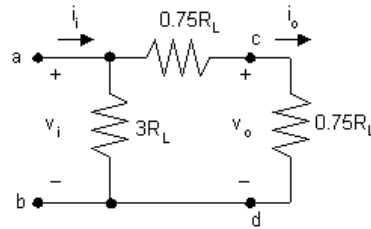[b] When $R = R_L$, the circuit reduces to



$$i_o = \frac{i_i(3R_L)}{4.5R_L} = \frac{1}{1.5}i_i = \frac{1}{1.5} \frac{v_i}{R_L}, \quad v_o = 0.75R_L i_o = \frac{1}{2}v_i,$$

$$\text{Therefore } \frac{v_o}{v_i} = 0.5$$


P 3.66 [a] $3.5(3R - R_L) = 3R + R_L$

$$10.5R - 1050 = 3R + 300$$

$$7.5R = 1350, \quad R = 180 \Omega$$

$$R_2 = \frac{2(180)(300)^2}{3(180)^2 - (300)^2} = 4500 \Omega$$

[b]

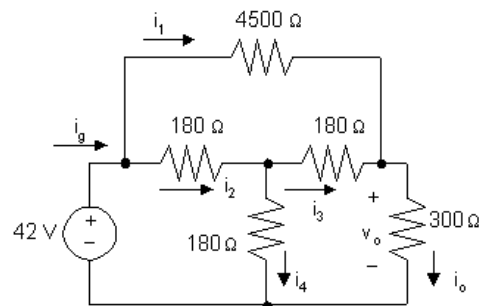

$$v_o = \frac{v_i}{3.5} = \frac{42}{3.5} = 12 \text{ V}$$

$$i_o = \frac{12}{300} = 40 \text{ mA}$$

$$i_1 = \frac{42 - 12}{4500} = \frac{30}{4500} = 6.67 \text{ mA}$$

$$i_g = \frac{42}{300} = 140 \text{ mA}$$

$$i_2 = 140 - 6.67 = 133.33 \text{ mA}$$

$$i_3 = 40 - 6.67 = 33.33 \text{ mA}$$

$$i_4 = 133.33 - 33.33 = 100 \text{ mA}$$

$$p_{4500 \text{ top}} = (6.67 \times 10^{-3})^2(4500) = 0.2 \text{ W}$$

$$p_{180 \text{ left}} = (133.33 \times 10^{-3})^2(180) = 3.2 \text{ W}$$

$$p_{180 \text{ right}} = (33.33 \times 10^{-3})^2(180) = 0.2 \text{ W}$$

$$p_{180 \text{ vertical}} = (100 \times 10^{-3})^2(180) = 0.48 \text{ W}$$

$$p_{300 \text{ load}} = (40 \times 10^{-3})^2(300) = 0.48 \text{ W}$$


The 180 Ω resistor carrying i_2

[c] $p_{180 \text{ left}} = 3.2 \text{ W}$

[d] Two resistors dissipate minimum power – the 4500 Ω resistor and the 180 Ω resistor carrying i_3 .

[e] They both dissipate 0.2 W.

P 3.67 [a]

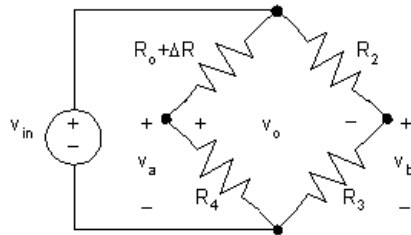

$$v_a = \frac{v_{in} R_4}{R_o + R_4 + \Delta R}$$

$$v_b = \frac{R_3}{R_2 + R_3} v_{in}$$

$$v_o = v_a - v_b = \frac{R_4 v_{in}}{R_o + R_4 + \Delta R} - \frac{R_3}{R_2 + R_3} v_{in}$$

When the bridge is balanced,

$$\frac{R_4}{R_o + R_4} v_{in} = \frac{R_3}{R_2 + R_3} v_{in}$$

$$\therefore \frac{R_4}{R_o + R_4} = \frac{R_3}{R_2 + R_3}$$

$$\begin{aligned} \text{Thus, } v_o &= \frac{R_4 v_{in}}{R_o + R_4 + \Delta R} - \frac{R_4 v_{in}}{R_o + R_4} \\ &= R_4 v_{in} \left[\frac{1}{R_o + R_4 + \Delta R} - \frac{1}{R_o + R_4} \right] \\ &= \frac{R_4 v_{in} (-\Delta R)}{(R_o + R_4 + \Delta R)(R_o + R_4)} \\ &\approx \frac{-(\Delta R) R_4 v_{in}}{(R_o + R_4)^2}, \quad \text{since } \Delta R \ll R_4 \end{aligned}$$

$$[b] \Delta R = 0.03R_o$$

$$R_o = \frac{R_2 R_4}{R_3} = \frac{(1000)(5000)}{500} = 10,000 \Omega$$

$$\Delta R = (0.03)(10^4) = 300 \Omega$$

$$\therefore v_o \approx \frac{-300(5000)(6)}{(15,000)^2} = -40 \text{ mV}$$

$$[c] \begin{aligned} v_o &= \frac{-(\Delta R)R_4 v_{in}}{(R_o + R_4 + \Delta R)(R_o + R_4)} \\ &= \frac{-300(5000)(6)}{(15,300)(15,000)} \\ &= -39.2157 \text{ mV} \end{aligned}$$

$$P 3.68 \quad [a] \text{ approx value} = \frac{-(\Delta R)R_4 v_{in}}{(R_o + R_4)^2}$$

$$\text{true value} = \frac{-(\Delta R)R_4 v_{in}}{(R_o + R_4 + \Delta R)(R_o + R_4)}$$

$$\therefore \frac{\text{approx value}}{\text{true value}} = \frac{(R_o + R_4 + \Delta R)}{(R_o + R_4)}$$

$$\therefore \% \text{ error} = \left[\frac{R_o + R_4}{R_o + R_4 + \Delta R} - 1 \right] \times 100 = \frac{-\Delta R}{R_o + R_4} \times 100$$

Note that in the above expression, we take the ratio of the true value to the approximate value because both values are negative.

$$\text{But } R_o = \frac{R_2 R_4}{R_3}$$

$$\therefore \% \text{ error} = \frac{-R_3 \Delta R}{R_4 (R_2 + R_3)}$$

$$[b] \% \text{ error} = \frac{-(500)(300)}{(5000)(1500)} \times 100 = -2\%$$

$$P 3.69 \quad \frac{\Delta R (R_3)(100)}{(R_2 + R_3)R_4} = 0.5$$

$$\frac{\Delta R (500)(100)}{(1500)(5000)} = 0.5$$

$$\therefore \Delta R = 75 \Omega$$

$$\% \text{ change} = \frac{75}{10,000} \times 100 = 0.75\%$$

P 3.70 [a] From Eq 3.64 we have

$$\left(\frac{i_1}{i_2}\right)^2 = \frac{R_2^2}{R_1^2(1+2\sigma)^2}$$

Substituting into Eq 3.63 yields

$$R_2 = \frac{R_2^2}{R_1^2(1+2\sigma)^2} R_1$$

Solving for R_2 yields

$$R_2 = (1+2\sigma)^2 R_1$$

[b] From Eq 3.67 we have

$$\frac{i_1}{i_b} = \frac{R_2}{R_1 + R_2 + 2R_a}$$

But $R_2 = (1+2\sigma)^2 R_1$ and $R_a = \sigma R_1$ therefore

$$\begin{aligned} \frac{i_1}{i_b} &= \frac{(1+2\sigma)^2 R_1}{R_1 + (1+2\sigma)^2 R_1 + 2\sigma R_1} = \frac{(1+2\sigma)^2}{(1+2\sigma) + (1+2\sigma)^2} \\ &= \frac{1+2\sigma}{2(1+\sigma)} \end{aligned}$$

It follows that

$$\left(\frac{i_1}{i_b}\right)^2 = \frac{(1+2\sigma)^2}{4(1+\sigma)^2}$$

Substituting into Eq 3.66 gives

$$R_b = \frac{(1+2\sigma)^2 R_a}{4(1+\sigma)^2} = \frac{(1+2\sigma)^2 \sigma R_1}{4(1+\sigma)^2}$$

P 3.71 From Eq 3.69

$$\frac{i_1}{i_3} = \frac{R_2 R_3}{D}$$

$$\text{But } D = (R_1 + 2R_a)(R_2 + 2R_b) + 2R_b R_2$$

$$\text{where } R_a = \sigma R_1; R_2 = (1+2\sigma)^2 R_1 \text{ and } R_b = \frac{(1+2\sigma)^2 \sigma R_1}{4(1+\sigma)^2}$$

Therefore D can be written as

$$\begin{aligned}
 D &= (R_1 + 2\sigma R_1) \left[(1 + 2\sigma)^2 R_1 + \frac{2(1 + 2\sigma)^2 \sigma R_1}{4(1 + \sigma)^2} \right] + \\
 &\quad 2(1 + 2\sigma)^2 R_1 \left[\frac{(1 + 2\sigma)^2 \sigma R_1}{4(1 + \sigma)^2} \right] \\
 &= (1 + 2\sigma)^3 R_1^2 \left[1 + \frac{\sigma}{2(1 + \sigma)^2} + \frac{(1 + 2\sigma)\sigma}{2(1 + \sigma)^2} \right] \\
 &= \frac{(1 + 2\sigma)^3 R_1^2}{2(1 + \sigma)^2} \{2(1 + \sigma)^2 + \sigma + (1 + 2\sigma)\sigma\} \\
 &= \frac{(1 + 2\sigma)^3 R_1^2}{(1 + \sigma)^2} \{1 + 3\sigma + 2\sigma^2\}
 \end{aligned}$$

$$D = \frac{(1 + 2\sigma)^4 R_1^2}{(1 + \sigma)}$$

$$\begin{aligned}
 \therefore \frac{i_1}{i_3} &= \frac{R_2 R_3 (1 + \sigma)}{(1 + 2\sigma)^4 R_1^2} \\
 &= \frac{(1 + 2\sigma)^2 R_1 R_3 (1 + \sigma)}{(1 + 2\sigma)^4 R_1^2} \\
 &= \frac{(1 + \sigma) R_3}{(1 + 2\sigma)^2 R_1}
 \end{aligned}$$

When this result is substituted into Eq 3.69 we get

$$R_3 = \frac{(1 + \sigma)^2 R_3^2 R_1}{(1 + 2\sigma)^4 R_1^2}$$

Solving for R_3 gives

$$R_3 = \frac{(1 + 2\sigma)^4 R_1}{(1 + \sigma)^2}$$

P 3.72 From the dimensional specifications, calculate σ and R_3 :

$$\sigma = \frac{y}{x} = \frac{0.025}{1} = 0.025; \quad R_3 = \frac{V_{dc}^2}{p} = \frac{12^2}{120} = 1.2 \Omega$$

Calculate R_1 from R_3 and σ :

$$R_1 = \frac{(1 + \sigma)^2}{(1 + 2\sigma)^4} R_3 = 1.0372 \Omega$$

Calculate R_a , R_b , and R_2 :

$$R_a = \sigma R_1 = 0.0259 \Omega \quad R_b = \frac{(1 + 2\sigma)^2 \sigma R_1}{4(1 + \sigma)^2} = 0.0068 \Omega$$

$$R_2 = (1 + 2\sigma)^2 R_1 = 1.1435 \Omega$$

Using symmetry,

$$R_4 = R_2 = 1.1435 \Omega \quad R_5 = R_1 = 1.0372 \Omega$$

$$R_c = R_b = 0.0068 \Omega \quad R_d = R_a = 0.0259 \Omega$$

Test the calculations by checking the power dissipated, which should be 120 W/m. Calculate D , then use Eqs. (3.58)-(3.60) to calculate i_b , i_1 , and i_2 :

$$D = (R_1 + 2R_a)(R_2 + 2R_b) + 2R_2R_b = 1.2758$$

$$i_b = \frac{V_{dc}(R_1 + R_2 + 2R_a)}{D} = 21 \text{ A}$$

$$i_1 = \frac{V_{dc}R_2}{D} = 10.7561 \text{ A} \quad i_2 = \frac{V_{dc}(R_1 + 2R_a)}{D} = 10.2439 \text{ A}$$

It follows that $i_b^2 R_b = 3 \text{ W}$ and the power dissipation per meter is $3/0.025 = 120 \text{ W/m}$. The value of $i_1^2 R_1 = 120 \text{ W/m}$. The value of $i_2^2 R_2 = 120 \text{ W/m}$. Finally, $i_1^2 R_a = 3 \text{ W/m}$.

- P 3.73 From the solution to Problem 3.72 we have $i_b = 21 \text{ A}$ and $i_3 = 10 \text{ A}$. By symmetry $i_c = 21 \text{ A}$ thus the total current supplied by the 12 V source is $21 + 21 + 10$ or 52 A. Therefore the total power delivered by the source is $p_{12V}(\text{del}) = (12)(52) = 624 \text{ W}$. We also have from the solution that $p_a = p_b = p_c = p_d = 3 \text{ W}$. Therefore the total power delivered to the vertical resistors is $p_V = (8)(3) = 24 \text{ W}$. The total power delivered to the five horizontal resistors is $p_H = 5(120) = 600 \text{ W}$.

$$\therefore \sum p_{\text{diss}} = p_H + p_V = 624 \text{ W} = \sum p_{\text{del}}$$

- P 3.74 [a] $\sigma = 0.03/1.5 = 0.02$

Since the power dissipation is 200 W/m the power dissipated in R_3 must be $200(1.5)$ or 300 W. Therefore

$$R_3 = \frac{12^2}{300} = 0.48 \Omega$$

From Table 3.1 we have

$$R_1 = \frac{(1 + \sigma)^2 R_3}{(1 + 2\sigma)^4} = 0.4269 \Omega$$

$$R_a = \sigma R_1 = 0.0085 \Omega$$

$$R_2 = (1 + 2\sigma)^2 R_1 = 0.4617 \Omega$$

$$R_b = \frac{(1 + 2\sigma)^2 \sigma R_1}{4(1 + \sigma)^2} = 0.0022 \Omega$$

Therefore

$$R_4 = R_2 = 0.4617 \Omega \quad R_5 = R_1 = 0.4269 \Omega$$

$$R_c = R_b = 0.0022 \Omega \quad R_d = R_a = 0.0085 \Omega$$

$$[\mathbf{b}] \quad D = [0.4269 + 2(0.0085)][0.4617 + 2(0.0022)] + 2(0.4617)(0.0022) = 0.2090$$

$$i_1 = \frac{V_{\text{dc}} R_2}{D} = 26.51 \text{ A}$$

$$i_1^2 R_1 = 300 \text{ W or } 200 \text{ W/m}$$

$$i_2 = \frac{R_1 + 2R_a}{D} V_{\text{dc}} = 25.49 \text{ A}$$

$$i_2^2 R_2 = 300 \text{ W or } 200 \text{ W/m}$$

$$i_1^2 R_a = 6 \text{ W or } 200 \text{ W/m}$$

$$i_b = \frac{R_1 + R_2 + 2R_a}{D} V_{\text{dc}} = 52 \text{ A}$$

$$i_b^2 R_b = 6 \text{ W or } 200 \text{ W/m}$$

$$i_{\text{source}} = 52 + 52 + \frac{12}{0.48} = 129 \text{ A}$$

$$p_{\text{del}} = 12(129) = 1548 \text{ W}$$

$$p_H = 5(300) = 1500 \text{ W}$$

$$p_V = 8(6) = 48 \text{ W}$$

$$\sum p_{\text{del}} = \sum p_{\text{diss}} = 1548 \text{ W}$$