

CHAPTER 3

OHM'S LAW, ENERGY, AND POWER

BASIC PROBLEMS

SECTION 3-1 Ohm's Law

1. I is directly proportional to V and will change the same percentage as V .
 - (a) $I = 3(1 \text{ A}) = \mathbf{3 \text{ A}}$
 - (b) $I = 1 \text{ A} - (0.8)(1 \text{ A}) = 1 \text{ A} - 0.8 \text{ A} = \mathbf{0.2 \text{ A}}$
 - (c) $I = 1 \text{ A} + (0.5)(1 \text{ A}) = 1 \text{ A} + 0.5 \text{ A} = \mathbf{1.5 \text{ A}}$
2. (a) When the resistance doubles, the current is halved from 100 mA to **50 mA**.
 (b) When the resistance is reduced by 30%, the current increases from 100 mA to
 $I = V/0.7R = 1.429(V/R) = (1.429)(100 \text{ mA}) \approx \mathbf{143 \text{ mA}}$
 (c) When the resistance is quadrupled, the current decreases from 100 mA to **25 mA**.
3. Tripling the voltage triples the current from 10 mA to 30 mA, but doubling the resistance halves the current to **15 mA**.

SECTION 3-2 Application of Ohm's Law

4. (a) $I = \frac{V}{R} = \frac{5 \text{ V}}{1 \Omega} = \mathbf{5 \text{ A}}$ (b) $I = \frac{V}{R} = \frac{15 \text{ V}}{10 \Omega} = \mathbf{1.5 \text{ A}}$
 (c) $I = \frac{V}{R} = \frac{50 \text{ V}}{100 \Omega} = \mathbf{0.5 \text{ A}}$ (d) $I = \frac{V}{R} = \frac{30 \text{ V}}{15 \text{ k}\Omega} = \mathbf{2 \text{ mA}}$
 (e) $I = \frac{V}{R} = \frac{250 \text{ V}}{4.7 \text{ M}\Omega} = \mathbf{53.2 \mu\text{A}}$
5. (a) $I = \frac{V}{R} = \frac{9 \text{ V}}{2.7 \text{ k}\Omega} = \mathbf{3.33 \text{ mA}}$ (b) $I = \frac{V}{R} = \frac{5.5 \text{ V}}{10 \text{ k}\Omega} = \mathbf{550 \mu\text{A}}$
 (c) $I = \frac{V}{R} = \frac{40 \text{ V}}{68 \text{ k}\Omega} = \mathbf{588 \mu\text{A}}$ (d) $I = \frac{V}{R} = \frac{1 \text{ kV}}{2 \text{ k}\Omega} = \mathbf{500 \text{ mA}}$
 (e) $I = \frac{V}{R} = \frac{66 \text{ kV}}{10 \text{ M}\Omega} = \mathbf{6.60 \text{ mA}}$
6. $I = \frac{V}{R} = \frac{12 \text{ V}}{10 \Omega} = \mathbf{1.2 \text{ A}}$

7. (a) $I = \frac{V}{R} = \frac{25 \text{ V}}{10 \text{ k}\Omega} = 2.50 \text{ mA}$ (b) $I = \frac{V}{R} = \frac{5 \text{ V}}{2.2 \text{ M}\Omega} = 2.27 \mu\text{A}$

(c) $I = \frac{V}{R} = \frac{15 \text{ V}}{1.8 \text{ k}\Omega} = 8.33 \text{ mA}$

8. Orange, violet, yellow, gold, brown $\equiv 37.4 \Omega \pm 1\%$

$$I = \frac{V_s}{R} = \frac{12 \text{ V}}{37.4 \Omega} = 0.321 \text{ A}$$

9. $I = \frac{24 \text{ V}}{37.4 \Omega} = 0.642 \text{ A}$

0.642 A is greater than 0.5 A, so **the fuse will blow.**

10. (a) $V = IR = (2 \text{ A})(18 \Omega) = 36 \text{ V}$ (b) $V = IR = (5 \text{ A})(47 \Omega) = 235 \text{ V}$
 (c) $V = IR = (2.5 \text{ A})(620 \Omega) = 1550 \text{ V}$ (d) $V = IR = (0.6 \text{ A})(47 \Omega) = 28.2 \text{ V}$
 (e) $V = IR = (0.1 \text{ A})(470 \Omega) = 47 \text{ V}$

11. (a) $V = IR = (1 \text{ mA})(10 \Omega) = 10 \text{ mV}$ (b) $V = IR = (50 \text{ mA})(33 \Omega) = 1.65 \text{ V}$
 (c) $V = IR = (3 \text{ A})(4.7 \text{ k}\Omega) = 14.1 \text{ kV}$ (d) $V = IR = (1.6 \text{ mA})(2.2 \text{ k}\Omega) = 3.52 \text{ V}$
 (e) $V = IR = (250 \mu\text{A})(1 \text{ k}\Omega) = 250 \text{ mV}$ (f) $V = IR = (500 \text{ mA})(1.5 \text{ M}\Omega) = 750 \text{ kV}$
 (g) $V = IR = (850 \mu\text{A})(10 \text{ M}\Omega) = 8.5 \text{ kV}$ (h) $V = IR = (75 \mu\text{A})(47 \Omega) = 3.53 \text{ mV}$

12. $V = IR = (3 \text{ A})(20 \text{ m}\Omega) = 60 \text{ mV}$

13. (a) $V = IR = (3 \text{ mA})(27 \text{ k}\Omega) = 81 \text{ V}$ (b) $V = IR = (5 \mu\text{A})(100 \text{ M}\Omega) = 500 \text{ V}$
 (c) $V = IR = (2.5 \text{ A})(47 \Omega) = 117.5 \text{ V}$

14. (a) $R = \frac{V}{I} = \frac{10 \text{ V}}{2 \text{ A}} = 5 \Omega$ (b) $R = \frac{V}{I} = \frac{90 \text{ V}}{45 \text{ A}} = 2 \Omega$
 (c) $R = \frac{V}{I} = \frac{50 \text{ V}}{5 \text{ A}} = 10 \Omega$ (d) $R = \frac{V}{I} = \frac{5.5 \text{ V}}{10 \text{ A}} = 0.55 \Omega$
 (e) $R = \frac{V}{I} = \frac{150 \text{ V}}{0.5 \text{ A}} = 300 \Omega$

15. (a) $R = \frac{V}{I} = \frac{10 \text{ kV}}{5 \text{ A}} = 2 \text{ k}\Omega$ (b) $R = \frac{V}{I} = \frac{7 \text{ V}}{2 \text{ mA}} = 3.5 \text{ k}\Omega$
 (c) $R = \frac{V}{I} = \frac{500 \text{ V}}{250 \text{ mA}} = 2 \text{ k}\Omega$ (d) $R = \frac{V}{I} = \frac{50 \text{ V}}{500 \mu\text{A}} = 100 \text{ k}\Omega$
 (e) $R = \frac{V}{I} = \frac{1 \text{ kV}}{1 \text{ mA}} = 1 \text{ M}\Omega$

16. $R = \frac{V}{I} = \frac{6\text{ V}}{2\text{ mA}} = 3\text{ k}\Omega$

17. (a) $R = \frac{V}{I} = \frac{8\text{ V}}{2\text{ A}} = 4\text{ }\Omega$ (b) $R = \frac{V}{I} = \frac{12\text{ V}}{4\text{ mA}} = 3\text{ k}\Omega$

(c) $R = \frac{V}{I} = \frac{30\text{ V}}{150\mu\text{A}} = 0.2\text{ M}\Omega = 200\text{ k}\Omega$

18. $I = \frac{V}{R} = \frac{3.2\text{ V}}{3.9\text{ }\Omega} = 0.82\text{ A}$

SECTION 3-3 Energy and Power

19. $P = \frac{W}{t} = \frac{26\text{ J}}{10\text{ s}} = 2.6\text{ W}$

20. Since 1 watt = 1 joule, $P = 350\text{ J/s} = 350\text{ W}$

21. $P = \frac{W}{t} = \frac{7500\text{ J}}{5\text{ h}}$
 $\left(\frac{7500\text{ J}}{5\text{ h}}\right)\left(\frac{1\text{ h}}{3600\text{ s}}\right) = \frac{7500\text{ J}}{18,000\text{ s}} = 0.417\text{ J/s} = 417\text{ mW}$

22. (a) $1000\text{ W} = 1 \times 10^3\text{ W} = 1\text{ kW}$ (b) $3750\text{ W} = 3.750 \times 10^3\text{ W} = 3.75\text{ kW}$
(c) $160\text{ W} = 0.160 \times 10^3\text{ W} = 0.160\text{ kW}$ (d) $50,000\text{ W} = 50 \times 10^3\text{ W} = 50\text{ kW}$

23. (a) $1,000,000\text{ W} = 1 \times 10^6\text{ W} = 1\text{ MW}$ (b) $3 \times 10^6\text{ W} = 3\text{ MW}$
(c) $15 \times 10^7\text{ W} = 150 \times 10^6\text{ W} = 150\text{ MW}$ (d) $8700\text{ kW} = 8.7 \times 10^6\text{ W} = 8.7\text{ MW}$

24. (a) $1\text{ W} = 1000 \times 10^{-3}\text{ W} = 1000\text{ mW}$ (b) $0.4\text{ W} = 400 \times 10^{-3}\text{ W} = 400\text{ mW}$
(c) $0.002\text{ W} = 2 \times 10^{-3}\text{ W} = 2\text{ mW}$ (d) $0.0125\text{ W} = 12.5 \times 10^{-3}\text{ W} = 12.5\text{ mW}$

25. (a) $2\text{ W} = 2,000,000\text{ }\mu\text{W}$ (b) $0.0005\text{ W} = 500\text{ }\mu\text{W}$
(c) $0.25\text{ mW} = 250\text{ }\mu\text{W}$ (d) $0.00667\text{ mW} = 6.67\text{ }\mu\text{W}$

26. (a) $1.5\text{ kW} = 1.5 \times 10^3\text{ W} = 1500\text{ W}$ (b) $0.5\text{ MW} = 0.5 \times 10^6\text{ W} = 500,000\text{ W}$
(c) $350\text{ mW} = 350 \times 10^{-3}\text{ W} = 0.350\text{ W}$ (d) $9000\text{ }\mu\text{W} = 9000 \times 10^{-6}\text{ W} = 0.009\text{ W}$

$$27. \quad P = \frac{W}{t} \text{ in watts}$$

$$V = \frac{W}{Q}$$

$$I = \frac{Q}{t}$$

$$P = VI = \frac{W}{t}$$

So, (1 V)(1 A) = 1 W

$$28. \quad P = \frac{W}{t} = \frac{1 \text{ J}}{1 \text{ s}} = 1 \text{ W}$$

$$1 \text{ kW} = 1000 \text{ W} = \frac{1000 \text{ J}}{1 \text{ s}}$$

$$1 \text{ kW-second} = 1000 \text{ J}$$

$$1 \text{ kWh} = 3600 \times 1000 \text{ J}$$

$$\mathbf{1 \text{ kWh} = 3.6 \times 10^6 \text{ J}}$$

SECTION 3-4 Power in an Electric Circuit

$$29. \quad P = VI = (5.5 \text{ V})(3 \text{ mA}) = \mathbf{16.5 \text{ mW}}$$

$$30. \quad P = VI = (115 \text{ V})(3 \text{ A}) = \mathbf{345 \text{ W}}$$

$$31. \quad P = I^2R = (500 \text{ mA})^2(4.7 \text{ k}\Omega) = \mathbf{1.18 \text{ kW}}$$

$$32. \quad P = I^2R = (5.0 \text{ A})^2(20 \times 10^{-3} \Omega) = \mathbf{500 \text{ mW}}$$

$$33. \quad P = \frac{V^2}{R} = \frac{(60 \text{ V})^2}{620 \Omega} = \mathbf{5.81 \text{ W}}$$

$$34. \quad P = \frac{V^2}{R} = \frac{(1.5 \text{ V})^2}{56 \Omega} = 0.0402 \text{ W} = \mathbf{40.2 \text{ mW}}$$

$$35. \quad P = I^2R$$

$$R = \frac{P}{I^2} = \frac{100 \text{ W}}{(2 \text{ A})^2} = \mathbf{25 \Omega}$$

36. 5×10^6 watts for 1 minute = 5×10^3 kWmin

$$\frac{5 \times 10^3 \text{ kWmin}}{60 \text{ min/1 hr}} = \mathbf{83.3 \text{ kWh}}$$

37. $\frac{6700 \text{ W/s}}{(1000 \text{ W/kW})(3600 \text{ s/h})} = \mathbf{0.00186 \text{ kWh}}$

38. $(50 \text{ W})(12 \text{ h}) = \mathbf{600 \text{ Wh}}$
 $50 \text{ W} = 0.05 \text{ kW}$
 $(0.05 \text{ kW})(12 \text{ h}) = \mathbf{0.6 \text{ kWh}}$

39. $I = \frac{V}{R_L} = \frac{1.25 \text{ V}}{10 \Omega} = 0.125 \text{ A}$

$$P = VI = (1.25 \text{ V})(0.125 \text{ A}) = 0.156 \text{ W} = \mathbf{156 \text{ mW}}$$

40. $P = \frac{W}{t}$

$$156 \text{ mW} = \frac{156 \text{ mJ}}{1 \text{ s}}$$

$$W_{\text{tot}} = (156 \text{ mJ/s})(90 \text{ h})(3600 \text{ s/h}) = \mathbf{50,544 \text{ J}}$$

SECTION 3-5 The Power Rating of Resistors

41. $P = I^2R = (10 \text{ mA})^2(6.8 \text{ k}\Omega) = 0.68 \text{ W}$

Use the next highest standard power rating of **1 W**.

42. If the 8 W resistor is used, it will be operating in a marginal condition.
To allow for a **safety margin of 20%**, use a **12 W** resistor.

SECTION 3-6 Energy Conversion and Voltage Drop in a Resistance

43. (a) + at top, - at bottom of resistor (b) + at bottom, - at top of resistor

- (c) + on right, - on left of resistor

SECTION 3-7 Power Supplies and Batteries

44. $V_{\text{OUT}} = \sqrt{P_L R_L} = \sqrt{(1 \text{ W})(50 \Omega)} = \mathbf{7.07 \text{ V}}$

45. Ampere-hour rating = $(1.5 \text{ A})(24 \text{ h}) = \mathbf{36 \text{ Ah}}$

$$46. \quad I = \frac{80 \text{ Ah}}{10 \text{ h}} = \mathbf{8 \text{ A}}$$

$$47. \quad I = \frac{650 \text{ mAh}}{48 \text{ h}} = \mathbf{13.5 \text{ mA}}$$

$$48. \quad P_{\text{LOST}} = P_{\text{IN}} - P_{\text{OUT}} = 500 \text{ mW} - 400 \text{ mW} = \mathbf{100 \text{ mW}}$$

$$\% \text{ efficiency} = \left(\frac{P_{\text{OUT}}}{P_{\text{IN}}} \right) 100\% = \left(\frac{400 \text{ mW}}{500 \text{ mW}} \right) 100\% = \mathbf{80\%}$$

$$49. \quad P_{\text{OUT}} = (\text{efficiency})P_{\text{IN}} = (0.85)(5 \text{ W}) = \mathbf{4.25 \text{ W}}$$

SECTION 3-8 Introduction to Troubleshooting

50. The 4th bulb from the left is open.

51. If should take **five** (maximum) resistance measurements.

ADVANCED PROBLEMS

52. Assume that the total consumption of the power supply is the input power plus the power lost.

$$P_{\text{OUT}} = 2 \text{ W}$$

$$\% \text{ efficiency} = \left(\frac{P_{\text{OUT}}}{P_{\text{IN}}} \right) 100\%$$

$$P_{\text{IN}} = \left(\frac{P_{\text{OUT}}}{\% \text{ efficiency}} \right) 100\% = \left(\frac{2 \text{ W}}{60\%} \right) 100\% = 3.33 \text{ W}$$

The power supply itself uses

$$P_{\text{IN}} - P_{\text{OUT}} = 3.33 \text{ W} - 2 \text{ W} = 1.33 \text{ W}$$

$$\text{Energy} = W = Pt = (1.33 \text{ W})(24 \text{ h}) = 31.9 \text{ Wh} \cong \mathbf{0.032 \text{ kWh}}$$

$$53. \quad R_f = \frac{V}{I} = \frac{120 \text{ V}}{0.8 \text{ A}} = \mathbf{150 \Omega}$$

54. Measure the current with an ammeter connected as shown in Figure 3-1. Then calculate the unknown resistance with the formula, $R = 12 \text{ V}/I$.

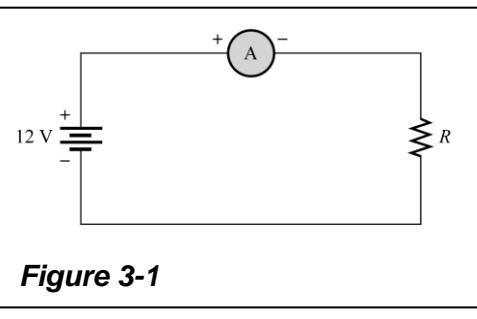


Figure 3-1

55. Calculate I for each value of V :

$$\begin{array}{ll} I_1 = \frac{0 \text{ V}}{100\Omega} = 0 \text{ A} & I_2 = \frac{10 \text{ V}}{100\Omega} = 100 \text{ mA} \\ I_3 = \frac{20 \text{ V}}{100\Omega} = 200 \text{ mA} & I_4 = \frac{30 \text{ V}}{100\Omega} = 300 \text{ mA} \\ I_5 = \frac{40 \text{ V}}{100\Omega} = 400 \text{ mA} & I_6 = \frac{50 \text{ V}}{100\Omega} = 500 \text{ mA} \\ I_7 = \frac{60 \text{ V}}{100\Omega} = 600 \text{ mA} & I_8 = \frac{70 \text{ V}}{100\Omega} = 700 \text{ mA} \\ I_9 = \frac{80 \text{ V}}{100\Omega} = 800 \text{ mA} & I_{10} = \frac{90 \text{ V}}{100\Omega} = 900 \text{ mA} \\ I_{11} = \frac{100 \text{ V}}{100\Omega} = 1 \text{ A} & \end{array}$$

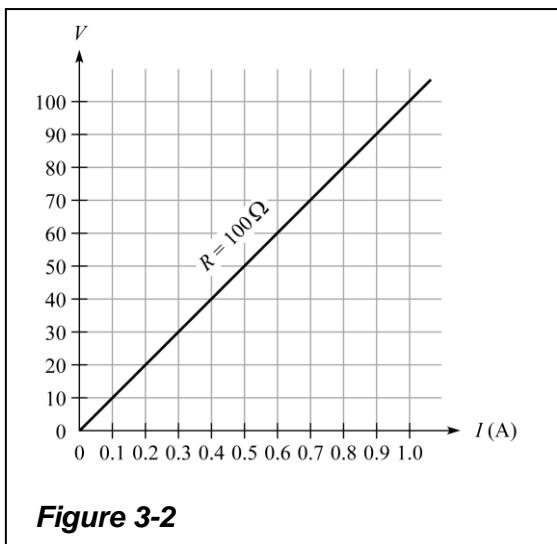


Figure 3-2

The graph is a straight line as shown in Figure 3-2. This indicates a *linear* relationship between I and V .

56. $R = \frac{V_s}{I} = \frac{1\text{ V}}{5\text{ mA}} = 200\Omega$

(a) $I = \frac{V_s}{R} = \frac{1.5\text{ V}}{200\Omega} = 7.5\text{ mA}$

(b) $I = \frac{V_s}{R} = \frac{2\text{ V}}{200\Omega} = 10\text{ mA}$

(c) $I = \frac{V_s}{R} = \frac{3\text{ V}}{200\Omega} = 15\text{ mA}$

(d) $I = \frac{V_s}{R} = \frac{4\text{ V}}{200\Omega} = 20\text{ mA}$

(e) $I = \frac{V_s}{R} = \frac{10\text{ V}}{200\Omega} = 50\text{ mA}$

57. $R_1 = \frac{V}{I} = \frac{1\text{ V}}{2\text{ A}} = 0.5\Omega$ $R_2 = \frac{V}{I} = \frac{1\text{ V}}{1\text{ A}} = 1\Omega$ $R_3 = \frac{V}{I} = \frac{1\text{ V}}{0.5\text{ A}} = 2\Omega$

58. $\frac{V_2}{30\text{ mA}} = \frac{10\text{ V}}{50\text{ mA}}$

$$V_2 = \frac{(10\text{ V})(30\text{ mA})}{50\text{ mA}} = 6\text{ V} \quad \text{new value}$$

The voltage decreased by 4 V, from 10 V to 6 V.

59. The current increase is 50%, so the voltage increase must be the same; that is, the voltage must be increased by $(0.5)(20\text{ V}) = 10\text{ V}$.

The new value of voltage is $V_2 = 20\text{ V} + (0.5)(20\text{ V}) = 20\text{ V} + 10\text{ V} = 30\text{ V}$

60. Wire resistance: $R_w = \frac{(10.4\text{ CM} \cdot \Omega/\text{ft})(24\text{ ft})}{1624.3\text{ CM}} = 0.154\Omega$

(a) $I = \frac{V}{R + R_w} = \frac{6\text{ V}}{100.154\Omega} = 59.9\text{ mA}$

(b) $V_R = (59.9\text{ mA})(100\Omega) = 5.99\text{ V}$

(c) $V_{R_w} = 6\text{ V} - 5.99\text{ V} = 0.01\text{ V}$

For one length of wire, $V = \frac{0.01\text{ V}}{2} = 0.005\text{ V}$

61. $300\text{ W} = 0.3\text{ kW}$

$30\text{ days} = (30\text{ days})(24\text{ h/day}) = 720\text{ h}$

Energy = $(0.3\text{ kW})(720\text{ h}) = 216\text{ kWh}$

62. $\frac{1500\text{ kWh}}{31\text{ days}} = 48.39\text{ kWh/day}$

$P = \frac{48.39\text{ kWh/day}}{24\text{ h/day}} = 2.02\text{ kW}$

63. The minimum power rating you should use is **12 W** so that the power dissipation does not exceed the rating.

64. (a) $P = \frac{V^2}{R} = \frac{(12\text{ V})^2}{10\Omega} = \mathbf{14.4\text{ W}}$

(b) $W = Pt = (14.4\text{ W})(2\text{ min})(1/60\text{ h/min}) = \mathbf{0.48\text{ Wh}}$

(c) Neither, the power is the same because it is not time dependent.

65. $V_{R(\max)} = 120\text{ V} - 100\text{ V} = 20\text{ V}$

$$I_{\max} = \frac{V_{R(\max)}}{R_{\min}} = \frac{20\text{ V}}{8\Omega} = 2.5\text{ A}$$

A fuse with a rating of less than 2.5 A must be used. **A 2 A fuse is recommended.**


66. $I = \sqrt{\frac{P}{R}} = \sqrt{\frac{0.5\text{ W}}{0.030\Omega}} = \mathbf{4.08\text{ A}}$

67. Power will increase by four times.

66. The materials required for the Load Test Box are as follows:

Item	Component	Qty
1	Resistor: 5.0Ω , 10 W	1
2	Resistor: 16Ω , 5 W	1
3	Resistor: 100Ω , 2.0 W	1
4	Resistor: 150Ω , 3.0 W	1
5	1 pole, 4 position rotary switch	1
6	Knob	1
7	Enclosure (4" x 4" x 2" Al)	1
8	Banana plug terminals	2
9	Fuse (1.5 A) and fuse holder	1
10	PC board (etched with pattern)	1
11	Screws, washers, nuts	4
12	Standoffs	4

69. See Figure 3-3.

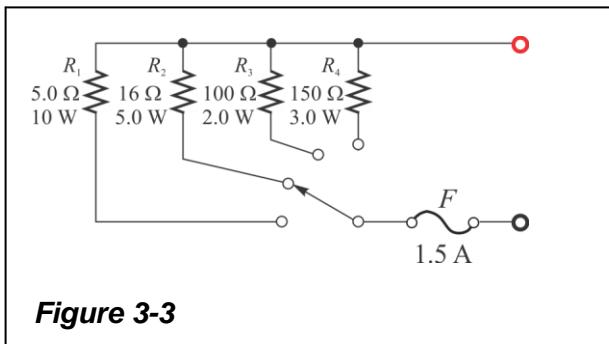

Multisim Troubleshooting Problems

70. R is open.
71. No fault
72. R_1 is shorted.
73. Lamp 4 is shorted.
74. Lamp 6 is open.