

Chapter 02 Test Bank: Electronic Fundamentals for Communications KEY

1. Gain means attenuation.

FALSE

Blooms: 3. Apply
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.01 Gain, Attenuation, and Decibels
Subtopic: Gain, Attenuation, and Decibels
Topic: Electronic Fundamentals for Communications

2. Circuits that introduce attenuation have a gain that is less than 1.

TRUE

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.01 Gain, Attenuation, and Decibels
Subtopic: Gain, Attenuation, and Decibels
Topic: Electronic Fundamentals for Communications

3. The gain or loss of a circuit is usually expressed in volts (V).

FALSE

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Subtopic: Gain, Attenuation, and Decibels
Topic: Electronic Fundamentals for Communications

4. When a decibel value is computed by comparing a power value to 1 mW, the result is a value called the dBm.

TRUE

Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.01 Gain, Attenuation, and Decibels
Subtopic: Gain, Attenuation, and Decibels
Topic: Electronic Fundamentals for Communications

5. Both coils and capacitors offer an opposition to alternating current flow known as resistance.

FALSE

*Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

6. The basic unit of inductance is the henry.

TRUE

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

7. The tendency of electrons flowing in a conductor to flow near and on the outer surface of a conductor at very high frequencies is called skin effect.

TRUE

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

8. Resonance in a series tuned circuit is the point at which X_L equals X_C .

TRUE

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

9. The bandwidth of a resonant circuit defines its selectivity.

TRUE

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

10. The bandwidth of a circuit is directly proportional to Q.

FALSE

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

11. A frequency-selective circuit designed to pass some frequencies and reject others is a(n)

- A. tank circuit
- B.** filter
- C. harmonic circuit
- D. frequency doubler

*Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications*

12. A circuit that rejects or stops frequencies over a narrow range but allows frequencies above and below to pass is the

- A. high-pass filter
- B. bandpass filter
- C.** band-reject filter
- D. all-pass filter

Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications

13. The signal attenuation in the passband of a filter is called

- A.** insertion loss
- B. roll-off loss
- C. notch loss
- D. impedance

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications

14. Which of the following is also known as a notch filter?

- A. low-pass
- B. high-pass
- C. bandpass
- D.** band-reject

*Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications*

15. The rate of change of amplitude with frequency in a filter is the

- A. shape factor
- B.** roll-off
- C. insertion loss
- D. attenuation

*Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications*

16. Which of the following, also known as a Thomson filter, provides the desired frequency response but has a constant time delay in the passband?

A. Butterworth

B. Chebyshev

C. Cauer

D. Bessel

*Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications*

17. Which of the following is not an advantage of an active filter?

A. gain

B. easy to tune

C. use of inductors

D. isolation

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications*

18. Which of the following filter is used to supply signals on exact frequencies with good stability?

A. RC low-pass

B. Bessel

C. crystal

D. LC notch

*Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications*

19. Which of the following filter is very small and inexpensive and widely used in communication transmitters and receivers?

A. Bessel

B. Butterworth

C. LC

D. ceramic

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications*

20. Which of the following is a fixed tuned bandpass filter that is designed to provide the exact selectivity required by a given application?

A. Bessel

B. surface acoustic wave

C. switched capacitor filters

D. ceramic

Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications

21. The primary advantage of **SCFs** is that they provide a way to make tuned or selective circuits in an IC without the use of discrete inductors, capacitors, or resistors.

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications

22. One characteristic of the commutating filter is that it is sensitive to the **harmonics** of the center frequency for which it is designed.

Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.03 Filters
Subtopic: Filters
Topic: Electronic Fundamentals for Communications

23. A non-sine wave approach used to determine the characteristics and performance of any communication circuit or system is **Fourier** analysis.

Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.04 Fourier Theory
Subtopic: Fourier Theory
Topic: Electronic Fundamentals for Communications

24. Most signals and waveforms discussed and analyzed are expressed in the **time** domain.

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.04 Fourier Theory
Subtopic: Fourier Theory
Topic: Electronic Fundamentals for Communications

25. The bandwidth of a rectangular wave is equal to 0.35 divided by **rise** time.

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Hard
Section: 02.04 Fourier Theory
Subtopic: Fourier Theory
Topic: Electronic Fundamentals for Communications

26. When two or more stages of amplification are cascaded, the overall gain of the combination is the **product** of the individual circuit gains.

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.01 Gain, Attenuation, and Decibels
Subtopic: Gain, Attenuation, and Decibels
Topic: Electronic Fundamentals for Communications

27. **Attenuation** refers to a loss introduced by a circuit or component.

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.01 Gain, Attenuation, and Decibels
Subtopic: Gain, Attenuation, and Decibels
Topic: Electronic Fundamentals for Communications

28. When gain is converted to decibels, the overall gain of an electronic circuit can be computed by **adding** the individual gains expressed in decibels.

Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.01 Gain, Attenuation, and Decibels
Subtopic: Gain, Attenuation, and Decibels
Topic: Electronic Fundamentals for Communications

29. When a decibel value is computed by comparing a power value to 1 mW, the result is a value called the **dBm**.

Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.01 Gain, Attenuation, and Decibels
Subtopic: Gain, Attenuation, and Decibels
Topic: Electronic Fundamentals for Communications

30. Circuits made up of inductors and capacitors that resonate at specific frequencies are called **tuned** circuits.

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

31. The reactance of a capacitor is **inversely** proportional to the value of capacitance and operating frequency.

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

32. A(n) **inductor** also called a coil or choke is simply a winding of multiple turns of wire.

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

33. An important characteristic of an inductor is the ratio of inductive power to resistive power referred to as its **quality** factor.

*Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Medium
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

34. When the inductive and capacitive reactances are equal, **resonance** occurs.

*Blooms: 2. Understand
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

35. The **bandwidth** of a tuned circuit is defined as the difference between its upper and lower cutoff frequencies.

*Blooms: 1. Remember
Chapter: 02 Electronic Fundamentals for Communications
Difficulty: Easy
Section: 02.02 Tuned Circuits
Subtopic: Tuned Circuits
Topic: Electronic Fundamentals for Communications*

Chapter 02 Test Bank: Electronic Fundamentals for Communications Summary

<u>Category</u>	<u># of Questions</u>
Blooms: 1. Remember	17
Blooms: 2. Understand	17
Blooms: 3. Apply	1
Chapter: 02 Electronic Fundamentals for Communications	35
Difficulty: Easy	16
Difficulty: Hard	9
Difficulty: Medium	10
Section: 02.01 Gain, Attenuation, and Decibels	7
Section: 02.02 Tuned Circuits	12
Section: 02.03 Filters	12
Section: 02.04 Fourier Theory	3
Subtopic: Filters	12
Subtopic: Fourier Theory	3
Subtopic: Gain, Attenuation, and Decibels	8
Subtopic: Tuned Circuits	12
Topic: Electronic Fundamentals for Communications	35